



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 1 / 22     |

Copyright ©2017. cAAS. All rights reserved.

Ref No:

< Sri Krishna Institute of Technology, Bengaluru >



## COURSE PLAN

Academic Year 2018-2019

|                      |  |
|----------------------|--|
| Program:             | B E – Electrical & Electronics Engineering |
| Semester :           | 2 <sup>nd</sup>                            |
| Course Code:         | 18ELEL27                                   |
| Course Title:        | Basic Electrical Engineering Laboratory    |
| Credit / L-T-P:      | 1 / 0-0-2                                  |
| Total Contact Hours: | 30   |
| Course Plan Author:  | AVINASH S                                  |

Academic Evaluation and Monitoring Cell

No.29, Hesaraghatta Main  
Road, Chimney Hills,  
Chikkabanavara Post

Bengaluru – 560090, Karnataka, INDIA

Phone / Fax :+91 90367 90005 , 0802839 2221, 2372 1315,

2372 1477 / 080 28392221

Web: skit1princi@gmail.com

[principal@skit.org.in](mailto:principal@skit.org.in)



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 2 / 22     |

Copyright ©2017. CAAS. All rights reserved.

## Table of Contents

|  |    |
|--|----|
| 18ELE27/27 : Basic Electrical Engineering Lab..... | 4  |
| A. COURSE INFORMATION                              |    |
| 1. Course Overview.....                            | 4  |
| 2. Course Content.....                             | 4  |
| 3. Course Material.....                            | 5  |
| 4. Course Prerequisites.....                       | 6  |
| B. OBE PARAMETERS.....                             | 6  |
| 1. Course Outcomes.....                            | 6  |
| 2. Course Applications.....                        | 7  |
| 3. Articulation Matrix.....                        | 7  |
| 4. Mapping Justification.....                      | 8  |
| 5. Curricular Gap and Content.....                 | 9  |
| 6. Content Beyond Syllabus.....                    | 9  |
| C. COURSE ASSESSMENT.....                          | 9  |
| 1. Course Coverage.....                            | 9  |
| 2. Continuous Internal Assessment (CIA).....       | 10 |
| D1. TEACHING PLAN - 1.....                         | 10 |
| Module - 1.....                                    | 10 |
| Module - 2.....                                    | 11 |
| E1. CIA EXAM - 1.....                              | 12 |
| a. Model Question Paper - 1.....                   | 12 |
| b. Assignment -1.....                              | 13 |
| D2. TEACHING PLAN - 2.....                         | 15 |
| Module - 3.....                                    | 15 |
| Module - 4.....                                    | 16 |
| E2. CIA EXAM - 2.....                              | 17 |
| a. Model Question Paper - 2.....                   | 17 |
| b. Assignment - 2.....                             | 18 |
| D3. TEACHING PLAN - 3.....                         | 20 |
| Module - 5.....                                    | 20 |
| E3. CIA EXAM - 3.....                              | 21 |
| a. Model Question Paper - 3.....                   | 21 |
| b. Assignment - 3.....                             | 22 |
| F. EXAM PREPARATION.....                           | 24 |
| 1. University Model Question Paper.....            | 24 |
| 2. SEE Important Questions.....                    | 26 |
| 1. TLPA Parameters.....                            | 28 |
| 2. Concepts and Outcomes:.....                     | 29 |

Note : Remove "Table of Content" before including in CP Book  
Each Laboratory Plan shall be printed and made into a book with cover page  
Blooms Level in all sections match with A.2, only if you plan to teach / learn at higher levels



|                          |                  |                  |
|--------------------------|------------------|------------------|
| INST                     | Teaching Process | Rev No.: 1.0     |
| Doc Code: INST.Ph5b1.F03 |                  | Date: 11-07-2018 |
| Title: Course Lab Manual |                  | Page: 3 / 22     |

Copyright ©2017, CAAS. All rights reserved.

## 18ELEL27 : BASIC ELECTRICAL ENGINEERING LAB

### A. LABORATORY INFORMATION

#### 1. Lab Overview

|                      |                                  |                |                |
|----------------------|----------------------------------|----------------|----------------|
| Degree:              | B.Tech                           | Program:       | EE             |
| Year / Semester :    | 1 / 1                            | Academic Year: | 2019-20        |
| Course Title:        | Basic Electrical Engineering Lab | Course Code:   | 18ELEL27       |
| Credit / L-T-P:      | 1 / 0-0-2                        | SEE Duration:  | 180 Minutes    |
| Total Contact Hours: | 30 Hrs                           | SEE Marks:     | 60 Marks       |
| CIA Marks:           | 40                               | Assignment     | 1 / experiment |
| Course Plan Author:  | Mr. Avinash S                    | Sign           | Dt :           |
| Checked By:          |                                  | Sign           | Dt :           |

#### 2. Lab Content

| Unit | Title of the Experiments   | Lab Hours | Concept                               | Blooms Level |
|------|--|-----------|---------------------------------------|--------------|
| 1    | VERIFICATION OF KCL AND KVL FOR DC CIRCUITS.   | 3         | DC circuits                           | L3           |
| 2    | MEASUREMENT OF CURRENT, POWER AND POWER FACTOR OF INCANDESCENT LAMP, FLUORESCENT LAMP AND LED LAMP | 3         | Measurements of Electrical Quantities | L2           |
| 3    | MEASUREMENT OF RESISTANCE AND INDUCTANCE OF A CHOKE COIL USING 3-VOLTMETER METHOD                  | 3         | Choke Coil                            | L2           |
| 4    | DETERMINATION OF PHASE AND LINE QUANTITIES IN THREE PHASE STAR AND DELTA CONNECTION                | 3         | Star-delta connection                 | L3           |
| 5    | MEASUREMENT OF THREE PHASE POWER USING TWO WATTMETER METHOD  | 3         | 3phase power                          | L2           |
| 6    | TWO WAY AND THREE WAY CONTROL OF LAMP  | 3         | Lamp control                          | L2           |
| 7    | MEASUREMENT OF EARTH RESISTANCE  | 3         | Earth resistance                      | L2           |
| 8    | STUDY OF EFFECT OF OPEN AND SHORT CIRCUITS IN SIMPLE CIRCUITS                                      | 3         | OC & SC                               | L2           |
|      |  |           |                                       |              |

#### 3. Lab Material

| Expt.           | Details  | Expt. in book | Availability     |
|-----------------|--|---------------|------------------|
| <b>A</b>        | <b>Text books (Title, Authors, Edition, Publisher, Year.)</b>  | -             | -                |
| 2,6,7,9,10      | 1 Basic Electrical Engineering D C Kulshreshtha Tata McGraw Hill, Revised First Edition                              | -             | In Lib / In Dept |
| 1,3,4,5,8,11,12 | 2 Principles of Electrical Engineering & Electronics V.K. Mehta, Rohit S.ChandPublications                           | -             | In Lib/ In dept  |
| <b>B</b>        | <b>Reference books (Title, Authors, Edition, Publisher, Year.)</b>   | -             | -                |
| 12              | 1 Fundamentals of Electrical Engineering and Electronics B. L. Theraja S. Chand & Company Ltd, Reprint Edition 2013. | -             | In Lib           |
| 8,              | 2 Electrical Technology E. Hughes International Students 9 <sup>th</sup> Edition, Pearson, 2005                      | -             | In Lib           |

EE

Prepared by Avinash S

Checked by

Approved



|                          |                  |                  |
|--------------------------|------------------|------------------|
| INST                     | Teaching Process | Rev No.: 1.0     |
| Doc Code: INST.Ph5b1.F03 |                  | Date: 11-07-2018 |
| Title: Course Lab Manual |                  | Page: 4 / 22     |

Copyright ©2017, cAAS. All rights reserved.

|          |   |   |                               |
|----------|---|---|-------------------------------|
| 3        | Basic Electrical Engineering D. P. Kothari and I. J. Nagrath Tata McGraw Hill, 2017.  | -   | In lib                        |
| <b>C</b> | <b>Concept Videos or Simulation for Understanding</b>   | -   | -                             |
|          | Ohm's law by Dc circuits<br><a href="https://www.youtube.com/watch?v=liLj7NS4DI">https://www.youtube.com/watch?v=liLj7NS4DI</a>   |   |                               |
|          | Measurement of electrical quantities of different lamps   |   |                               |
|          | Resistance and Inductance of choke coil<br><a href="https://www.youtube.com/watch?v=LY_itjFKLM">https://www.youtube.com/watch?v=LY_itjFKLM</a>  |   |                               |
|          | Control methods of Lamps<br><a href="https://www.youtube.com/watch?v=6z-R7pZUIDs">https://www.youtube.com/watch?v=6z-R7pZUIDs</a>   |   |                               |
|          | Star and Delta connection<br><a href="https://www.youtube.com/watch?v=9b17eqCT4-g">https://www.youtube.com/watch?v=9b17eqCT4-g</a><br><a href="https://www.youtube.com/watch?v=9b17eqCT4-g">https://www.youtube.com/watch?v=9b17eqCT4-g</a>     |   |                               |
|          | Measurements of 3 phase power<br><a href="https://www.youtube.com/watch?v=oBMU1qLzFhg">https://www.youtube.com/watch?v=oBMU1qLzFhg</a><br><a href="https://www.youtube.com/watch?v=784LkH03L1E">https://www.youtube.com/watch?v=784LkH03L1E</a> |   |                               |
|          | Earth Resistance<br><a href="https://www.youtube.com/watch?v=aXhT9UT9Ld8">https://www.youtube.com/watch?v=aXhT9UT9Ld8</a><br><a href="https://www.youtube.com/watch?v=M3fWNAIKGaM">https://www.youtube.com/watch?v=M3fWNAIKGaM</a>              |   |                               |
|          | OC and SC test<br><a href="https://www.youtube.com/watch?v=_wevDhc_rGo">https://www.youtube.com/watch?v=_wevDhc_rGo</a><br><a href="https://www.youtube.com/watch?v=ghBmgdGjt1Y">https://www.youtube.com/watch?v=ghBmgdGjt1Y</a>                |   |                               |
| <b>D</b> | <b>Software Tools for Design</b>  | -   | -                             |
|          | -   |   |                               |
| <b>E</b> | <b>Recent Developments for Research</b>   | -   | -                             |
|          |   |   |                               |
| <b>F</b> | <b>Others (Web, Video, Simulation, Notes etc.)</b>  |   |                               |
|          | Nptel online video lecture  | Www.on<br>linecour<br>ses.nptel<br>.ac.in | Nptel online<br>video lecture |

#### 4. Lab Prerequisites:

| SNo | Course Code | Base Course: Course Name | Topic / Description | Sem | Remarks |
|-----|-------------|--------------------------|---------------------|-----|---------|
|     |             | -                        | -                   |     |         |

Note: If prerequisites are not taught earlier, GAP in curriculum needs to be addressed. Include in Remarks and implement in B.5.

#### 5. General Instructions

| SNo | Instructions  | Remarks |
|-----|---|---------|
| 1   | Observation book and Lab record are compulsory.   |         |
| 2   | Students should report to the concerned lab as per the time table.  |         |
| 3   | After completion of the program, certification of the concerned staff in-charge in the observation book is necessary.   |         |
| 4   | Student should bring a notebook of 100 pages and should enter the readings /observations into the notebook while performing the experiment.   |         |
| 5   | The record of observations along with the detailed experimental procedure of the experiment in the Immediate last session should be submitted and certified staff member in-charge. |         |
| 6   | Should attempt all problems / assignments given in the list session wise.   |         |
| 7   | It is responsibility to create a separate directory to store all the programs, so   |         |

EE

Prepared by Avinash S

Checked by

Approved



|                          |                  |                  |
|--------------------------|------------------|------------------|
| INST                     | Teaching Process | Rev No.: 1.0     |
| Doc Code: INST.Ph5b1.F03 |                  | Date: 11-07-2018 |
| Title: Course Lab Manual |                  | Page: 5 / 22     |

Copyright ©2017, CAAS. All rights reserved.

|    |  |  |
|----|--|--|
|    | that nobody else can read or copy.   |  |
| 8  | When the experiment is completed, should disconnect the setup made by them, and should return all the components/instruments taken for the purpose.                                      |  |
| 9  | Any damage of the equipment or burn-out components will be viewed seriously either by putting penalty or by dismissing the total group of students from the lab for the semester/year    |  |
| 10 | Completed lab assignments should be submitted in the form of a Lab Record in which you have to write the algorithm, program code along with comments and output for various inputs given |  |

## 6. Lab Specific Instructions

| SNo | Specific Instructions  | Remarks |
|-----|--|---------|
| 1   | Students are expected to study the circuit, theory and procedures, expected output before doing the experiment.  |         |
| 2   | Multi-meter adjustments:-<br>a. Set the right mode before taking the readings.<br>b. For current reading, connect the multimeter in mA (or A) mode to the circuit before switching on the supply. Do not remove the current meter when the supply is on. Check for ac and dc modes as required.<br>c. For voltage reading ensure that proper ac or dc setting.<br>d. Use the proper leads for the measurement. Wrong cables damage the instrument. |         |
| 3   | Don't pull out the connections with the power supply on.   |         |
| 4   | Wear your College ID card Do not operate the IC trainer kits without permission  |         |
| 5   | Avoid loose connection and short circuits  |         |
| 6   | Do not panic if you do not get the output  |         |
| 7   | After completion of the experiment switch off the power and return the components  |         |

## B. OBE PARAMETERS

### 1. Lab / Course Outcomes

| # | Lab Code #  | COs   | Teach Hours | Concept               | Instr Method     | Assessme nt Method | Blooms ' Level |
|---|-------------|---|-------------|-----------------------|------------------|--------------------|----------------|
| 1 | 18ELEL2 7.1 | Analysis of DC circuits by using KVL & KCL  | 3           | DC circuits           | Conduc tion demo | Viva & test        | L3             |
| 2 | 18ELEL2 7.2 | Analysis the incandescent lamp, FL, LED lamp & measure the current,power & power factor     | 3           | measureme nts         | Conduc tion demo | Viva & test        | L2             |
| 3 | 18ELEL2 7.1 | Analysis the chokecoil & measurement of resistance & inductance by using 3 voltmeter method | 3           | Chock coil            | Conduc tion demo | Viva & test        | L2             |
| 4 | 18ELEL2 7.3 | Determine phase & line voltage by using star delta connection                               | 3           | Star delta connection | Conduc tion demo | Viva & test        | L3             |
| 5 | 18ELEL2 7.3 | Determine the power in electric circuit by using 3phase load.                               | 3           | 3phase power          | Conduc tion demo | Viva & test        | L2             |
| 6 | 18ELEL2 7.4 | Understand lamp,switches & lamp controller by two way & three way switches                  | 3           | Lamp control          | Conduc tion demo | Viva & test        | L2             |
| 7 | 18ELEL2     | Determine earth resistance by using   | 3           | Earth                 | Conduc           | Viva & test        | L2             |

EE

Prepared by Avinash S

Checked by

Approved



|                          |                  |                  |
|--------------------------|------------------|------------------|
| INST                     | Teaching Process | Rev No.: 1.0     |
| Doc Code: INST.Ph5b1.F03 |                  | Date: 11-07-2018 |
| Title: Course Lab Manual |                  | Page: 6 / 22     |

Copyright ©2017, CAAS. All rights reserved.

|     |                |  |            |                  |                  |                |
|-----|----------------|--|------------|------------------|------------------|----------------|
| 7.4 | Erath Tester   |  | resistance | tion demo        |                  |                |
| 8   | 18ELEL2<br>7.1 | Study the circuit & effect of OC & SC circuits | 3          | OC & SC circuits | Conduc tion demo | Viva & test L2 |
| -   | <b>Total</b>   |  | -          | -                | -                | -              |

Note: Identify a max of 2 Concepts per unit. Write 1 CO per concept.

## 2. Lab Applications

| SNo | Application Area  | CO  | Level |
|-----|---|-----|-------|
| 1   | The practical application of KCL and KVL is to determine the amount of current flowing through individual electronic component in a circuit and voltage drop in each one. Using that law we can manipulate voltage and current to the component by controlling resistance to it.<br><a href="https://www.youtube.com/watch?v=cUu81SbD6o">https://www.youtube.com/watch?v=cUu81SbD6o</a> | CO1 | L3    |
| 2   | In Lightnings   | CO2 | L2    |
| 3   | Used in fluorescent lamps   | CO1 | L2    |
| 4   | Used in residential, appartments and in industries.   | CO3 | L3    |
| 5   | Used in connection of various loads.  | CO3 | L2    |
| 6   | Used to measure 3phase power.   | CO4 | L2    |
| 7   | To measure earth resistance.  | CO4 | L2    |
| 8   | Used to calculate transformer losses.   | CO1 | L2    |

Note: Write 1 or 2 applications per CO.

## 4. Articulation Matrix

### (CO – PO MAPPING)

| CO Number      | Course Outcomes<br>At the end of the course student should be able to ..  | Program Outcomes |     |     |     |     |     |     |     |     |      |      |      |      |      |      | Level |
|----------------|---|------------------|-----|-----|-----|-----|-----|-----|-----|-----|------|------|------|------|------|------|-------|
|                |   | PO1              | PO2 | PO3 | PO4 | PO5 | PO6 | PO7 | PO8 | PO9 | PO10 | PO11 | PO12 | PSO1 | PSO2 | PSO3 |       |
| CO1            | Identify the common electrical components and measuring instruments used for conducting experiments in the electrical Laboratory.   | 3                | 2   | -   | -   | -   | -   | -   | -   | -   | -    | -    | -    | 2    | -    | -    | L3    |
| CO2            | Compare power factors of lamp..   | 3                | 1   | -   | -   | -   | -   | -   | -   | -   | -    | -    | -    | 2    | -    | -    | L3    |
| CO3            | Determine the Electrical quantities of an electrical circuit and power consumed in a 3 phase load.  | 3                | 2   | -   | -   | -   | -   | -   | -   | -   | -    | -    | -    | 2    | -    | -    | L3    |
| CO4            | Determine earth resistance and understand two way and three way control of lamps  | 2                | -   | -   | -   | -   | -   | 2   | -   | -   | -    | -    | -    | 1    | -    | -    | L2    |
| <b>ELE23PC</b> | <b>Average attainment (1, 2, or 3)</b>  |                  |     |     |     |     |     |     |     |     |      |      |      |      |      |      | -     |
| PO, PSO        | 1.Engineering Knowledge; 2.Problem Analysis; 3.Design / Development of Solutions; 4.Conduct Investigations of Complex Problems; 5.Modern Tool Usage; 6.The Engineer and Society; 7.Environment and Sustainability; 8.Ethics; 9.Individual and Teamwork; 10.Communication; 11.Project Management and Finance; 12.Life-long Learning; S1.Software Engineering; S2.Data Base Management; S3.Web Design |                  |     |     |     |     |     |     |     |     |      |      |      |      |      |      |       |

EE

Prepared by Avinash S

Checked by

Approved



|                          |                  |                  |
|--------------------------|------------------|------------------|
| INST                     | Teaching Process | Rev No.: 1.0     |
| Doc Code: INST.Ph5b1.F03 |                  | Date: 11-07-2018 |
| Title: Course Lab Manual |                  | Page: 7 / 22     |

Copyright ©2017. CAAS. All rights reserved.

|                                     |  |
|-------------------------------------|--|
| C<br>t<br>u<br>r<br>e<br><br>1<br>7 | <p>PSO 1: Apply fundamental knowledge to identify, formulate, design and investigate various problems of electrical and electronic circuits, power electronics, and power systems.</p> <p>PSO 2: Use latest Electrical and Electronics related softwares for simple design, drafting, manufacturing, maintenance and documentation of Electrical and Electronics components .</p> <p>PSO 3: Manage the Electrical process by selection and scheduling right type of machinery, Conductors, Electrical equipment, power quality control techniques, operational parameters and softwares for a particular power transmission process to achieve reliability and economical operation.</p> |
|-------------------------------------|--|

Note: Mention the mapping strength as 1, 2, or 3

## C. COURSE ASSESSMENT

### Continuous Internal Assessment (CIA)

| Evaluation                            | Weightage in Marks | CO                  | Levels    |
|---------------------------------------|--------------------|---------------------|-----------|
| CIA Exam – 1                          | 40                 | CO1, CO2, CO3,      | L2, L3    |
| CIA Exam – 2                          | 40                 | CO1, CO3, CO4,      | L2, L3 .. |
| CIA Exam – 3                          | 40                 | CO1, CO2, CO3, CO4, | L2, L3 .. |
| Other Activities – define – Slip test |                    | CO1 to Co49         | L2, L3..  |
| <b>Final CIA Marks</b>                | <b>40</b>          | <b>-</b>            | <b>-</b>  |

| SNo | Description                                  | Marks                  |
|-----|--|------------------------|
| 1   | Observation and Weekly Laboratory Activities | 15 Marks               |
| 2   | Record Writing                               | 15 Marks for each Expt |
| 3   | Internal Exam Assessment                     | 10 Marks               |
| 4   | Internal Assessment                          | 40 Marks               |
| 5   | SEE  | 60 Marks               |
| -   | <b>Total</b>                                 | <b>100 Marks</b>       |

## D. EXPERIMENTS

### Experiment 01 : VERIFICATION OF KCL AND KVL FOR DC CIRCUITS.

| - | Experiment No.:               | 1   | Marks                        | Date Planned                              | Date Conducted |
|---|-------------------------------|---|------------------------------|---|----------------|
| 1 | Title                         | VERIFICATION OF KCL AND KVL FOR DC CIRCUITS |                              |   |                |
| 2 | Course Outcomes               | Able to verify Electrical Laws.             |                              |   |                |
| 3 | Aim                           | VERIFICATION OF KCL AND KVL FOR DC CIRCUITS |                              |   |                |
| 4 | Material / Equipment Required | Lab Manual                                  |                              |   |                |
|   |                               | SL.No.                                      | Apparatus                    | Range                                     | Quantity       |
|   |                               | 1   | RPS (regulated power supply) | (0-30V)                                   | 2              |
|   |                               | 2   | Resistance                   | 330 $\Omega$ , 220 $\Omega$ , 1k $\Omega$ | 6              |
|   |                               | 3   | Ammeter                      | (0-30mA)MC                                | 3              |
|   |                               | 4   | Voltmeter                    | (0-30V)MC                                 | 3              |

EE

Prepared by Avinash S

Checked by

Approved



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 8 / 22     |

Copyright ©2017, CAAS. All rights reserved.

|           |  | 5   | Bread Board & Wires | --              | Required          |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
|-----------|--|---|---------------------|-----------------|-------------------|-----------|---------|--|--|-----------------|-------------------|----------------|----------------|----------------|-------|----|----|----|----|----|---|--|--|--|--|--|----|--|--|--|--|--|----|--|--|--|--|--|
| 5         | Theory, Formula, Principle, Concept                              | <p>The practical application of KCL and KVL is to determine the amount of current flowing through individual component in a circuit and voltage drop across each component. These laws are applicable for both DC and AC circuits.</p> <p>Kirchhoff's Current Law: It states that "In any electrical network the algebraic sum of currents meeting at a node is zero."</p> $\Sigma I = 0$ <p>Kirchhoff's Voltage Law: It states that "The algebraic sum of product of current and resistance in each of the conductors in any closed path in a network plus the algebraic sum of the e.m.f.s. in the closed path is zero."</p> $\Sigma IR + \Sigma E.M.F = 0$ |                     |                 |                   |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
| 6         | Procedure, Program, Activity, Algorithm, Pseudo Code             | <p>Procedure for KCL:</p> <ol style="list-style-type: none"> <li>1. Connections are made as per the circuit diagram.</li> <li>2. Set a particular value in RPS.</li> <li>3. Note down the corresponding ammeter reading.</li> <li>4. Repeat the same for different voltages.</li> </ol> <p>Procedure for KVL:</p> <ol style="list-style-type: none"> <li>1. Connections are made as per the circuit diagram.</li> <li>2. Set a particular value in RPS.</li> <li>3. Note all the voltage reading.</li> </ol> <p>Repeat the same for different voltages.</p>   |                     |                 |                   |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
| 7         | Block, Circuit, Model Diagram, Reaction Equation, Expected Graph |   |                     |                 |                   |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
| 8         | Observation Table, Look-up Table, Output                         | <p>Tabular Column for KCL</p> <table border="1"> <thead> <tr> <th rowspan="2">Voltage E</th> <th colspan="3">Current</th> <th rowspan="2">Practical Value</th> <th rowspan="2">Theoretical Value</th> </tr> <tr> <th>I<sub>1</sub></th> <th>I<sub>2</sub></th> <th>I<sub>3</sub></th> </tr> </thead> <tbody> <tr> <td>Volts</td> <td>mA</td> <td>mA</td> <td>mA</td> <td>mA</td> <td>mA</td> </tr> <tr> <td>5</td> <td></td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td>10</td> <td></td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td>15</td> <td></td> <td></td> <td></td> <td></td> <td></td> </tr> </tbody> </table>                |                     |                 |                   | Voltage E | Current |  |  | Practical Value | Theoretical Value | I <sub>1</sub> | I <sub>2</sub> | I <sub>3</sub> | Volts | mA | mA | mA | mA | mA | 5 |  |  |  |  |  | 10 |  |  |  |  |  | 15 |  |  |  |  |  |
| Voltage E | Current  |   |                     | Practical Value | Theoretical Value |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
|           | I <sub>1</sub>   | I <sub>2</sub>  | I <sub>3</sub>      |                 |                   |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
| Volts     | mA   | mA  | mA                  | mA              | mA                |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
| 5         |  |   |                     |                 |                   |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
| 10        |  |   |                     |                 |                   |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |
| 15        |  |   |                     |                 |                   |           |         |  |  |                 |                   |                |                |                |       |    |    |    |    |    |   |  |  |  |  |  |    |  |  |  |  |  |    |  |  |  |  |  |





|                          |                  |                  |
|--------------------------|------------------|------------------|
| INST                     | Teaching Process | Rev No.: 1.0     |
| Doc Code: INST.Ph5b1.F03 |                  | Date: 11-07-2018 |
| Title: Course Lab Manual |                  | Page: 9 / 22     |

Copyright ©2017, CAAS. All rights reserved.

|   |                               |   |                |                |   |                   |
|---|-------------------------------|---|----------------|----------------|---|-------------------|
| <b>C<br/>t<br/>u<br/>r<br/>e</b><br><br><b>1<br/>7</b><br><br>.<br>.<br>. | 20                            |   |                |                |   |                   |
|   | 25                            |   |                |                |   |                   |
|   | <b>Tabular column for KVL</b> |   |                |                |   |                   |
|   | Input Voltage                 |   | Voltage Drops  |                | Practical Value   | Theoretical Value |
|   | E <sub>1</sub>                | E <sub>2</sub>  | V <sub>1</sub> | V <sub>2</sub> | E <sub>1</sub> - E <sub>2</sub> = V <sub>1</sub> + V <sub>2</sub> |                   |
|   | Volts                         | Volts   | Volts          | Volts          | Volts   | Volts             |
|   | 3                             | 2   |                |                |   |                   |
|   | 5                             | 4   |                |                |   |                   |
|   | 7                             | 6   |                |                |   |                   |
|   | 10                            | 8   |                |                |   |                   |
| 15  | 10                            |   |                |                |   |                   |
| 9   | Sample Calculations           | <p>1. <math>I_1 = I_2 + I_3</math></p> <p>2. <math>E_1 - E_2 = V_1 + V_2</math></p>                         |                |                |   |                   |
| 10  | Graphs, Outputs               |   |                |                |   |                   |
| 11  | Results & Analysis            | Thus Kirchoff's voltage law and Kirchoff's current law are verified theoretically as well as practically.   |                |                |   |                   |
| 12  | Application Areas             | They can be used to analyze any electrical circuit. Computation of current and voltage of complex circuits. |                |                |   |                   |
| 13  | Remarks                       |   |                |                |   |                   |
| 14  | Faculty Signature with Date   |   |                |                |   |                   |

**Experiment 02 : MEASUREMENT OF CURRENT, POWER AND POWER FACTOR OF INCANDESCENT LAMP, FLUORESCENT LAMP AND LED LAMP**

| - | Experiment No.:             | 2   | Marks  | Date Planned  | Date Conducted  |  |
|---|-----------------------------|---|--|---------------|-----------------|--|
| 1 | Title                       | <b>MEASUREMENT OF CURRENT, POWER AND POWER FACTOR OF INCANDESCENT LAMP, FLUORESCENT LAMP AND LED LAMP</b> |  |               |                 |  |
| 2 | Course Outcomes             | Able to find less power consumption in various loads  |  |               |                 |  |
| 3 | Aim                         | Measurement of current, power and power factor of incandescent lamp, fluorescent lamp and LED lamp.       |  |               |                 |  |
| 4 | Material Equipment Required | /Lab Manual   |  |               |                 |  |
|   |                             | <b>Sl.No.</b>   | <b>Apparatus</b>                                 | <b>Range</b>  | <b>Quantity</b> |  |
|   |                             | 1   | Ammeter  | (0-5A)        | 1               |  |
|   |                             | 2   | Voltmeter  | (0-300V)      | 1               |  |
|   |                             | 3   | Wattmeter  | 250V, 5A, UPF | 1               |  |
|   |                             | 4   | Bread Board & Wires                              | --            | Required        |  |
|   |                             | 5   | Incandescent lamp, fluorescent lamp and LED lamp |               | 1 each          |  |



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 10 / 22    |

Copyright ©2017, cAAS. All rights reserved.

|   |                                     |   |
|---|-------------------------------------|---|
| 5 | Theory, Formula, Principle, Concept | <p>In electrical engineering, the <b>power factor</b> of an AC electrical power system is defined as the ratio of the real power flowing to the load to the apparent power in the circuit. Real power is the capacity of the circuit for performing work in a particular time. Apparent power is the product of the current and voltage of the circuit.</p> <p>In an electric power system, a load with a low power factor draws more current than a load with a high power factor for the same amount of useful power transferred.</p> <p><b>Incandescent light bulb:</b> is an electric light with a wire filament heated to such a high temperature that it glows with visible light (incandescence). The filament is protected from oxidation with a glass or fused quartz bulb that is filled with inert gas or a vacuum. In a halogen lamp, filament evaporation is slowed by a chemical process that redeposit's metal vapor onto the filament, thereby extending its life.</p> <p><b>Fluorescent lamp:</b> is a low-pressure mercury-vapor gas-discharge lamp that uses fluorescence to produce visible light. An electric current in the gas excites mercury vapor, which produces short-wave ultraviolet light that then causes a phosphor coating on the inside of the lamp to glow. A fluorescent lamp converts electrical energy into useful light much more efficiently than incandescent lamps. The typical luminous efficacy of fluorescent lighting systems is 50–100 lumens per watt, several times the efficacy of incandescent bulbs with comparable light output.</p> <p>Operation of Fluorescent lamp: When the supply is switched ON, heat is produced due to glow discharge between electrodes of starter is sufficient to bend bimetallic strip until it makes contact with fixed electrode. Thus circuit, between two electrode F1 &amp; F2 is completed &amp; relatively large current circulated through them. The electrodes are then heated to incandescence by this circulating current&amp; gas in their immediate vicinity is ionized. After a second or two, due to absence of glow discharge a bimetallic strip cools sufficiently.</p> <p><b>Choke:</b></p> <ol style="list-style-type: none"> <li>1. It provides a necessary high voltage to start discharge in the tube.</li> <li>2. Since the voltage required across the tube during normal operation is small, the excess voltage appears as drop across the choke.</li> <li>3. It acts as a stabilizer.</li> </ol> <p><b>Starter:</b></p> <p>The Starter is a switch that is normally closed, that opens a few seconds after power is applied. When the Starter opens, current flows through the tube and it lights up by ionizing the gas.</p> <p><b>LED lamp:</b> is an electric light for use in light fixtures that produces light using light-emitting diode (LED). LED lamps have a lifespan and electrical</p> |
|---|-------------------------------------|---|



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 11 / 22    |

Copyright ©2017, CAAS. All rights reserved.

|                   |  | efficiency which are several times greater than incandescent lamps, and are significantly more efficient than most fluorescent lamps.   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
|-------------------|--|---|-----------------------------------|-------------------------------------|------------------------------------|-----------------------------------|--------------|-------------------|--|--|--|--|------------------|--|--|--|--|----------|--|--|--|--|
| 6                 | Procedure, Program, Activity, Algorithm, Pseudo Code<br>1<br>7   | <ol style="list-style-type: none"> <li>1. Make the connections as shown in the circuit diagram.</li> <li>2. Connect an incandescent lamp &amp; apply 230 V supply.</li> <li>3. Take the readings of ammeter, voltmeter and wattmeter.</li> <li>4. Ammeter reads the current consumed by lamp.</li> <li>5. Wattmeter reads the power consumed by lamp.</li> <li>6. Calculate power factor of lamp using the formula.</li> <li>7. Repeat the same procedure for fluorescent lamp and LED lamp.</li> </ol>                 |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 7                 | Block, Circuit, Model Diagram, Reaction Equation, Expected Graph |   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 8                 | Observation Table, Look-up Table, Output                         | <p><b>TABULATION:</b></p> <table border="1"> <thead> <tr> <th>Types of loads</th> <th>Voltage Applied a/c Lamp<br/>V volts</th> <th>Current through the lamp<br/>I Amps</th> <th>Power consumed by Lamp<br/>W watts</th> <th>Power factor</th> </tr> </thead> <tbody> <tr> <td>Incandescent lamp</td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td>Fluorescent lamp</td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td>LED lamp</td> <td></td> <td></td> <td></td> <td></td> </tr> </tbody> </table> | Types of loads                    | Voltage Applied a/c Lamp<br>V volts | Current through the lamp<br>I Amps | Power consumed by Lamp<br>W watts | Power factor | Incandescent lamp |  |  |  |  | Fluorescent lamp |  |  |  |  | LED lamp |  |  |  |  |
| Types of loads    | Voltage Applied a/c Lamp<br>V volts                              | Current through the lamp<br>I Amps  | Power consumed by Lamp<br>W watts | Power factor                        |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| Incandescent lamp |  |   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| Fluorescent lamp  |  |   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| LED lamp          |  |   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 9                 | Sample Calculations  | $\text{Power factor} = \frac{\text{Wattmeter Reading}}{\text{Voltmeter Reading} \times \text{Ammeter Reading}}$   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 10                | Graphs, Outputs  |   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 11                | Results & Analysis   | The electrical quantities such as current, power and power factor of incandescent, fluorescent and LED lamps has been calculated. It is observed that LED lamp has a good power factor and draws less current for the same amount of useful power transferred compare to the other lamps.   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 12                | Application Areas  | In Lightnings   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 13                | Remarks  |   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |
| 14                | Faculty Signature with Date                                      |   |                                   |                                     |                                    |                                   |              |                   |  |  |  |  |                  |  |  |  |  |          |  |  |  |  |



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 12 / 22    |

Copyright ©2017, CAAS. All rights reserved.


## Experiment 03 : MEASUREMENT OF RESISTANCE AND INDUCTANCE OF A CHOKE COIL USING 3-VOLTMETER METHOD

| -    | Experiment No.:                                      | 1  | Marks    | Date Planned | Date Conducted |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
|------|--|--|----------|--------------|----------------|------|-----------|-------|----------|---|------------|--------------|------|---|-----------|--------|-------|---|---------|----------|------|---|--------------------------|----------------|------|---|----------|---------|-----|---|
| 1    | Title  | MEASUREMENT OF RESISTANCE AND INDUCTANCE OF A CHOKE COIL USING 3-VOLTMETER METHOD  |          |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 2    | Course Outcomes                                      | Able to find the passive elements of choke coil..  |          |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 3    | Aim  | To measure parameters of a choke coil in a single phase A.C. circuit by using three voltmeter method.  |          |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 4    | Material Equipment Required                          | <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th>S.No</th> <th>Apparatus</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Choke coil</td> <td>230 V, 0.39A</td> <td>1 No</td> </tr> <tr> <td>2</td> <td>Voltmeter</td> <td>0-300V</td> <td>3 Nos</td> </tr> <tr> <td>3</td> <td>Ammeter</td> <td>0-2000mA</td> <td>1 No</td> </tr> <tr> <td>4</td> <td>(Variac) Autotransformer</td> <td>230V/0-270V,2A</td> <td>1 No</td> </tr> <tr> <td>5</td> <td>Rheostat</td> <td>100 /1A</td> <td>1No</td> </tr> </tbody> </table>  |          |              |                | S.No | Apparatus | Range | Quantity | 1 | Choke coil | 230 V, 0.39A | 1 No | 2 | Voltmeter | 0-300V | 3 Nos | 3 | Ammeter | 0-2000mA | 1 No | 4 | (Variac) Autotransformer | 230V/0-270V,2A | 1 No | 5 | Rheostat | 100 /1A | 1No | / |
| S.No | Apparatus  | Range  | Quantity |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 1    | Choke coil   | 230 V, 0.39A   | 1 No     |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 2    | Voltmeter  | 0-300V   | 3 Nos    |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 3    | Ammeter  | 0-2000mA   | 1 No     |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 4    | (Variac) Autotransformer                             | 230V/0-270V,2A   | 1 No     |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 5    | Rheostat   | 100 /1A  | 1No      |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 5    | Theory, Formula, Principle, Concept                  | <p>In electronics, a <b>choke</b> is an inductor used to block higher-frequency alternating current (AC) in a circuit. A choke coil is represented by a pure inductance (L) in series with equivalent resistance (r). The choke coil parameters can be measured using 2 methods: 3-voltmeter method &amp; 3-Ammeter method. In addition to this these methods used to measure the quality factor and power absorbed by the given choke coil. The lower the value of resistance (r), better the quality of the coil. The Quality factor or the Q factor of an inductor at the operating frequency <math>\omega</math> is defined as the ratio of reactance of the coil to its resistance.</p> <p><b>Power consumed by load = <math>P = V_L I_L \cos \theta</math></b></p> <p><b>Power factor,</b></p> $\cos \theta = \frac{V_S^2 - V_R^2 - V_L^2}{2 V_R V_L}$ <p><b>Resistance, <math>R = \frac{V_L \cos \theta}{I}</math> ohms</b></p> <p><b>Inductive reactance, <math>X_L = \frac{V_L \sin \theta}{I}</math></b></p> |          |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 6    | Procedure, Program, Activity, Algorithm, Pseudo Code | <ol style="list-style-type: none"> <li>1. Make the connections as per the circuit diagram.</li> <li>2. Initially keep the autotransformer in minimum position.</li> <li>3. Vary the applied voltage by varying the auto-transformer until rated current flows through the choke coil.</li> <li>4. Note down the readings of all the meters.</li> </ol>   |          |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |
| 7    | Block, Circuit, Model Diagram,                       |  |          |              |                |      |           |       |          |   |            |              |      |   |           |        |       |   |         |          |      |   |                          |                |      |   |          |         |     |   |



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 13 / 22    |

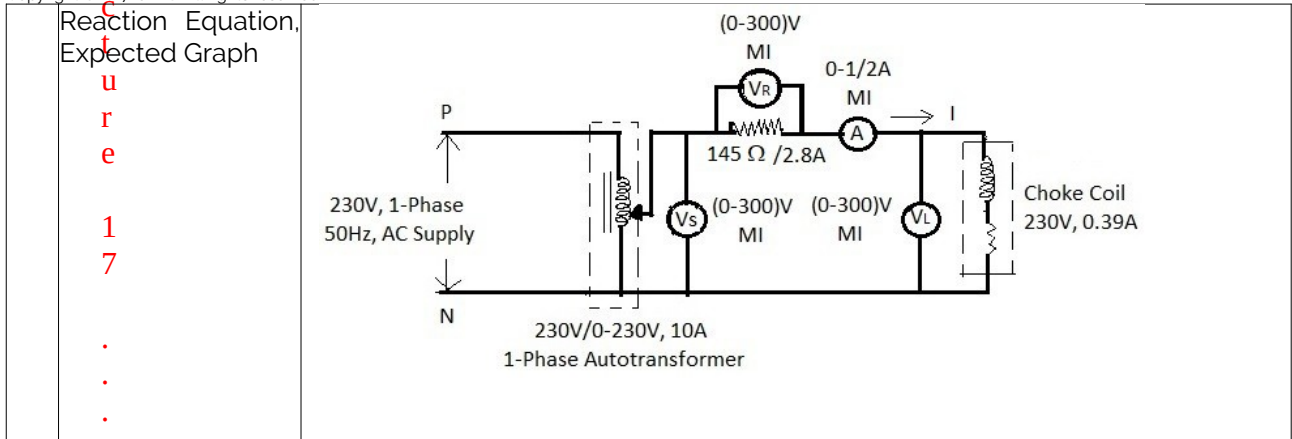Copyright ©2017, CAAS. All rights reserved.



8 Observation Table, Look-up Table, Output

| Sl.No | V <sub>s</sub> (V) | V <sub>R</sub> (V) | V <sub>L</sub> (V) | I (A) |
|-------|--------------------|--------------------|--------------------|-------|
| 1     |                    |                    |                    |       |
| 2     |                    |                    |                    |       |


9 Sample Calculations

$$\text{Power factor, } \cos\theta = \frac{V_s^2 - V_R^2 - V_L^2}{2V_R V_L}$$

$$\text{Resistance of the coil, } R = \frac{V_L \cos\theta}{I} \quad \Omega$$

$$\text{Inductive reactance, } X_L = \frac{V_L \sin\theta}{I} \quad \Omega$$

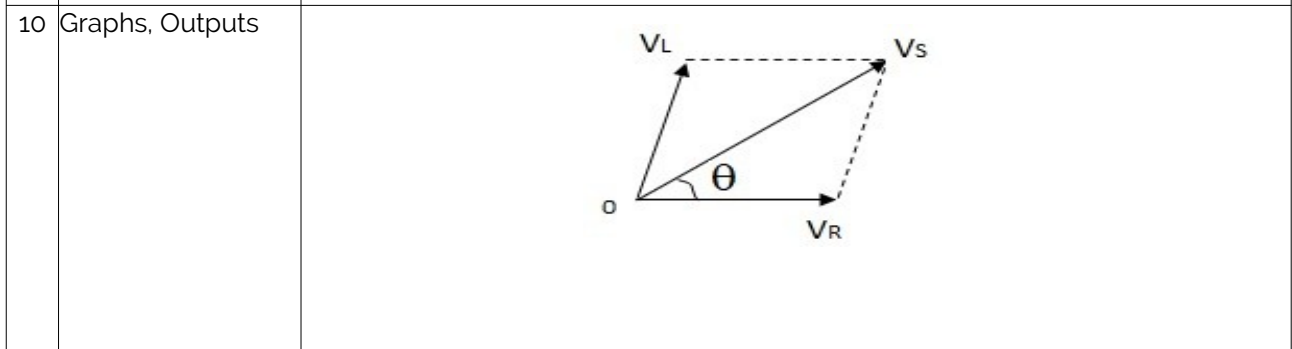Inductance,  $L = X_L / 2\pi f$ , Where f is the frequency of supply in Hertz = 50Hz



|                                |  |
|--------------------------------|--|
| 11 Results & Analysis          | The value of resistance and Inductance of choke coil is determined and tabulated |
| 12 Application Areas           | It is used mostly in wall mounted tube lights                                    |
| 13 Remarks                     |  |
| 14 Faculty Signature with Date |  |



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 14 / 22    |

Copyright ©2017, CAAS. All rights reserved.

## Experiment 04 : DETERMINATION OF PHASE AND LINE QUANTITIES IN THREE PHASE STAR AND DELTA CONNECTION

| -     | Experiment No.:  | 1   | Marks    | Date Planned | Date Conducted |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
|-------|--|---|----------|--------------|----------------|--|-------|-------------|-------|----------|---|-----------|-----------|------|---|---------|---------|-------|---|----------------------|-------------|------|---|-----------------|--|-------|---|------------------|----|-----|
| 1     | Title  | DETERMINATION OF PHASE AND LINE QUANTITIES IN THREE PHASE STAR AND DELTA CONNECTION   |          |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 2     | Course Outcomes  |   |          |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 3     | Aim  | To determine the phase and line quantities in three phase star and delta Connection.  |          |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 4     | Material Equipment Required                                      | Lab Manual<br><br><table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>Sl.no</th> <th>Particulars</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Voltmeter</td> <td>MI 0-600V</td> <td>2Nos</td> </tr> <tr> <td>2</td> <td>Ammeter</td> <td>MI 0-5A</td> <td>2 Nos</td> </tr> <tr> <td>3</td> <td>3-φ Auto-transformer</td> <td>415V/0-440V</td> <td>1 No</td> </tr> <tr> <td>4</td> <td>Rheostat 50E/5A</td> <td></td> <td>3 Nos</td> </tr> <tr> <td>5</td> <td>Connecting wires</td> <td>--</td> <td>Few</td> </tr> </tbody> </table>   |          |              |                |  | Sl.no | Particulars | Range | Quantity | 1 | Voltmeter | MI 0-600V | 2Nos | 2 | Ammeter | MI 0-5A | 2 Nos | 3 | 3-φ Auto-transformer | 415V/0-440V | 1 No | 4 | Rheostat 50E/5A |  | 3 Nos | 5 | Connecting wires | -- | Few |
| Sl.no | Particulars  | Range   | Quantity |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 1     | Voltmeter  | MI 0-600V   | 2Nos     |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 2     | Ammeter  | MI 0-5A   | 2 Nos    |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 3     | 3-φ Auto-transformer   | 415V/0-440V   | 1 No     |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 4     | Rheostat 50E/5A  |   | 3 Nos    |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 5     | Connecting wires   | --  | Few      |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 5     | Theory, Formula, Principle, Concept                              | <p>The <b>star connection</b> is formed by connecting starting or terminating ends of all the three windings together at a common point. This common point is called neutral point. The remaining three ends are brought out for the supply connection. Star connection is preferred for long distance <u>power transmission</u> because it is having the neutral point.</p> <p>In star connection, the line voltage is <math>\sqrt{3}</math> times of phase voltage where as the line current are equal to phase current.</p> <p><math>V_L = \sqrt{3}V_{ph}</math> and <math>I_L = I_{ph}</math></p> <p>Where Line voltage (<math>V_L</math>) is the voltage between two phases in three phase circuit and phase voltage (<math>V_{ph}</math>) is the voltage between one phase to the neutral line.</p> |          |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 6     | Procedure, Program, Activity, Algorithm, Pseudo Code             | <ol style="list-style-type: none"> <li>1. Connections are made as per the circuit diagram.</li> <li>2. Keep the position of the auto transformer at zero.</li> <li>3. Switch ON the supply.</li> <li>4. Set the rheostat to fixed value.</li> <li>5. Gradually vary the auto transformer in steps.</li> <li>6. Then note down the current and voltage readings.</li> <li>7. Repeat the above procedure for delta connection.</li> <li>8. Switch off the supply.</li> </ol>  |          |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |
| 7     | Block, Circuit, Model Diagram, Reaction Equation, Expected Graph |   |          |              |                |  |       |             |       |          |   |           |           |      |   |         |         |       |   |                      |             |      |   |                 |  |       |   |                  |    |     |



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 15 / 22    |

Copyright ©2017, CAAS. All rights reserved.

| <b>C</b><br><b>t</b><br><b>u</b><br><b>r</b><br><b>e</b><br><br><b>1</b><br><b>7</b> |   |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
|--|---|---|-------------------------------|---------------------------------|------------------|-------------------|---|--|--|--|--|---|--|--|--|--|
| 8  | Observation Table, Look-up Table, Output<br><table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>Sl.No</th> <th>V<sub>l</sub> in volt (line)</th> <th>V<sub>ph</sub> in volt (phase)</th> <th>I in amps (line)</th> <th>I in amps (phase)</th> </tr> </thead> <tbody> <tr> <td style="text-align: center;">1</td> <td></td> <td></td> <td></td> <td></td> </tr> <tr> <td style="text-align: center;">2</td> <td></td> <td></td> <td></td> <td></td> </tr> </tbody> </table> | Sl.No   | V <sub>l</sub> in volt (line) | V <sub>ph</sub> in volt (phase) | I in amps (line) | I in amps (phase) | 1 |  |  |  |  | 2 |  |  |  |  |
| Sl.No  | V <sub>l</sub> in volt (line)   | V <sub>ph</sub> in volt (phase)   | I in amps (line)              | I in amps (phase)               |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 1  |   |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 2  |   |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 9  | Sample Calculations   |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 10   | Graphs, Outputs   |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 11   | Results & Analysis<br>In star connected load:<br>Line voltages are $\sqrt{3}$ times of phase voltage.<br>Line currents are equal to phase currents.<br>In delta connection load:<br>Line currents are $\sqrt{3}$ times of phase currents<br>Line voltages are equal to phase voltages.  |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 12   | Application Areas   | Used to connect various loads. Used as starter for 3 phase Induction Motor. |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 13   | Remarks   |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |
| 14   | Faculty Signature with Date   |   |                               |                                 |                  |                   |   |  |  |  |  |   |  |  |  |  |

### Experiment 05 : MEASUREMENT OF THREE PHASE POWER USING TWO WATTMETER METHOD

| - | Experiment No.:             | 1   | Marks | Date Planned | Date Conducted |
|---|-----------------------------|---|-------|--------------|----------------|
| 1 | Title                       | MEASUREMENT OF THREE PHASE POWER USING TWO WATTMETER METHOD   |       |              |                |
| 2 | Course Outcomes             | Able to measure 3 phase power.  |       |              |                |
| 3 | Aim                         | Measurement of three phase power by using two wattmeter method during balanced and Unbalanced load condition. |       |              |                |
| 4 | Material Equipment Required | / Lab Manual<br>3 phase Autotransformer<br>A.C Wattmeter  |       |              |                |



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 16 / 22    |

Copyright ©2017. CAAS. All rights reserved.

|       | <b>C<br/>t<br/>u<br/>r</b>  | A.C Voltmeter<br>A.C ammeter<br>Connecting wires   |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
|-------|---|--|--------------------|--------------------|---------------------|--------------------|--------------------|---------------------|--|--|--|--|--|--|
| 5     | <b>1<br/>7</b>  | Theory, Formula, Principle, Concept<br>Wattmeter Constant = $k = (\text{Set current} \times \text{Set Voltage}) / \text{Full Scale Deflection}$  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 6     | Procedure, Program, Activity, Algorithm, Pseudo Code              | <ol style="list-style-type: none"> <li>1. Make the connections as per the circuit diagram</li> <li>2. Keep the three phase variac (autotransformer) at its zero position</li> <li>3. Switch on the main supply and gradually increase the input voltage so that all the meters give readable deflection.</li> <li>4. Note down the readings of all the meters.</li> </ol>                                |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 7     | Block, Model, Circuit, Diagram, Reaction Equation, Expected Graph |  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 8     | Observation Table, Look-up Table, Output                          | <p style="text-align: center;"><b>TABULATION:</b></p> <table border="1" style="margin-left: auto; margin-right: auto;"> <thead> <tr> <th>Sl.No</th> <th>V in Volts</th> <th>I in Amps</th> <th>W1 x k<br/>in Watts</th> <th>W2 x k<br/>in Watts</th> <th>P=W1+W2<br/>in watts</th> </tr> </thead> <tbody> <tr> <td> </td> <td> </td> <td> </td> <td> </td> <td> </td> <td> </td> </tr> </tbody> </table> | Sl.No              | V in Volts         | I in Amps           | W1 x k<br>in Watts | W2 x k<br>in Watts | P=W1+W2<br>in watts |  |  |  |  |  |  |
| Sl.No | V in Volts  | I in Amps  | W1 x k<br>in Watts | W2 x k<br>in Watts | P=W1+W2<br>in watts |                    |                    |                     |  |  |  |  |  |  |
|       |   |  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 9     | Sample Calculations   |  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 10    | Graphs, Outputs   |  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 11    | Results & Analysis  | The three-phase power is measured using two wattmeter method and it is observed that “Two wattmeter” method is sufficient to measure the three phase power.  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 12    | Application Areas   | Used to measure 3 phase power.   |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 13    | Remarks   |  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |
| 14    | Faculty Signature with Date                                       |  |                    |                    |                     |                    |                    |                     |  |  |  |  |  |  |

### Experiment 06 : TWO WAY AND THREE WAY CONTROL OF LAMP

| - | Experiment No.: | 1  | Marks | Date Planned | Date Conducted |
|---|-----------------|--|-------|--------------|----------------|
| 1 | Title           | TWO WAY AND THREE WAY CONTROL OF LAMP                |       |              |                |
| 2 | Course Outcomes | Able to control a lamp from two and three positions. |       |              |                |

EE

Prepared by Avinash S

Checked by

Approved





|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 17 / 22    |

Copyright ©2017, CAAS. All rights reserved.

|   |   |   |
|---|---|---|
| 3 | Aim   | To control one lamp by two 2-way switches and 3-way switches  |
| 4 | Material<br>Equipment<br>Required                             | <p>Lab Manual</p> <p>Kit Kat fuse: 5 Amps.<br/>Single pole switch: 5 Amps<br/>Lamp holders: 5 Amps<br/>Lamps:<br/>Round /Square wooden block:<br/>Square wooden block:<br/>Battens, Nails, Clips, CTS wire, Fuse wire.</p>  |
| 5 | Theory, Formula,<br>Principle, Concept                        | <p>The Electrical appliances and equipment like fan and lighting points can controlled by more than one switch. The most commonly used are: <b>Two Way Control</b> and <b>Three Way Control</b> of electrical appliances.</p> <p>Two way switching connection is used to control electrical appliances at two different places by using 2-way switches. The most common use of 2-way switching connection is staircase wiring where a light point can be controlled from two locations. One switch installed near the first step of the stairs. The other two way switch is installed at the upper part where the stair ends. The light point is provided between first and last stair at an adequate location and height if the lower switch switches ON the light and the other switch at the top can switch it off or Vice versa.</p> <p>The addition of an "intermediate" switch allows a</p> |
| 6 | Procedure,<br>Program, Activity,<br>Algorithm, Pseudo<br>Code | <p><b>For Two Way Control of lamp</b></p> <ol style="list-style-type: none"> <li>1. Verify the circuit as per circuit diagram.</li> <li>2. Switch on the supply.</li> <li>3. Keep switch SW1 and SW2 in L1 position.</li> <li>4. Note down the condition of the lamp.</li> <li>5. Repeat the step 3 for different positions.</li> </ol> <p>Note down the condition of the lamp.</p> <p><b>For Three Way Control of lamp</b></p> <ol style="list-style-type: none"> <li>1. Verify the circuit as per circuit diagram.</li> <li>2. Switch on the supply.</li> <li>3. Keep switches S1, S2 and S3 in as per the truth table.</li> <li>4. Note down the condition of the lamp.</li> <li>5. Repeat the step 3 for different positions.</li> </ol> <p>Note down the condition of the lamp.</p>  |





Copyright ©2017, CAAS. All rights reserved.

7 Block, Circuit, Model Diagram, Reaction Equation, Expected Graph

e

1  
7

⋮  
⋮  
⋮

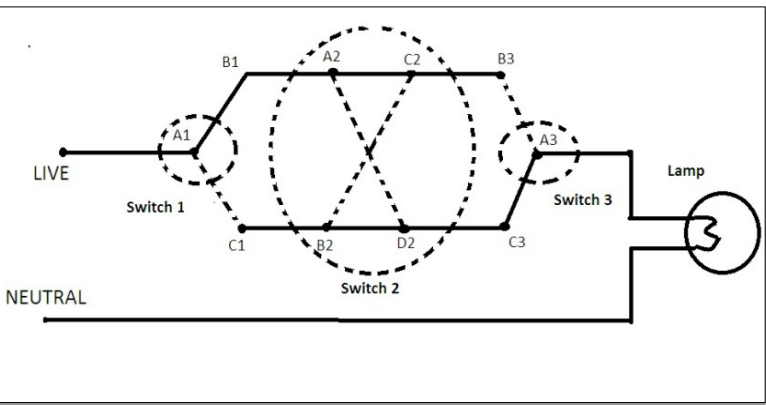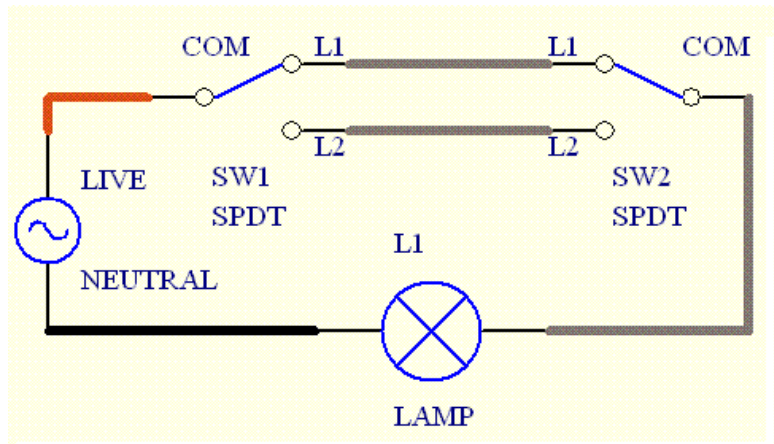

8 Observation Table, Look-up Table, Output

for two way control:

| Switch position |     | Lamp condition |
|-----------------|-----|----------------|
| SW1             | SW2 |                |
| L1              | L1  | ON             |
| L1              | L2  | OFF            |
| L2              | L1  | OFF            |
| L2              | L2  | ON             |

TABULATION FOR 3-WAY CONTROL:

| Sl. No | Switch S1<br>A1<br>connected to | Switch S2          |                    | Switch S3<br>A3<br>connected to | Lamp Condition |
|--------|---------------------------------|--------------------|--------------------|---------------------------------|----------------|
|        |                                 | A2<br>Connected to | B2<br>Connected to |                                 |                |
| 1      | B1                              | C2                 | D2                 | C3                              | OFF            |
| 2      | C1                              | C2                 | D2                 | C3                              | ON             |
| 3      | C1                              | D2                 | C2                 | C3                              | OFF            |
| 4      | C1                              | D2                 | C2                 | B3                              | ON             |

9 Sample



|                          |                  |                  |
|--------------------------|------------------|------------------|
| INST                     | Teaching Process | Rev No.: 1.0     |
| Doc Code: INST.Ph5b1.F03 |                  | Date: 11-07-2018 |
| Title: Course Lab Manual |                  | Page: 19 / 22    |

Copyright ©2017. CAAS. All rights reserved.

|    |                             |  |
|----|-----------------------------|--|
|    | Calculations                |  |
| 10 | Graphs, Outputs             |  |
| 11 | Results & Analysis          | Truth table of two way and three way control of lamps are formed and verified. |
| 12 | Application Areas           | Used in domestic and Industry wiring system.                                   |
| 13 | Remarks                     |  |
| 14 | Faculty Signature with Date |  |

## Experiment 07 : MEASUREMENT OF EARTH RESISTANCE

| -                     | Experiment No.:                                      | 1   | Marks | Date Planned | Date Conducted |  |                       |   |                  |    |                |   |
|-----------------------|--|---|-------|--------------|----------------|--|-----------------------|---|------------------|----|----------------|---|
| 1                     | Title  | MEASUREMENT OF EARTH RESISTANCE   |       |              |                |  |                       |   |                  |    |                |   |
| 2                     | Course Outcomes                                      | Able to find earth resistance.  |       |              |                |  |                       |   |                  |    |                |   |
| 3                     | Aim  | To measure the resistance of the earth.   |       |              |                |  |                       |   |                  |    |                |   |
| 4                     | Material Equipment Required                          | / Lab Manual<br><br><table border="1" style="margin-left: auto; margin-right: auto;"> <tr> <td>Earth tester (Megger)</td> <td>1</td> </tr> <tr> <td>Connecting wires</td> <td>5m</td> </tr> <tr> <td>Measuring Tape</td> <td>1</td> </tr> </table>  |       |              |                |  | Earth tester (Megger) | 1 | Connecting wires | 5m | Measuring Tape | 1 |
| Earth tester (Megger) | 1  |   |       |              |                |  |                       |   |                  |    |                |   |
| Connecting wires      | 5m   |   |       |              |                |  |                       |   |                  |    |                |   |
| Measuring Tape        | 1  |   |       |              |                |  |                       |   |                  |    |                |   |
| 5                     | Theory, Formula, Principle, Concept                  | <p>The resistance offered by the earth electrode to the flow of current into the ground is known as the earth resistance or resistance to earth. The earth resistance mainly implies the resistance between the electrode and the point of zero potential. Ideally, the ground resistance should be of zero ohms but there is no standard ground resistance threshold or value that is being followed. However, a ground resistance value of 5.0 ohm or less is recommended by IEEE.</p> <p>The grounding resistance is determined with this earth tester in three measuring ranges up to 2000 <math>\Omega</math> using three-wire technology. The Earth Tester or Megger is a handheld instrument used to quickly and easily determine earth and ground resistance.</p> |       |              |                |  |                       |   |                  |    |                |   |
| 6                     | Procedure, Program, Activity, Algorithm, Pseudo Code | <ol style="list-style-type: none"> <li>1. Connect C1 and P1 terminals on the test set to the earth electrode as shown in circuit diagram.</li> <li>2. Connect the terminal C2 to an electrode Z kept at 5m away from main electrode X and buried to a depth of 6 – 12 inches.</li> <li>3. Connect the terminal P2 to an electrode Y which is kept midway between X &amp; Z and buried to a depth of 6 – 12 inches.</li> <li>4. Rotate the megger handle and record the resistance measurement.</li> <li>5 .Note down the readings of measured resistance by changing the distance between electrodes.</li> </ol>  |       |              |                |  |                       |   |                  |    |                |   |

EE

Prepared by Avinash S

Checked by

Approved



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 20 / 22    |

Copyright ©2017. CAAS. All rights reserved.

| 7     | Block, Circuit, Model Diagram, Reaction Equation, Expected Graph |   |       |                 |                        |   |  |  |   |  |  |   |  |  |
|-------|--|---|-------|-----------------|------------------------|---|--|--|---|--|--|---|--|--|
| 8     | Observation Table, Look-up Table, Output                         | <table border="1"> <thead> <tr> <th>Sl No</th> <th>Distance in mtr</th> <th>Resistance in <math>\Omega</math></th> </tr> </thead> <tbody> <tr> <td>1</td> <td></td> <td></td> </tr> <tr> <td>2</td> <td></td> <td></td> </tr> <tr> <td>3</td> <td></td> <td></td> </tr> </tbody> </table> | Sl No | Distance in mtr | Resistance in $\Omega$ | 1 |  |  | 2 |  |  | 3 |  |  |
| Sl No | Distance in mtr  | Resistance in $\Omega$  |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 1     |  |   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 2     |  |   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 3     |  |   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 9     | Sample Calculations  |   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 10    | Graphs, Outputs  |   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 11    | Results & Analysis   | The average value of the earth resistance is _____ $\Omega$ .   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 12    | Application Areas  | Used to measure earth resistance.   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 13    | Remarks  |   |       |                 |                        |   |  |  |   |  |  |   |  |  |
| 14    | Faculty Signature with Date                                      |   |       |                 |                        |   |  |  |   |  |  |   |  |  |

### Experiment 08 : STUDY OF EFFECT OF OPEN AND SHORT CIRCUITS IN SIMPLE CIRCUITS

| - | Experiment No.:                                 | 1   | Marks | Date Planned | Date Conducted |  |
|---|---|---|-------|--------------|----------------|--|
| 1 | Title   | STUDY OF EFFECT OF OPEN AND SHORT CIRCUITS IN SIMPLE CIRCUITS   |       |              |                |  |
| 2 | Course Outcomes                                 | Able to know the effect of Open and Short circuit in AC circuits.   |       |              |                |  |
| 3 | Aim   |   |       |              |                |  |
| 4 | Material Equipment Required                     | Lab Manual<br>Voltmeter - 1 no.<br>Ammeter - 1 no<br>30V DC Power Supply - 1 no<br>Connecting wires   |       |              |                |  |
| 5 | Theory, Formula, Principle, Concept             | <p>An open circuit is a circuit where no current flows. The circuit which does not have a return path is an open circuit. Hence there is infinite impedance between two nodes therefore current becomes zero.</p> <p>A short circuit is an electrical circuit that allows a current to travel along a low electrical impedance path. This results in an excessive amount of current flowing into the circuit.</p> |       |              |                |  |
| 6 | Procedure, Program, Activity, Algorithm, Pseudo | 1) Make the connections as per the circuit diagram and make sure that autotransformer is at zero position.  |       |              |                |  |

EE

Prepared by Avinash S

Checked by

Approved



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 21 / 22    |

Copyright ©2017. CAAS. All rights reserved.

|   |   |
|---|---|
| Code<br>t<br>u<br>r<br>e<br><br>1<br>7<br><br>.<br>.<br>. | <p>2) Switch ON the supply. Now apply the rated voltage to the Primary winding by using variac.</p> <p>3) The readings of the Voltmeter, ammeter and wattmeter are noted down in Tabular form.</p> <p>4) Bring back the autotransformer to zero position and switch off the supply.</p> |
|---|---|

|   |  |  |
|---|--|--|
| 7 | Block, Circuit, Model Diagram, Reaction Equation, Expected Graph | <p style="text-align: center;">230V, 50Hz AC supply</p> <p style="text-align: center;">230, 1φ Auto Transformer</p> <p style="text-align: center;">1kVA, 1φ Transformer</p> <p style="text-align: center;">open circuit</p> <p style="text-align: center;">230V, 50Hz AC supply</p> <p style="text-align: center;">230, 1φ Auto Transformer</p> <p style="text-align: center;">1kVA, 1φ Transformer</p> <p style="text-align: center;">short circuit</p> |
|---|--|--|

| 8      | Observation Table, Look-up Table, Output | <table border="1" style="width: 100%;"> <thead> <tr> <th style="width: 20%;">Sl.No.</th> <th style="width: 30%;">V<sub>sc</sub><br/>Volts</th> <th style="width: 30%;">I<sub>sc</sub><br/>Amps</th> </tr> </thead> <tbody> <tr> <td>1</td> <td></td> <td></td> </tr> </tbody> </table> | Sl.No. | V <sub>sc</sub><br>Volts | I <sub>sc</sub><br>Amps | 1 |  |  |
|--------|--|--|--------|--------------------------|-------------------------|---|--|--|
| Sl.No. | V <sub>sc</sub><br>Volts                 | I <sub>sc</sub><br>Amps  |        |                          |                         |   |  |  |
| 1      |  |  |        |                          |                         |   |  |  |
| 9      | Sample Calculations                      |  |        |                          |                         |   |  |  |
| 10     | Graphs, Outputs                          |  |        |                          |                         |   |  |  |
| 11     | Results & Analysis                       | <p>It is observed that After open circuit, the voltage increases across the load but current becomes Zero.</p> <p>After short circuit, the current increase but voltage becomes Zero.</p>  |        |                          |                         |   |  |  |
| 12     | Application Areas                        | Used to obtain transformer losses.   |        |                          |                         |   |  |  |
| 13     | Remarks                                  |  |        |                          |                         |   |  |  |
| 14     | Faculty Signature                        |  |        |                          |                         |   |  |  |



|           |                   |                  |
|-----------|-------------------|------------------|
| INST      | Teaching Process  | Rev No.: 1.0     |
| Doc Code: | INST.Ph5b1.F03    | Date: 11-07-2018 |
| Title:    | Course Lab Manual | Page: 22 / 22    |

Copyright ©2017. cAAS. All rights reserved.

|           |  |
|-----------|--|
| with Date |  |
|-----------|--|

1  
u  
r  
e  
  
1  
7  
  
.  
.  
.