

Ref No:

Sri Krishna Institute of Technology
Bengaluru-560090



COURSE PLAN

Academic Year - 2018-2019

Program:	B E – Electrical & Electronics Engineering
Semester :	4
Course Code:	17EEL48
Course Title:	OP AMP & LIC Lab
Credit / L-T-P:	2 / 0-0-2
Total Contact Hours:	36
Course Plan Author:	Bharati.S.K

Academic Evaluation and Monitoring Cell

#29, Hesaragatta Main Road, Chimney Hills
Chikkabanavara Post Bengaluru – 560090, Karnataka, India
Phone / Fax :080-23721477/28392221/23721315
Web: www,skit.org, e-mail:skitprinci1@gmail.com

INSTRUCTIONS TO TEACHERS

- Classroom / Lab activity shall be started after taking attendance.
- Attendance shall only be signed in the classroom by students.
- Three hours attendance should be given to each Lab.
- Use only Blue or Black Pen to fill the attendance.
- Attendance shall be updated on-line & status discussed in DUGC.
- No attendance should be added to late comers.
- Modification of any attendance, over writings, etc is strictly prohibited.
- Updated register is to be brought to every academic review meeting as per the COE.

Table of Contents

A. LABORATORY INFORMATION	4
1. Laboratory Overview.....	4
2. Laboratory Content.....	4
3. Laboratory Material.....	5
4. Laboratory Prerequisites:.....	5
5. Content for Placement, Profession, HE and GATE.....	5
B. Laboratory Instructions	6
1. General Instructions.....	6
2. Laboratory Specific Instructions.....	6
C. OBE PARAMETERS	6
1. Laboratory Outcomes.....	6
2. Laboratory Applications.....	7
3. Mapping And Justification.....	8
4. Articulation Matrix.....	8
5. Curricular Gap and Experiments.....	9
6. Experiments Beyond Syllabus.....	9
D. COURSE ASSESSMENT	10
1. Laboratory Coverage.....	10
2. Continuous Internal Assessment (CIA).....	10
E. EXPERIMENTS	11
Experiment 01 : Structure of C program.....	11
Experiment 02 : Keywords and identifiers.....	12
Experiment 03 :	13
Experiment 04 :	13
F. Content to Experiment Outcomes	14
1. TLPA Parameters.....	14
2. Concepts and Outcomes:.....	15

Note : Remove "Table of Content" before including in CP Book

Each Laboratory Plan shall be printed and made into a book with cover page

Blooms Level in all sections match with A.2, only if you plan to teach / learn at higher levels

A. LABORATORY INFORMATION

1. Laboratory Overview

<i>Degree:</i>	B.E	<i>Program:</i>	EE
<i>Year / Semester :</i>	2/ 4	<i>Academic Year:</i>	2018-19
<i>Course Title:</i>	OP AMP & LIC Lab	<i>Course Code:</i>	17EEL48
<i>Credit / L-T-P:</i>	2 / 0-0-2	<i>SEE Duration:</i>	180 Minutes
<i>Total Contact Hours:</i>	36Hrs	<i>SEE Marks:</i>	60 Marks
<i>CIA Marks:</i>	40 Marks	<i>Assignment</i>	-
<i>Lab. Plan Author:</i>	Bharati S K	<i>Sign</i>	Dt :
<i>Checked By:</i>		<i>Sign</i>	Dt :

2. Laboratory Content

Expt.	Title of the Experiments	Lab	Concept	Blooms
-------	--------------------------	-----	---------	--------

		Hours		Level
1	Design and verify a precision full wave rectifier. Determine the performance parameters.	3	Rectification	L4
2	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non - inverting configuration for a given gain.	3	Frequency Response	L4
3	Design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency.	3	Sinoidal signal Generation	L4
4	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP).	3	Square/ Rectangular Wave Generation	L4
5	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector.	3	Voltage Comparison	L3
6	Design and verify the operation's of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator.	3	Airthmatic Operation	L4
7	Design and realize an op – amp based first order Butterworth (a) Low pass (b) High pass and (c) Band pass filters for a given cut off frequency frequencies to verify the frequency response characteristic.	3	Active filtration	L4
8	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency.	3	Different Signal Generation	L4
9	Design and realization of R – 2R ladder DAC	3	Digital to Analog Conversion	L4
10	Realization of Two bit Flash ADC.	3	Analog to Digital Conversion	L3
11	Design and verify an IC 555 timer based pulse generator for the specified pulse.	3	Pulse Generation	L4
12	Designing of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series.	3	Voltage Regulation	L4

3. Laboratory Material

Books & other material as recommended by university (A, B) and additional resources used by Laboratory teacher (C).

Expt.	Details	Expt. in book	Availability
A	Text books (Title, Authors, Edition, Publisher, Year.)	-	-
2,6,7,9,10	Op-Amps and Linear Integrated Circuits,Ramakant A Gayakwad, Pearson 4 th Edition 2015	5	In Lib / In Dept
1,3,4,5,8,11,12	Operational Amplifiers and Linear ICs,David A. Bell,Oxford,3 rd Edition 2011	7	In Lib/ In dept
B	Reference books (Title, Authors, Edition, Publisher, Year.)	-	-
12	Linear Integrated Circuits; Analysis,Design and Applications,B. Somanthan Nair, Wiley India,2013	8	In Lib
8.	Linear Integrated Circuits S. Salivahanan, et al McGraw Hill 2 nd Edition,2014.	7	In Lib
3	Operational Amplifiers and Linear Integrated Circuits K. Lal Kishore Pearson 1 st Edition, 2012	4	In lib
C	Concept Videos or Simulation for Understanding	-	-
co1	Rectification https://nptel.ac.in/courses/108101091/46		

co2	Frequency Response of Op Amp https://www.youtube.com/watch?v=wHNo-wQktZI		
co3	RC Phase Shift Oscillator: https://www.youtube.com/watch?v=8iPRR6iCD8A&t=778s https://www.youtube.com/watch?v=8eLolUGSXns		
co4	Schmitt Trigger: https://www.youtube.com/watch?v=V-bAduYlul&list=PLuv3GM6-gsE3npYPJJDnEF3pdiHZT6Kj3&index=50		
co5	Comparator and ZCD: https://www.youtube.com/watch?v=V-bAduYlul&list=PLuv3GM6-gsE3npYPJJDnEF3pdiHZT6Kj3&index=50		
co6	Mathematical Operations: https://www.youtube.com/watch?v=RSWsJjUqD2w&list=PLuv3GM6-gsE3npYPJJDnEF3pdiHZT6Kj3&index=49		
co7	Filter(LPF,HPF and BPF): https://www.youtube.com/watch?v=W70GFpflLk&list=PLuv3GM6-gsE3npYPJJDnEF3pdiHZT6Kj3&index=24 https://www.youtube.com/watch?v=2e0--YSb2lo&list=PLuv3GM6-gsE3npYPJJDnEF3pdiHZT6Kj3&index=25 https://www.youtube.com/watch?v=uj4b2O4XVVE&list=PLuv3GM6-gsE3npYPJJDnEF3pdiHZT6Kj3&index=26		
co8	Signal Generator(square,Triangular and Sin wave): https://www.youtube.com/watch?v=PlsNKqgkDTQ		
co9	R-2R Ladder DAC: https://www.youtube.com/watch?v=wa7plvIT-do&t=1991s		
co10	Flash ADC: https://www.youtube.com/watch?v=wa7plvIT-do&t=1991s		
co11	Multivibrators using 555 Timer: https://www.youtube.com/watch?v=Rd3QSzye72w		
co12	Voltage Regulation https://www.youtube.com/watch?v=5rRkmZs2lil		
D	Software Tools for Design	-	-
CO1- CO12	Multisim		
E	Recent Developments for Research	-	-
co1	Improved accuracy- https://ieeexplore.ieee.org/abstract/document/4303403		
co2	High performance- https://ieeexplore.ieee.org/abstract/document/896237		
co3	Improved linearity- https://ieeexplore.ieee.org/abstract/document/4671125		
co4	Improved timing accuracy - https://patents.google.com/patent/US6055287A/en		
co5	Improved timing accuracy - https://patents.google.com/patent/US6055287A/en		
co6	High		

	performance- https://ieeexplore.ieee.org/abstract/document/896237		
co7	High frequency operation - https://www.tandfonline.com/doi/abs/10.1080/00207219308925897		
co8	Improved linearity- https://ieeexplore.ieee.org/abstract/document/4671125		
co9	High performance- https://ieeexplore.ieee.org/abstract/document/896237		
co10	High performance- https://ieeexplore.ieee.org/abstract/document/896237		
co11	Reduced recovery time - https://digital-library.theiet.org/content/journals/10.1049/iet-cds_20060359		
co12	Low drop out voltage with improved stability - https://patents.google.com/patent/US6373233B2/en		
F	Others (Web, Video, Simulation, Notes etc.)		
	Nptel online video lecture	Www.on linecour ses.nptel .ac.in	Nptel online video lecture

4. Laboratory Prerequisites:

Refer to GL01. If prerequisites are not taught earlier, GAP in curriculum needs to be addressed. Include in Remarks and implement in B.5.

Students must have learnt the following Courses / Topics with described Content . . .

Expt.	Lab. Code	Lab. Name	Topic / Description	Sem	Remarks	Blooms Level
1	17ELN24	Basic Electronics	Semiconductor devices and BJT/ Fundamentals and characteristics of diode , transistor characteristics	2		L2 Understa nd
2	17EE34	Analog Electronics Circuits	Working and design of Clipping and Clamping circuits	3		L4 Analyze
3	17EE34	Analog Electronics Circuits	Feedback amplifier (Feedback concept)	3		L2 Understa nd
4	17EE34	Analog Electronics Circuits	Working and design of oscillators.	3		L4 Analyze

5. Content for Placement, Profession, HE and GATE

The content is not included in this course, but required to meet industry & profession requirements and help students for Placement, GATE, Higher Education, Entrepreneurship, etc. Identifying Area / Content requires experts consultation in the area.

Topics included are like, a. Advanced Topics, b. Recent Developments, c. Certificate Courses, d. Course Projects, e. New Software Tools, f. GATE Topics, g. NPTEL Videos, h. Swayam videos etc.

Expt.	Topic / Description	Area	Remarks	Blooms Level
1	NPTEL Videos /Experiment: Op-amp based ECG Signal Acquisition, Conditioning and Processing for	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and	Analyze L4

	Computation of BPM		assignment questions.	
2	NPTTEL Videos /Experiment: Op-amp based ECG Signal Acquisition, Conditioning and Processing for Computation of BPM	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
3	NPTTEL Videos /Experiment: Op-amp based ECG Signal Acquisition, Conditioning and Processing for Computation of BPM	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
4	NPTTEL Videos /Experiment: Op-amp based ECG Signal Acquisition, Conditioning and Processing for Computation of BPM	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
5	NPTTEL Videos /Experiment: Op-amp based ECG Signal Acquisition, Conditioning and Processing for Computation of BPM	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
6	NPTTEL Videos /Experiment: Op-amp based ECG Signal Acquisition, Conditioning and Processing for Computation of BPM	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
7	NPTTEL Videos /Introduction to Gas Sensors and Experiment on Signalconditioning Circuit for Operating Heater Voltage of MQ-7 Gas Sensor	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
8	NPTTEL Videos /Introduction to Gas Sensors and Experiment on Signalconditioning Circuit for Operating Heater Voltage of MQ-7 Gas Sensor	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
9	NPTTEL Videos /Introduction to Gas Sensors and Experiment on Signalconditioning Circuit for Operating Heater Voltage of MQ-7 Gas Sensor	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
10	NPTTEL Videos /Introduction to Gas Sensors and Experiment on Signalconditioning Circuit for Operating Heater Voltage of MQ-7 Gas Sensor	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
11	NPTTEL Videos /Introduction to Gas Sensors and Experiment on Signalconditioning Circuit for Operating Heater Voltage of MQ-7 Gas Sensor	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4
12	NPTTEL Videos /Introduction to Gas Sensors and Experiment on Signalconditioning Circuit for Operating Heater Voltage of MQ-7 Gas Sensor	Placement/ GATE	Video lecturing by IISc professor on "Electronics Modules for Industrial Applications" and assignment questions.	Analyze L4

B. Laboratory Instructions

1. General Instructions

SNo	Instructions	Remarks
1	Observation book and Lab record are compulsory.	
2	Students should report to the concerned lab as per the time table.	
3	After completion of the program, certification of the concerned staff in-charge in the observation book is necessary.	
4	Student should bring a notebook of 100 pages and should enter the readings /observations into the notebook while performing the experiment.	
5	The record of observations along with the detailed experimental procedure of the experiment in the Immediate last session should be submitted and certified staff member in-charge.	

6	Should attempt all problems / assignments given in the list session wise.	
7	It is responsibility to create a separate directory to store all the programs, so that nobody else can read or copy.	
8	When the experiment is completed, should disconnect the setup made by them, and should return all the components/instruments taken for the purpose.	
9	Any damage of the equipment or burn-out components will be viewed seriously either by putting penalty or by dismissing the total group of students from the lab for the semester/year	
10	Completed lab assignments should be submitted in the form of a Lab Record in which you have to write the algorithm, program code along with comments and output for various inputs given	

2. Laboratory Specific Instructions

SNo	Specific Instructions	Remarks
1	Students are expected to study the circuit, theory and procedures, expected output before doing the experiment.	
2	Adjustment of signal generator: - Before connecting the signal generator to the circuit check the followings. a. Set the shape of the waveform (sinusoidal), b. Set the frequency using coarse and fine adjustments. c. Set the offset adjustments. Set the CRO in DC mode and ensure the waveform is symmetry in both positive and negative cycle. If not , adjust it using the DC offsetting potentiometer d. Set the voltage magnitude using Vcourse settings and Vfine adjustments.	
3	Adjustment of CRO: a. Select the right voltage and time scale to get the proper waveform b. For clipper and clamper circuits, observe the waveform in DC mode only c. Set the input waveform mainly for offset setting in DC mode only. d. Before measurement, ensure X & Y are in calibrated mode (if provided externally) e. Ensure that Channel selection and trigger mode are properly set. f. In case of two channels do not mix the signal and ground terminals	
4	Multi-meter adjustments:- a. Set the right mode before taking the readings. b. For current reading, connect the multimeter in mA (or A) mode to the circuit before switching on the supply. Do not remove the current meter when the supply is on. Check for ac and dc modes as required. c. For voltage reading ensure that proper ac or dc setting. d. Use the proper leads for the measurement. Wrong cables damage the instrument.	
5	After adjusting the input voltage, check the circuit connections before turning the power on.	
6	After adjusting the input voltage, check the circuit connections before turning the power on.	
7	Don't pull out the connections with the power supply on.	
8	Wear your College ID card Do not operate the IC trainer kits without permission	
9	Avoid loose connection and short circuits	
10	Do not interchange the ICs while doing the experiment	
11	Handle the trainer kit properly	
12	Do not panic if you do not get the output	
13	After completion of the experiment switch off the power and return the components	

C. OBE PARAMETERS

1. Laboratory Outcomes

Expt.	Lab Code #	COs / Experiment Outcome	Teach. Hours	Concept	Instr Method	Assessment Method	Blooms' Level
-	-	At the end of the experiment, the student should be able to . . .	-	-	-	-	-
1	17EEL48.1	Design and verify OP-Amp as a precision full wave rectifier using lic hardware kit.	03	Rectification	Conduct ion	Test & Viva Voce	L4
2	17EEL48.2	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non - inverting configuration for a given gain using lic hardware kit.	03	Frequency Response	Conduct ion	Test & Viva Voce	L4
3	17EEL48.3	Design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency using lic hardware kit.	03	Sinoidal signal Generation	Conduct ion	Test & Viva Voce	L4
4	17EEL48.4	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP) using lic hardware kit.	03	Square/ Rectangular Wave Generation	Conduct ion	Test & Viva Voce	L4
5	17EEL48.5	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector using lic hardware kit.	03	Voltage Comparision	Conduct ion	Test & Viva Voce	L3
6	17EEL48.6	Design and verify the operation's of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator using lic hardware kit.	03	Airthmatic Operation	Conduct ion	Test & Viva Voce	L4
7	17EEL48.7	Design and realize an op – amp based first order Butterworth (a) Low pass (b) High pass and (c) Band pass filters for a given cut off frequency frequencies to verify the frequency response characteristic using lic hardware kit.	03	Active filteration	Conduct ion	Test & Viva Voce	L4
8	17EEL48.8	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency using lic hardware kit.	03	Different Signal Generation	Conduct ion	Test & Viva Voce	L4
9	17EEL48.9	Design and realize of R – 2R ladder DAC using lic hardware kit.	03	Digital to Analog Conversion	Conduct ion	Test & Viva Voce	L4
10	17EEL48.10	Realize of Two bit Flash ADC using lic hardware kit.	03	Analog to Digital Conversion	Conduct ion	Test & Viva Voce	L3
11	17EEL38.11	Design and verify an IC 555 timer based pulse generator for the specified pulse using lic hardware kit.	03	Pulse Generation	Conduct ion	Test & Viva Voce	L4
12	17EEL38.12	Designing of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series using lic hardware kit.	03	Voltage Regulation	Conduct ion	Test & Viva Voce	L4
-		Total	36	-	-	-	-

Note: Identify a max of 2 Concepts per unit. Write 1 CO per concept.

2. Laboratory Applications

Expt.	Application Area	CO	Level
1	Rectifiers are used in DC regulated power supply.	CO1	L4
2	Analysis of frequency response of op amp	CO2	L4
3	Signal generator is used in industry, agriculture, boimedicine and other fields such as high frequency induction heating, melting, quenching, ultrasonic diagnosis, nuclear magnetic resonance imaging etc..	CO3	L4
4	Used in square wave generation.	CO4	L4
5	Comparators are used in oscillators, DAC, ADC, multi-vibrators and etc	CO5	L3
6	Summing amplifier is Used in audio mixer to add different signals with n equal gains. Instrumentation amplifiers are used in data acquisition systems.	CO6	L4
7	Active filters are used in communication systems for suppressing noise, in audio systems, biomedical instruments to interface psychological sensors with diagnostic equipments and data logging.	CO7	L4
8	Use in signal/function generator.	CO8	L4
9	DAC are used in data acquisition system.	CO9	L4
10	ADC are used in data acquisition system.	CO10	L3
11	Use in frequency divider, pulse width modulation, linear ramp generator and voltage controlled oscillator.	CO11	L4
12	Regulators are used in developing regulated DC power supply.	CO12	L4

Note: Write 1 or 2 applications per CO.

3. Mapping And Justification

CO – PO Mapping with mapping Level along with justification for each CO-PO pair.

To attain competency required (as defined in POs) in a specified area and the knowledge & ability required to accomplish it.

Expt.	Mapping	Mapping Level	Justification for each CO-PO pair	Level	
-	CO	PO	-	'Area': 'Competency' and 'Knowledge' for specified 'Accomplishment'	-
1	1	1	3	Knowledge of rectification using op amp is required in a designing of DC regulated power supply.	L2
	1	2	3	Analysis of DC regulated power supply need knowledge of rectification using op amp.	L3
	1	3	3	Design of rectifier using op amp is a part of DC regulated power supply design.	L4
	1	11	3	The Design of rectifier using op amp will be used in projects.	L4
2	2	1	3	Knowledge of frequency response of op amp is required in a designing of electronics circuits	L2
	2	2	3	Analysis of problem of electronics circuits need knowledge of frequency response of op amp.	L3
	2	3	3	Design of amplifier using op amp for given gain is a part of electronics circuits design.	L4
	2	11	3	The Design of amplifier for desired gain using op amp will be used in projects.	L4
3	3	1	3	Knowledge of signal generator using op amp is required in a designing of complex electronics circuits.	L2
	3	2	3	Analysis of complex electronics circuits may need knowledge of signal generator using op amp.	L3
	3	3	3	Design of signal generator using op amp is a part of complex electronic circuits design.	L4
	3	11	3	The Design of signal generator using op amp may be used in projects.	L4
4	4	1	3	Knowledge of comparator and converter using op amp is required in a designing of complex electronics circuits.	L2
	4	2	3	Analysis of complex electronics circuits may need knowledge of using comparator and converter using op amp.	L3
	4	3	3	Design of comparator and converter using op amp is a part of complex electronic circuits design.	L4

	4	11	3	The Design of comparator and converter using op amp will be used in projects.	L4
5	5	1	3	Knowledge of comparator and converter using op amp is required in a designing of complex electronics circuits.	L2
	5	2	3	Analysis of complex electronics circuits may need knowledge of using comparator and converter using op amp.	L3
	5	11	3	The Design of comparator and converter using op amp will be used in projects.	L4
6	6	1	3	Knowledge of linear applications such as adder,summer,AC and DC amplifier using op amp is required in understanding the working of complex electronic circuits.	L2
	6	2	3	Analysis of complex electronic circuits needs knowledge of Op amp linear applications.	L3
	6	3	3	Design of linear applications such as adder,summer,AC and DC amplifier using op amp are used in many instrumentation amplifier	L4
	6	11	3	The Design knowledge of linear applications of Op Amp can be used in electronic-projects.	L4
7	7	1	3	Knowledge of filters using op amp is required in understanding the working of complex electronic circuits.	L2
	7	2	3	Analysis of complex electronic circuits needs knowledge of filters using op amp.	L3
	7	3	3	Design of filters using op amp are used usually part of communication systems.	L4
	7	11	3	The Design knowledge of filters using Op Amp can be used in electronic-projects.	L4
8	8	1	3	Knowledge of signal generator using op amp is required in a designing of complex electronics circuits.	L2
	8	2	3	Analysis of complex electronics circuits may need knowledge of signal generator using op amp.	L3
	8	3	3	Design of signal generator using op amp is a part of complex electronic circuits design.	L4
	8	11	3	The Design of signal generator using op amp may be used in projects.	L4
9	9	1	3	Knowledge of D/A conversion using op amp is required in a designing of Data acquisition systems.	L2
	9	2	3	Analysis of Data acquisition system need knowledge of D/A conversion using op amp.	L3
	9	3	3	Knowledge of D/A conversion using op amp will be applied in projects.	L4
	9	11	3	Knowledge of D/A conversion using op amp will be applied in projects.	L4
10	10	1	3	Knowledge of A/D conversion using op amp is required in a designing of Data acquisition systems.	L2
	10	2	3	Analysis of Data acquisition system need knowledge of A/D conversion using op amp.	L3
	10	11	3	Knowledge of A/D conversion using op amp will be applied in projects.	L4
11	11	1	3	Knowledge of pulse generation using 555 timer is required in delay and timing circuits such as clock pulse generation.	L2
	11	2	3	Analysis of delay and timing circuits need knowledge of pulse generation using 555 timer.	L3
	11	3	3	Design of multi-vibrator using 555 timer can be a part of complex application design.	L4
	11	11	3	Knowledge of pulse generation using 555 timer will be applied in projects.	L4
12	12	1	3	Knowledge of regulators using op amp is required in a designing of DC power supply.	L2
	12	2	3	Analysis of DC power supply needs knowledge of regulator using op amp.	L3
	12	3	3	Design of regulator using op amp is a part of DC power supply design.	L4
	12	11	3	The Design of DC power supply is used in developing a power supply system for projects.	L4

4. Articulation Matrix

CO – PO Mapping with mapping level for each CO-PO pair, with course average attainment.

-	-	Experiment Outcomes	Program Outcomes															-	
			PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12	PS O1	PS O2	PS O3		Level
1	17EEL48.1	Design and verify OP-Amp as a precision full wave rectifier using lic hardware kit.	3	3	3									3					L4
2	17EEL48.2	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non - inverting configuration for a given gain using lic hardware kit.	3	3	3									3					L4
3	17EEL48.3	Design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency using lic hardware kit.	3	3	3									3					L4
4	17EEL48.4	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP) using lic hardware kit.	3	3	3									3					L3
5	17EEL48.5	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector using lic hardware kit.	3	3										3					L4
6	17EEL48.6	Design and verify the operation's of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator using lic hardware kit.	3	3	3									3					L4
7	17EEL48.7	Design and realize an op – amp based first order Butterworth (a) Low pass (b) High pass and (c) Band pass filters for a given cut off frequency frequencies to verify the frequency response characteristic using lic hardware kit.	3	3	3									3					L4
8	17EEL48.8	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency using lic hardware kit.	3	3	3									3					L4
9	17EEL48.9	Design and realize of R – 2R ladder DAC using lic hardware kit.	3	3	3									3					L3
10	17EEL48.10	Realize of Two bit Flash ADC using lic hardware kit.	3	3										3					L4
11	17EEL38.11	Design and verify an IC 555 timer based pulse generator for the specified pulse using lic hardware kit.	3	3	3									3					L4
12	17EEL38.12	Designing of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series using lic hardware kit.	3	3	3									3					
-	PO, PSO	1.Engineering Knowledge; 2.Problem Analysis; 3.Design / Development of Solutions;																	

		4. Conduct Investigations of Complex Problems; 5. Modern Tool Usage; 6. The Engineer and Society; 7. Environment and Sustainability; 8. Ethics; 9. Individual and Teamwork; 10. Communication; 11. Project Management and Finance; 12. Life-long Learning; S1. Software Engineering; S2. Data Base Management; S3. Web Design
--	--	---

5. Curricular Gap and Experiments

Topics & contents not covered (from A.4), but essential for the course to address POs and PSOs.

Expt	Gap Topic	Actions Planned	Schedule Planned	Resources Person	PO Mapping
1					
2					
3					
4					
5					

Note: Write Gap topics from A.4 and add others also.

6. Experiments Beyond Syllabus

Topics & contents required (from A.5) not addressed, but help students for Placement, GATE, Higher Education, Entrepreneurship, etc.

Expt	Gap Topic	Actions Planned	Schedule Planned	Resources Person	PO Mapping
1	Experiment: Op-amp based ECG Signal Acquisition, Conditioning and Processing for Computation of BPM	Video Session	14 th Feb 2019	Dr Hardik Pandey, IISc Professor	3

D. COURSE ASSESSMENT

1. Laboratory Coverage

Assessment of learning outcomes for Internal and end semester evaluation. Distinct assignment for each student. 1 Assignment per chapter per student. 1 seminar per test per student.

Unit	Title	Teaching Hours	No. of question in Exam							CO	Levels
			CIA-1	CIA-2	CIA-3	Asg-1	Asg-2	Asg-3	SEE		
1	Design and verify a precision full wave rectifier. Determine the performance parameters.	03		1	-	-	-	-	1	CO1	L4
2	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non- inverting configuration for a given gain.	03	1	-	-	-	-	-	1	CO2	L4
3	Design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency.	03	-	1	-	-	-	-	1	CO3	L4
4	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP).	03	-	1	-	-	-	-	1	CO4	L4
5	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector.	03	1	-	-	-	-	-	1	CO5	L3
6	Design and verify the operation	03	1	-	-	-	-	-	1	CO6	L4

	of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator.											
7	Design and realize an op – amp based first order Butterworth (a) low pass (b) high pass and (c) band pass filters for a given cut off frequency/frequencies to verify the frequency response characteristic.	03	1	-	-	-	-	-	1	CO7	L4	
8	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency.	03		1	-	-	-	-	1	CO8	L4	
9	Design and realization of R – 2R ladder DAC	03	-	-	1	-	-	-	1	CO9	L4	
10	Realization of Two bit Flash ADC.	03	-	-	1	-	-	-	1	CO10	L3	
11	Design and verify an IC 555 timer based pulse generator for the specified pulse.	03	-	-	1	-	-	-	1	CO11	L4	
12	Designing of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series.	03	-	-	1	-	-	-	1	CO12	L4	
-	Total	40	4	4	4				12	-	-	

2. Continuous Internal Assessment (CIA)

Assessment of learning outcomes for Internal exams. Blooms Level in last column shall match with A.2.

Evaluation	Weightage in Marks	CO	Levels
CIA Exam – 1	30	CO2, CO5, CO6, CO7	L4, L3, L4,L4
CIA Exam – 2	30	CO1, CO3, CO4,CO8	L4, L4, L3,L4
CIA Exam – 3	30	CO9, CO10, CO11,CO12	L4, L3, L4 ,L4
Assignment - 1	10	CO2, CO5, CO6, CO7	L4, L3, L4,L4
Assignment - 2	10	CO1, CO3, CO4,CO8	L4, L4, L3,L4
Assignment - 3	10	CO9, CO10, CO11,CO12	L4, L3, L4 ,L4
Seminar - 1			
Seminar - 2			
Seminar - 3			
Other Activities – define – Slip test			
Final CIA Marks	40	-	-


-

SNo	Description	Marks
1	Observation and Weekly Laboratory Activities	05 Marks
2	Record Writing	10 Marks for each Expt
3	Internal Exam Assessment	25 Marks
4	Internal Assessment	40 Marks
5	SEE	60 Marks
-	Total	100 Marks

E. EXPERIMENTS

Experiment 01 : Precision Full Wave Rectifier

-	Experiment No.:	1	Marks		Date Planned		Date Conducted	
1	Title	Design and verify a precision full wave rectifier. Determine the performance parameters.						
2	Course Outcomes	Design and verify OP-Amp as a precision full wave rectifier using licr hardware kit.						
3	Aim	To Design and verify OP-Amp as a precision full wave rectifier.						
4	Material / Equipment Required	Lab Manual/ CRO, Signal generator, capacitor, diodes, power chord, ameter, multi-meter, .						
		SI NO	Name	Range	Quantity			
		1	Regulated Dual Power Supply	0-20V	1			
		2	Resistors	1.5K Ω (1),22K Ω (2),10K Ω (1)	4			
		3	Capacitors	0.1 μ F, 0.01 μ F	2			
		4	CRO	-	1			
		5	Multimeter	-	1			
		6	IC μ A741	-	1			
		7	Patch Chords	-				
		8	LIC Trainer Kit	-	1			
		9	Stepdown Transformer					
5	Theory, Formula, Principle, Concept	Full wave precision rectifier consisting of a summing circuit and a precision half wave rectifier.The advantage of the op-amp precision rectifier circuit over a simple diode rectifier are 1) no diode voltage drop between input and output 2) the ability to rectify very small voltages(less than the typical 0.7V diode forward voltage drop) 3) amplification . if required and 4) low output impedence .						

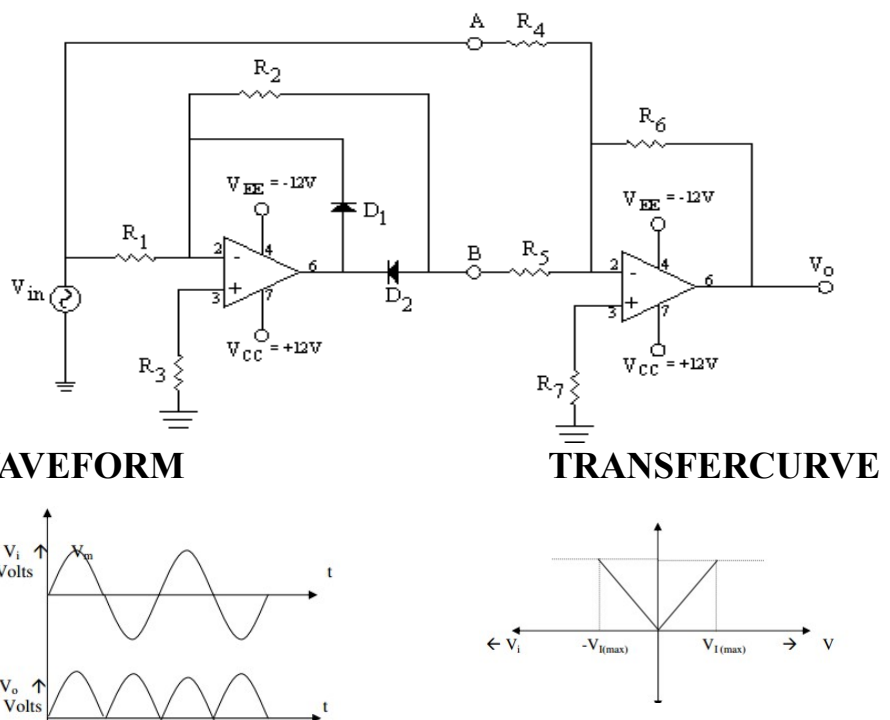		<p>During positive half cycle , the output $V_o = (R_6/R_5)V_{in}$</p> <p>During negative half cycle, the output $V_o = -(R_6/R_5)V_{in}$</p> <p>It is seen that the output V_o is a full wave rectified version of the input voltage.If resistors R_6 equals R_4 and R_5, the circuit has an overall gain of 1.When R_6 is greater than R_4 and R_5, amplification and rectification both occur.</p>
<p>6 Procedure, Program Activity, Algorithm, Pseudo Code</p>	<p>Step 1: Do the connections as per the circuit diagram.</p> <p>Step2: sine wave of 0.5Vp, 1MHZ as input to the op – amp. Bias the op – amp with supply voltage of +12V and -12V.</p> <p>Step3:observe input and rectified output waveform in CRO.</p> <p>Step4:calculate ripple fctor and efficiency of full wave prcision rectifier.</p> <p>Step5: Draw the output waveform</p>	
<p>7 Block, Circuit, Model Diagram, Reaction Equation, Expected Graph</p>		 <p>WAVEFORM</p> <p>TRANSFER CURVE</p>
<p>8 Observation Table, Look-up Table, Output</p>		
<p>9 Sample Calculation</p>		<p>Design a precision full wave rectifier circuit to produce a 2V peak output from a sine wave input with a peak value of 0.5V and a frequency of 1 MHZ..</p> <p>Let $I_1 = 500\mu A$ (for adequate diode current)</p> <p>$R_1 = V_i / I_1 = 0.5V / 500\mu A = 1K\Omega$</p> <p>$R_2 = 2R_1 = 2 K\Omega$ (use two 1KΩ resistors in series)</p> <p>$R_3 = R_1 \parallel R_2 = 1K\Omega \parallel 2K\Omega = 670\Omega$ (use 680Ω standard value)</p> <p>$R_4 = R_5 = R_1 = 1K\Omega$ (std value)</p> <p>For the output to be 2V when the input is 0.5V</p> <p>$R_6 = (V_o / V_{in}) \times R_5$</p> <p>$= (2v / 0.5v) \times 1K\Omega$</p>

		$= 4\text{ K}\Omega$ (use $3.9\text{ K}\Omega$ std value) $R7 = R4 \parallel R5 \parallel R6 = 1\text{K}\Omega \parallel 1\text{K}\Omega \parallel 3.9\text{K}\Omega$ $= 443\text{ K}\Omega$ (use 470Ω std value) Calculations: Ripple Factor = $V_{\text{oac}} / V_{\text{odc}}$
10	Graphs, Outputs	
11	Results & Analysis	Designed and Verified the output of a precision full wave rectifier and determined the performance parameters such as efficiency and regulation.
12	Application Areas	Rectifiers are used in DC regulated power supply.
13	Remarks	
14	Faculty Signature with Date	


Experiment 02 : Frequency Response of an Op – Amp

-	Experiment No.:	2	Marks	Date Planned	Date Conducted
1	Title	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non- inverting configuration for a given gain.			
2	Course Outcomes	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non- inverting configuration for a given gain using lic hardware kit.			
3	Aim	To design and realize to analyse the frequency response of an op – amp amplifier under inverting and non- inverting configuration for a given gain.			
4	Material Equipment Required	/Lab Manual/ CRO, Signal generator, capacitor, diodes, power chord, ammeter, multi-meter.			
		SI NO	Name	Range	Quantity
		1	Regulated Dual Power Supply	0-20V	1
		2	Resistors	1.5KΩ(1),22KΩ(2),10KΩ(1)	4
		3	Capacitors	0.1μF, 0.01μF	2
		4	CRO	-	1
		5	Multimeter	-	1
		6	ICμA741	-	1
		7	Patch Chords	-	

		8	LIC Trainer Kit	-	1
		9	Stepdown Transformer		
5	Theory, Formula, Principle, Concept	<p>THEORY:</p> <p>INVERTING AMPLIFIER: The fundamental component of any analog computer is the operational amplifier or op-amp and the frequency configuration in which it is used as an inverting amplifier. An input voltage V_{in} is applied to the input voltage. It receives and inverts its polarity producing an output voltage. this same output voltage is also applied to a feedback resistor R_f, which is connected to the amplifier input analog with R_1. The amplifier itself has a very high voltage gain.</p> <p style="text-align: center;">$\text{If } R_f = R_1 \text{ then } V_o = -V_i$</p> <p>NON- INVERTING AMPLIFIER: Although the standard op-amp configuration is as an inverting amplifier, there are some applications where such inversion is not wanted. However, we cannot just switch the inverting and non inverting inputs to the amplifier itself. We will still need negative feedback to control the working gain of the circuit .Therefore, we will need to leave the resistor structure around the op-amp intact and swap the input and ground connections to the overall circuit.</p> <p style="text-align: center;">$V_o / V_i = (R_f / R_i) + 1$</p> <p>From the calculations, we can see that the effective voltage gain of the non-inverting amplifier is set by the resistance ratio. Thus, if the two resistors are equal value, then the gain will be 2 rather than 1.</p>			
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<ol style="list-style-type: none"> 1) Do the connection as per the circuit diagram 2) Bias the op - amp with supply voltage of +12V and -12V. Apply a input sinusoidal signal of constant voltage to the inverting / non inverting terminal of the op-amp. 3) Tabulate the o/p voltage V_o w.r.t. different values of input frequency. 4) Calculate the gain A_f and plot the graph of frequency V/S A_f and check the graph to get approximately the same characteristic as shown in the expected graph. 			
7	Block, Circuit, Model Diagram, Reaction Equation, Expected Graph	<p style="text-align: center;">CIRCUIT DIAGRAM:</p> <div style="display: flex; justify-content: space-around;"> <div data-bbox="491 1713 821 2011"> </div> <div data-bbox="965 1713 1321 2011"> </div> </div> <p style="text-align: center;">Fig 2.1 Inverting Amplifier Fig2.2 Non -</p>			

Inverting Amplifier

SPECIMEN GRAPH

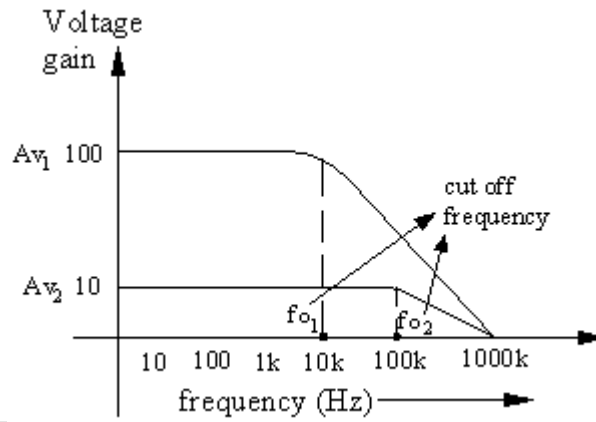

8 Observation Table, Look-up Table, Output

TABULAR COLUMN

Inverting Amplifier for a gain of _ ,the v_{in} ----- V

Frequency(HZ)	V_o (volts)	$A_f = V_o / V$	Gain in dB $A_{fdB} = 20 \log V_o / V_{in}$

Non -Inverting Amplifier for a gain of ----- the V_{in} is ---- V

Frequency(HZ)	V_o (volts)	$A_f = V_o / V$	Gain in dB $A_{fdB} = 20 \log V_o / V_{in}$

9	Sample Calculations	<p>DESIGN</p> <p>Inverting Amplifier:-</p> <p>a) Let gain $A_f = 10$ As WKT $A_f = -R_f / R_1$ and $UGB = 1\text{MHz}$ let $R_1 = 1\text{k}\Omega$ Therefore $R_f = A_f R_1 = 10\text{k}\Omega$, $R_{\text{comp}} = R_f \parallel R_1 = 10\text{k}\Omega \parallel 1\text{k}\Omega = 1\text{k}\Omega$ $\beta = R_1 / (R_1 + R_f) = 1\text{k}\Omega / (1\text{k}\Omega + 10\text{k}\Omega) = 1/11$ $f_F = f_O (1 + A\beta) = 5 (1 + 200,000 \times (1/11)) = 90\text{KHZ}$</p> <p>b) Let gain $A_f = 100$ As WKT $A_f = -R_f / R_1$ and $UGB = 1\text{MHz}$ let $R_1 = 1\text{k}\Omega$ Therefore $R_f = A_f R_1 = 100\text{k}\Omega$, $R_{\text{comp}} = R_f \parallel R_1 = 100\text{k}\Omega \parallel 1\text{k}\Omega = 1\text{k}\Omega$ $\beta = R_1 / (R_1 + R_f) = 1\text{k}\Omega / (1\text{k}\Omega + 100\text{k}\Omega) = 1/101$ $f_F = f_O (1 + A\beta) = 5 (1 + 200,000 \times (1/101)) = 10\text{KHZ}$</p> <p>Non -Inverting Amplifier:-</p> <p>a) Let gain $A_f = 10$ As WKT $A_f = 1 + (R_f / R_1)$ and $UGB = 1\text{MHz}$ Let $R_1 = 1\text{k}\Omega$ $10 = 1 + (R_f / 1\text{k}\Omega)$ $R_f = 9\text{k}\Omega = 10\text{k}\Omega$ $\beta = R_1 / (R_1 + R_f) = 1\text{k}\Omega / (1\text{k}\Omega + 10\text{k}\Omega) = 1/11$ $f_F = f_O (1 + A\beta) = 5 (1 + 200,000 \times (1/11)) = 90\text{KHZ}$</p> <p>b) Let gain $A_f = 100$ As WKT $A_f = 1 + (R_f / R_1)$ and $UGB = 1\text{MHz}$ Let $R_1 = 1\text{k}\Omega$ $100 = 1 + (R_f / 1\text{k}\Omega)$</p>			

		$R_f = 99K\Omega = 100K\Omega$, $R_{comp} = R_f \parallel R_1 = 100K\Omega \parallel 1K\Omega = 1K\Omega$ $\beta = R_1 / (R_1 + R_f) = 1K\Omega / (1K\Omega + 100K\Omega) = 1/101$ $f_F = f_O (1 + A\beta) = 5 (1 + 200,000 \times (1/101)) = 10KHZ$
10	Graphs, Outputs	
11	Results & Analysis	Designed and realized to analyse the frequency response of an op – amp amplifier under inverting and non- inverting configuration for a gain of 10.
12	Application Areas	Analysis of frequency response of op amp
13	Remarks	
14	Faculty Signature with Date	RC Phase Shift Oscillator

Experiment 03: RC Phase Shift Oscillator

-	Experiment No.:	3	Marks		Date Planned		Date Conducted	
1	Title	Design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency.						
2	Course Outcomes	Design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency using lic hardware kit.						
3	Aim	To design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency.						
4	Material Equipment Required	/Lab Manual/ CRO, Signal generator, capacitor, resistors, power chord, ammeter, multi-meter, BJT.						
		SI NO	Name	Range	Quantity			
		1	Regulated Dual Power Supply	0-20V	1			
		2	Resistors	1.5K Ω (1),22K Ω (2),10K Ω (1)	4			
		3	Capacitors	0.1 μ F, 0.01 μ F	2			
		4	CRO	-	1			
		5	Multimeter	-	1			
		6	IC μ A741	-	1			
		7	Patch Chords	-				
		8	LIC Trainer Kit	-	1			
		9	Stepdown Transformer					
5	Theory, Formula, Principle, Concept	THEORY: RC phase shift oscillator produces 360° of phase shift in two parts. Firstly, each and every RC pair in the feedback network produces						

60° phase shift and totally there were three pairs, thus producing 180° Phase shift and secondly, the feedback input is given to the inverting terminal of op-amp to produce another 180° phase shift and a total phase shift of 360°.

The frequency of oscillation is given by $f_0 = 1 / 2\pi\sqrt{6 RC}$; If an inverting amplifier is used, the gain must be atleast equal to 29 to ensure the oscillations with constant amplitude that is, $|A_V\beta| < 1$. Otherwise the oscillation will die out.

6 Procedure, Program, Activity, Algorithm, Pseudo Code

PROCEDURE:

- 1) Do the connection as per the circuit diagram.
- 2) Bias the op – amp with supply voltage of +12V and -12V.
- 3) Observe the amplitude and frequency of output waveform in CRO.
- 4) Draw the waveform

7 Block, Circuit, Model Diagram, Reaction Equation, Expected Graph

CIRCUIT DI


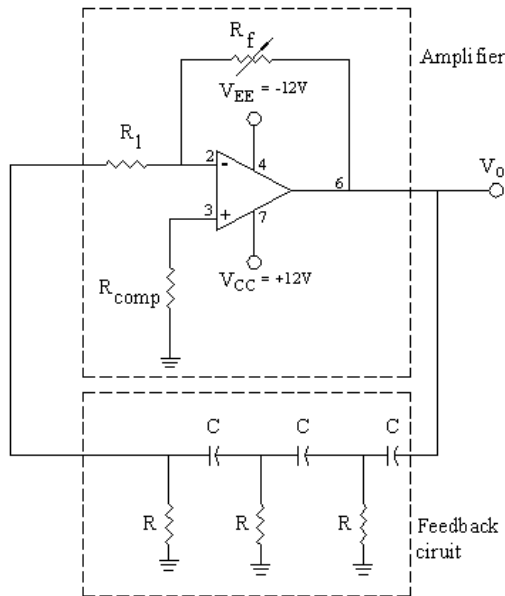


Fig. 3.4 RC Phase Shift Oscillator

WAVEFORM:


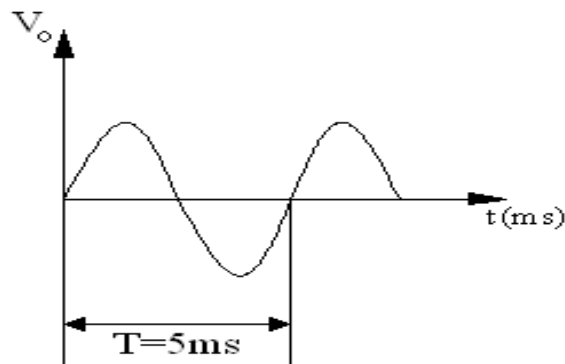


8	Observation Table, Look-up Table, Output	
9	Sample Calculations	<p>DESIGN:</p> <p>Design Problem: Design of RC Phase shift oscillator to oscillate at $f_0 = 500$ HZ.</p> <p>1) Let C = 0.1 μF W.K.T $f_0 = 1 / 2\pi\sqrt{6} RC$ $f_0 = 0.065/RC$ therefore $R = 0.065/f_0 C$ $= 0.065 / (500 \times 0.1 \times 10^{-6})$ $= 1.31 \text{ K}\Omega$ R = 1.5 KΩ (std)</p> <p>2) To prevent the loading of amplifier because of RC network, it is necessary that $R_1 \geq 10R$ so take $R_1 = 10 \times 1.5 \text{ K}\Omega$ R₁ = 15 KΩ</p> <p>3) At the given frequency, the gain must be atleast 29 i.e (for inverting) $R_f/R_1 = 29$ Therefore $R_f = 29 R_1$ $= 29 \times 15 \text{ K}\Omega$ $R_f = 435 \text{ K}\Omega$ R_f = 1MΩ (std value)</p> <p>4) Let $R_{comp} = R_f \parallel R_1$ $= 15\text{K}\Omega \parallel 1\text{M}\Omega$ R_{comp} = 15KΩ •</p>
10	Graphs, Outputs	
11	Results & Analysis	Designed and verified the output waveform of an op – amp RC phase shift oscillator for a frequency of 500HZ
12	Application Areas	Signal generator is used in industry, agriculture, boimedicine and other fields

		such as high frequency induction heating, melting , quenching, ultrasonic diagnosis, nuclear magnetic resonance imaging etc..
13	Remarks	
14	Faculty Signature with Date	

Experiment 04 : Schmitt Trigger Circuit using an Op – Amp

-	Experiment No.:	4	Marks		Date Planned		Date Conducted	
1	Title	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP).						
2	Course Outcomes	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP) using lic hardware kit.						
3	Aim	To design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP).						
4	Material Equipment Required	/	SI NO	Name	Range	Quantity		
			1	Regulated Dual Power Supply	0-20V	1		
			2	Resistors	1,5KΩ(1),22KΩ(2),10KΩ(1)	4		
			3	Capacitors	0.1μF, 0.01μF	2		
			4	CRO	-	1		
			5	Multimeter	-	1		
			6	ICμA741	-	1		
			7	Patch Chords	-			
			8	LIC Trainer Kit	-	1		
			9	Stepdown Transformer				
5	Theory, Formula, Principle, Concept	<p>THEORY: A circuit which converts a irregular shaped waveform to a square wave or pulse is called a Schmitt trigger or squaring circuit. The input voltage V_{in} triggers the output V_o every time it exceeds certain voltage levels called upper threshold voltage V_{UT} and lower threshold voltage V_{LT}. The threshold voltages are obtained by using the voltage divider. A comparator with positive feedback is said to exhibit hysteresis, a dead band condition. The hysteresis voltage is the difference between V_{UT} & V_{LT}.</p> <p>There are two types of Schmitt trigger based on where the irregular wave is given. They are, Inverting & non-inverting Schmitt trigger. Schmitt trigger finds application in wave shaping circuits. The other name given to Schmitt trigger is regenerative comparator</p>						
6	Procedure, Program, Activity,	<p>PROCEDURE: 1) Do the connection as per the circuit diagram.</p>						

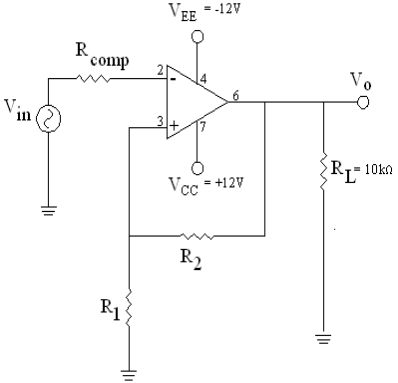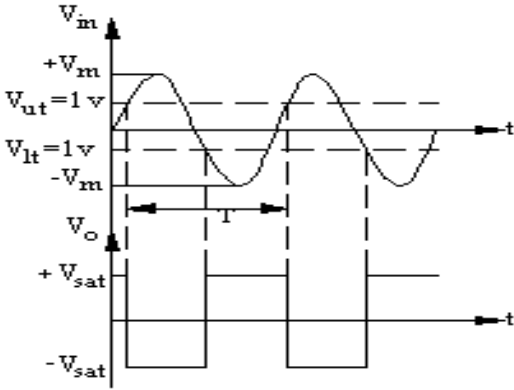	Algorithm, Pseudo Code	<p>2) Bias the op - amp with supply voltage of +12V and -12V.</p> <p>3) Apply the input signal to the inverting terminal of op - amp and set $V_{utp} = 1V$ and $V_{ltp} = -1V$.</p> <p>4) Observe the Input and output waveform in CRO.</p>
7	Block, Model, Circuit, Diagram, Reaction Equation, Expected Graph	<p>CIRCUIT DIAGRAM:</p>  <p>WAVEFORMS:</p> 
8	Observation Table, Look-up Table, Output	
9	Sample Calculations	<p>DESIGN:</p> <p>Select the desired value of V_{utp} and V_{ltp} with same magnitude and opposite polarity.</p> <p>Let $V_{utp} = +2V$ and $V_{ltp} = -2V$</p> <p>Inverting Schmitt Trigger</p> <p>1) For op - amp $\mu A741$ IC $+V_{supply} = +12V$ and $+V_{sat} = +11V$.</p> <p>2) $I_2 \geq I_{B(max)}$, Let $I_2 = 100 \times I_{B(max)} = 100 \times 500 \text{ nA} = 50 \mu A$</p> <p>3) $R_2 = \text{Trigger Voltage} / I_2 = 2V / 50 \mu A = 40K\Omega = 39K\Omega$ (standard value) $I_{2new} = 2V / 39K\Omega = 51.3 \mu A$</p> <p>4) $R_1 = (V_o - \text{Trigger Voltage}) / I_{2new} = (V_{sat} - 2V) / 51.3 \mu A = (11 - 2) / 51.3 \mu A = 175K\Omega = 180K\Omega$ (standard value)</p>

		<p>Non - Inverting Schmitt Trigger</p> <p>1) For op - amp $\mu A741$ IC $-V_{\text{supply}} = -12\text{V}$ and $-V_{\text{sat}} = -11\text{V}$.</p> <p>2) $I_2 \geq I_{B(\text{max})}$. Let $I_2 = 100 \times I_{B(\text{max})} = 100 \times 500 \text{ nA} = 50 \mu\text{A}$</p> <p>3) $R_1 = \text{Trigger Voltage} / I_2 = 2\text{V} / 50 \mu\text{A} = 40\text{K}\Omega = 39\text{K}\Omega$ (standard value)</p> <p>$I_{2\text{new}} = 2\text{V} / 39\text{K}\Omega = 51.3 \mu\text{A}$</p> <p>4) $R_2 = V_o / I_{2\text{new}} = 11 / 51.3 \mu\text{A} = (11 - 2) / 51.3 \mu\text{A} = 214\text{K}\Omega$ $= 180\text{K}\Omega$ (standard value)</p>
10	Graphs, Outputs	
11	Results & Analysis	Designed and realized Schmitt trigger circuit using an op - amp for upper trip point (UTP) of +2v and lower trip point (LTP) of -2V.
12	Application Areas	Used in square wave generation.
13	Remarks	
14	Faculty Signature with Date	

Experiment 05: Voltage Comparator and zero Crossing Detector using Op Amp

-	Experiment No.:	5	Marks		Date Planned		Date Conducted																																									
1	Title	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector.																																														
2	Course Outcomes	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector using lic hardware kit.																																														
3	Aim	To verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector.																																														
4	Material Equipment Required	/	<table border="1"> <thead> <tr> <th>SI NO</th> <th>Name</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Regulated Dual Power Supply</td> <td>0-20V</td> <td>1</td> </tr> <tr> <td>2</td> <td>Resistors</td> <td>1,5KΩ(1),22KΩ(2),10KΩ(1)</td> <td>4</td> </tr> <tr> <td>3</td> <td>Capacitors</td> <td>0.1μF, 0.01μF</td> <td>2</td> </tr> <tr> <td>4</td> <td>CRO</td> <td>-</td> <td>1</td> </tr> <tr> <td>5</td> <td>Multimeter</td> <td>-</td> <td>1</td> </tr> <tr> <td>6</td> <td>ICμA741</td> <td>-</td> <td>1</td> </tr> <tr> <td>7</td> <td>Patch Chords</td> <td>-</td> <td></td> </tr> <tr> <td>8</td> <td>LIC Trainer Kit</td> <td>-</td> <td>1</td> </tr> <tr> <td>9</td> <td>Stepdown Transformer</td> <td></td> <td></td> </tr> </tbody> </table>						SI NO	Name	Range	Quantity	1	Regulated Dual Power Supply	0-20V	1	2	Resistors	1,5KΩ(1),22KΩ(2),10KΩ(1)	4	3	Capacitors	0.1μF, 0.01μF	2	4	CRO	-	1	5	Multimeter	-	1	6	ICμA741	-	1	7	Patch Chords	-		8	LIC Trainer Kit	-	1	9	Stepdown Transformer		
SI NO	Name	Range	Quantity																																													
1	Regulated Dual Power Supply	0-20V	1																																													
2	Resistors	1,5KΩ(1),22KΩ(2),10KΩ(1)	4																																													
3	Capacitors	0.1μF, 0.01μF	2																																													
4	CRO	-	1																																													
5	Multimeter	-	1																																													
6	ICμA741	-	1																																													
7	Patch Chords	-																																														
8	LIC Trainer Kit	-	1																																													
9	Stepdown Transformer																																															
5	Theory, Formula, Principle, Concept	<p>THEORY: Comparator:</p> <p>A comparator circuit is one which compares a voltage signal at one input with a known reference signal at the other input. It works in open loop mode. There are basically two types of comparator namely inverting and non-inverting comparators. The output will be either +V_{sat} or -V_{sat} depending upon the amplitude of the signal at the input terminal. If the amplitude of the noninverting terminal signal is greater than the inverting terminal signal then the output will be +V_{sat} and vice-versa.</p>																																														

Zero Crossing Detector:

The zero crossing detector is a special case basic comparator circuit. If we set reference voltage zero then a comparator behaves like a zero crossing detector.


6 Procedure, Program, Activity, Algorithm, Pseudo Code

PROCEDURE:

- 1) Do the connection as per the circuit diagrams.
- 2) Bias the op - amp with supply voltage of +12V and -12V.
- 3) A fixed reference voltage V_{ref} is applied to the inverting terminal and to the non inverting terminal a varying voltage V_{in} is applied as shown in circuit diagram.
- 4) Vary the input voltage above and below the V_{ref} and note down the output at pin 6 of 741 IC.
- 5) Observe that, when V_{in} is less than V_{ref} , the output voltage is $-V_{sat}$ (@ - VEE) when V_{in} is greater than V_{ref} , the output voltage is $+V_{sat}$ (@+VCC)
- 6) Observe input and output waveforms in CRO.
- 7) Draw the waveforms.

7 Block, Model, Reaction Equation, Expected Graph

CIRCUIT DIAGRAM:

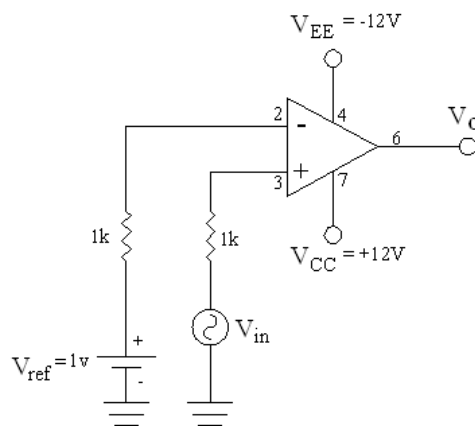

Fig

5.1 Voltage Comparator


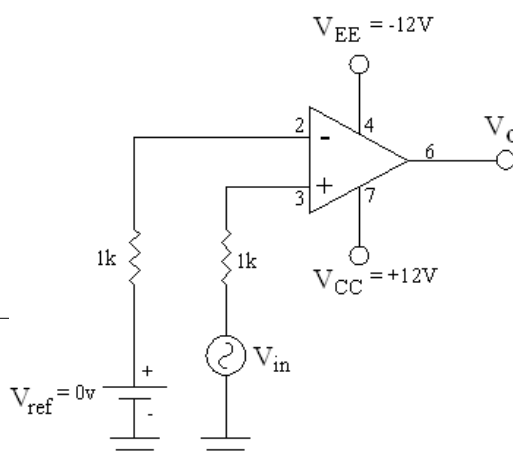



Fig 5.2 Zero Crossing Detector

W WA EFORM:

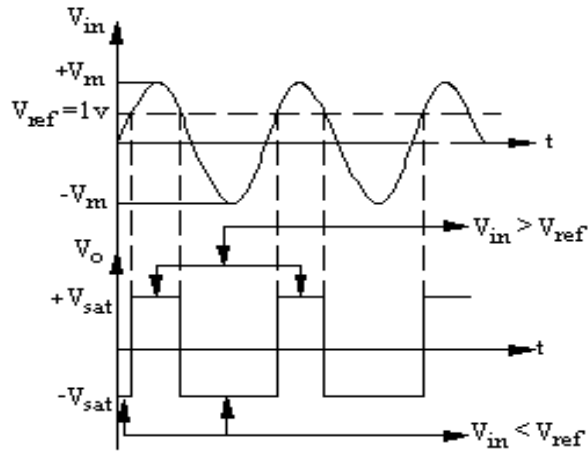

Volt

Voltage Comparator

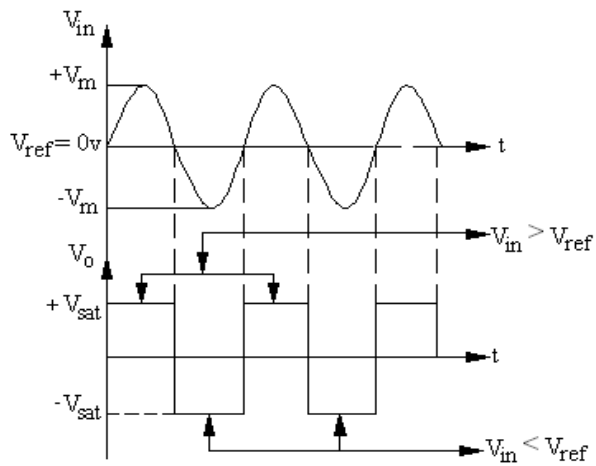

Z

Zero Crossing Detector

8	Observation Table, Look-up Table, Output
9	Sample Calculations
10	Graphs, Outputs

11	Results & Analysis	Verified the operation of an op – amp as (a) voltage comparator circuit for $V_{ref} \pm 1V$ and (b) zero crossing detector.
12	Application Areas	Comparators are used in oscillators, DAC, ADC , multi-vibrators and etc
13	Remarks	
14	Faculty Signature with Date	

Experiment 06: Op – Amp as an (a) Adder (b) Subtractor (c) Integrator and (d) Differentiator.

-	Experiment No.:	6	Marks		Date Planned		Date Conducted	
1	Title	Design and verify the operation of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator.						
2	Course Outcomes	Design and verify the operation of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator using lic hardware kit.						
3	Aim	To design and verify the operation of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator.						
4	Material Equipment Required	/	SI NO	Name	Range	Quantity		
			1	Regulated Dual Power Supply	0-20V	1		
			2	Resistors	1.5K Ω (1),22K Ω (2),10K Ω (1)	4		
			3	Capacitors	0.1 μ F, 0.01 μ F	2		
			4	CRO	-	1		
			5	Multimeter	-	1		
			6	IC μ A741	-	1		
			7	Patch Chords	-			
			8	LIC Trainer Kit	-	1		
5	Theory, Formula, Principle, Concept	<p>THEORY:</p> <p>Adder: A two input summing amplifier may be constructed using the inverting mode. The adder can be obtained by using either non-inverting mode or differential amplifier. Here the inverting mode is used. So the inputs are applied through resistors to the inverting terminal and non-inverting terminal is grounded. This is called "virtual ground", i.e. the voltage at that terminal is zero. The gain of this summing amplifier is 1, any scale factor can be used for the inputs by selecting proper external resistors.</p> <p>Subtractor: A basic differential amplifier can be used as a subtractor as shown in the circuit diagram. In this circuit, input signals can be scaled to the desired values by selecting appropriate values for the resistors. When this is done, the circuit is referred to as scaling amplifier. However in this circuit all external resistors are equal in value. So the gain of amplifier is equal to one. The output voltage V_o is equal to the voltage applied to the noninverting terminal minus the voltage applied to the inverting</p>						

		<p>terminal; hence the circuit is called a subtractor.</p> <p>Integrator: In an integrator circuit, the output voltage is integral of the input signal. The output voltage of an integrator is given by $V_o = -1/R_1 C_f \int V_i dt$ At low frequencies the gain becomes infinite, so the capacitor is fully charged and behaves like an open circuit. The gain of an integrator at low frequency can be limited by connecting a resistor in shunt with capacitor.</p> <p>Differentiator: In the differentiator circuit the output voltage is the differentiation of the input voltage. The output voltage of a differentiator is given by $V_o = -R_f C_1 dV_i / dt$. The input impedance of this circuit decreases with increase in frequency, thereby making the circuit sensitive to high frequency noise. At high frequencies circuit may become unstable.</p>
<p>6</p>	<p>Procedure, Program, Activity, Algorithm, Pseudo Code</p>	<p>PROCEDURE</p> <p>Adder/Substractor</p> <ol style="list-style-type: none"> 1. Connect the circuit as shown in the diagram. 2. Apply the bias voltages of $\pm 12V$ to pin 7 and pin 4 of IC741 respectively. 3. Apply two different signals (DC/AC) to the inputs. 4. Vary the input voltages and note down the corresponding output at pin 6 of IC741 5. Notice that the output is equal to the sum/difference of the two inputs. <p>Integrator</p> <ol style="list-style-type: none"> 1. Connect the circuit as per the diagram shown in Fig6.3 2. Apply a square wave/sine input of 4V(p-p) at 1KHz 3. Observe the output at pin 6. 4. Draw input and output waveforms . <p>Differentiator</p> <ol style="list-style-type: none"> 1. Connect the circuit as per the diagram shown in Fig 6.4 2. Apply a square wave/sine input of 4V(p-p) at 1KHz

		3. Observe the output at pin 6 4. Draw the input and output waveforms .
7	Block, Circuit, Model Diagram, Reaction Equation, Expected Graph	CIRCUIT DIAGRAM Fig 6.4 Differentiator
8	Observation Table, Look-up Table, Output	
9	Sample Calculations	
10	Graphs, Outputs	
11	Results & Analysis	Designed and verified the operation of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator.
12	Application Areas	Summing amplifier is Used in audio mixer to add different signals with n equal gains. Instrumentaion amplifiers are used in data acquisition systems.
13	Remarks	
14	Faculty Signature with Date	

Experiment 07: Op – Amp Based First Order Butterworth (a) Low Pass (b) High Pass and (c)Band pass Filters

-	Experiment No.:	7	Marks		Date Planned		Date Conducted																																									
1	Title	Design and realize an op – amp based first order Butterworth (a) low pass (b) high pass and (c)band pass filters for a given cut off frequency/frequencies to verify the frequency response characteristic.																																														
2	Course Outcomes	Design and realize an op – amp based first order Butterworth (a) low pass (b) high pass and (c)band pass filters for a given cut off frequency/frequencies to verify the frequency response characteristic using lic hardware kit.																																														
3	Aim	To design and realize an op – amp based first order Butterworth (a) low pass (b) high pass and (c)band pass filters for a given cut off frequency/frequencies to verify the frequency response characteristic.																																														
4	Material Equipment Required	/	<table border="1"> <thead> <tr> <th>SI NO</th> <th>Name</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Regulated Dual Power Supply</td> <td>0-20V</td> <td>1</td> </tr> <tr> <td>2</td> <td>Resistors</td> <td>1.5KΩ(1),22KΩ(2),10KΩ(1)</td> <td>4</td> </tr> <tr> <td>3</td> <td>Capacitors</td> <td>0.1μF, 0.01μF</td> <td>2</td> </tr> <tr> <td>4</td> <td>CRO</td> <td>-</td> <td>1</td> </tr> <tr> <td>5</td> <td>Multimeter</td> <td>-</td> <td>1</td> </tr> <tr> <td>6</td> <td>ICμA741</td> <td>-</td> <td>1</td> </tr> <tr> <td>7</td> <td>Patch Chords</td> <td>-</td> <td></td> </tr> <tr> <td>8</td> <td>LIC Trainer Kit</td> <td>-</td> <td>1</td> </tr> <tr> <td>9</td> <td>Stepdown Transformer</td> <td></td> <td></td> </tr> </tbody> </table>						SI NO	Name	Range	Quantity	1	Regulated Dual Power Supply	0-20V	1	2	Resistors	1.5KΩ(1),22KΩ(2),10KΩ(1)	4	3	Capacitors	0.1μF, 0.01μF	2	4	CRO	-	1	5	Multimeter	-	1	6	ICμA741	-	1	7	Patch Chords	-		8	LIC Trainer Kit	-	1	9	Stepdown Transformer		
SI NO	Name	Range	Quantity																																													
1	Regulated Dual Power Supply	0-20V	1																																													
2	Resistors	1.5KΩ(1),22KΩ(2),10KΩ(1)	4																																													
3	Capacitors	0.1μF, 0.01μF	2																																													
4	CRO	-	1																																													
5	Multimeter	-	1																																													
6	ICμA741	-	1																																													
7	Patch Chords	-																																														
8	LIC Trainer Kit	-	1																																													
9	Stepdown Transformer																																															
5	Theory, Formula, Principle, Concept	<p>THEORY: Active Lpf : A filter circuit which allows only low frequency range up to a higher cut-off frequency f_H is called as Low Pass Filter. An active filter uses transistor and components such as resistor & capacitor for its design. An active filter offers the following advantages over a passive filter.</p> <ol style="list-style-type: none"> Gain & frequency adjustment flexibility. No loading problem because of high input impedance & low output impedance. 																																														

		<p>3. More economical because of variety of op-amps and absence of inductors. From the frequency response, when $f < f_H$; the gain is maximum A. When $f = f_H$; the gain is 70.7% of the maximum gain and when $f > f_H$; the gain drops or rolls off. The frequency range from 0 to f_H is called as Passband & f_H to is called as Stopband. Out of Butterworth, chebyshev & cauer filters, Butterworth filter is preferred because it has flat pass band as well as flat stop band (flat-flat) filter.</p> <p>Active Hpf: An active high pass filter is simply formed by interchanging the frequency determining resistor and capacitor in lowpass filter. A filter circuit which allows only high frequency range greater then a lower cut-off frequency f_L is called as HIGH PASS FILTER. From the frequency response, when $f < f_L$; the gain gradually increases from the lowest value. When $f = f_L$; the gain reaches 70.7% of the maximum gain A and when $f > f_L$, the gain is maximum A. The frequency range from 0 to f_L is called as Stopband & f_L to is called as Passband. (This is exactly opposite to active LPF)The order of the filter tells the roll-off rate at stop band. Order $n = 1$ indicates $-20\text{dB} / \text{dec}$ ($-6\text{dB} / \text{octave}$); Order $n = 2$ indicates $-40\text{dB} / \text{dec}$ & so on. Higher the order of the filter, better the quality will be & complex the circuit will be.</p> <p>Active Bandpass Filter: A filter which has a pass band between two cut-off frequencies f_H & f_L is called as Bandpass filter. Where $f_H > f_L$ BPF is basically of two types (i) Wide band pass filter. (ii) Narrow band pass filter. Based on figure of merit or quality factor Q, the types are classified as follows. If $Q < 10$, selectivity is poor & allows higher bandwidth & such BPF is called as wide BPF. If $Q > 10$, selective is more and allows only narrow bandwidth & such BPF is called as Narrow BPF. Relationship between Q & center frequency f_C is given as</p> <p>When frequency $f_L < f < f_H$ then gain is maximum. At $f < f_L$ the gain is gradually increasing (positive roll-off) from lower value & at $f > f_H$ the gain is gradually decreasing (Negative roll-off) & exactly when $f = f_L$ & $f = f_H$ the gain is 70.7% of maximum gain A.</p>
<p>6</p>	<p>Procedure, Program, Activity, Algorithm, Pseudo Code</p>	<p>PROCEDURE (LPF /HPF /BPF):</p> <ul style="list-style-type: none"> • 1) Do the connection as per the circuit diagram. • 2) Bias the op – amp with supply voltage of +12V and -12V. • 3) Apply a input sinusoidal signal of constant voltage to the non inverting terminal of the op-amp. • 4) Tabulate the o/p voltage V_o w.r.t. different values of input frequency. • 5) Calculate pass band gain and plot the graph of frequency V/S A_v and check the graph to get approximately the same characteristic as shown in the expected graph.
<p>7</p>	<p>Block, Circuit, Model Diagram, Reaction Equation, Expected Graph</p>	<p>CIRCUIT DIAGRAM</p> <p>Fig 7.1 Low Pass Filter</p> <p>Fig 7.2 High Pass Filter</p> <p>Fig 7.3 Band Pass Filter</p>

8	Observation Table, Look-up Table, Output	<p>OBSERVATION TABLE:</p> <p>For LPF $V_{in} = \text{-----}V$</p> <table border="1" style="width: 100%; border-collapse: collapse; margin-bottom: 20px;"> <thead> <tr> <th style="width: 25%;">I/P frequency, f(HZ)</th> <th style="width: 25%;">Output Voltage Vo </th> <th style="width: 25%;">Gain $A_f = V_o/V_{in}$</th> <th style="width: 25%;">Gain (dB) = $20\log V_o/V_{in}$</th> </tr> </thead> <tbody> <tr> <td style="height: 40px;"></td> <td></td> <td></td> <td></td> </tr> </tbody> </table> <p>For HPF $V_{in} = \text{-----}V$</p> <table border="1" style="width: 100%; border-collapse: collapse; margin-bottom: 20px;"> <thead> <tr> <th style="width: 25%;">I/P frequency, f(HZ)</th> <th style="width: 25%;">Output Voltage Vo </th> <th style="width: 25%;">Gain $A_f = V_o/V_{in}$</th> <th style="width: 25%;">Gain (dB) = $20\log V_o/V_{in}$</th> </tr> </thead> <tbody> <tr> <td style="height: 40px;"></td> <td></td> <td></td> <td></td> </tr> </tbody> </table> <p>For BPF $V_{in} = \text{-----}V$</p> <table border="1" style="width: 100%; border-collapse: collapse;"> <thead> <tr> <th style="width: 25%;">I/P frequency, f(HZ)</th> <th style="width: 25%;">Output Voltage Vo </th> <th style="width: 25%;">Gain $A_f = V_o/V_{in}$</th> <th style="width: 25%;">Gain (dB) = $20\log V_o/V_{in}$</th> </tr> </thead> <tbody> <tr> <td style="height: 40px;"></td> <td></td> <td></td> <td></td> </tr> </tbody> </table>	I/P frequency, f(HZ)	Output Voltage Vo	Gain $A_f = V_o/V_{in} $	Gain (dB) = $20\log V_o/V_{in} $					I/P frequency, f(HZ)	Output Voltage Vo	Gain $A_f = V_o/V_{in} $	Gain (dB) = $20\log V_o/V_{in} $					I/P frequency, f(HZ)	Output Voltage Vo	Gain $A_f = V_o/V_{in} $	Gain (dB) = $20\log V_o/V_{in} $				
I/P frequency, f(HZ)	Output Voltage Vo	Gain $A_f = V_o/V_{in} $	Gain (dB) = $20\log V_o/V_{in} $																							
I/P frequency, f(HZ)	Output Voltage Vo	Gain $A_f = V_o/V_{in} $	Gain (dB) = $20\log V_o/V_{in} $																							
I/P frequency, f(HZ)	Output Voltage Vo	Gain $A_f = V_o/V_{in} $	Gain (dB) = $20\log V_o/V_{in} $																							

					V_{in}^l	
<p>9</p>	<p>Sample Calculations</p>	<p>DESIGN: Design Problem : Design of LP/HP filters for cut – off frequency of $f_H = f_L = 1\text{kHz}$ and pass band gain = 2 1) Select the value of $C < 1 \mu\text{F}$. 2) Assume $C = 0.1 \mu\text{F}$. Calculate R from $f_H = f_L = 1 / 2\pi RC$ $R = 1 / 2\pi (f_H \text{ or } f_L) C$ $= 1 / 2\pi \times 1 \times 10^3 \times 0.1 \times 10^{-6}$ $R = 1.5\text{K}\Omega$ 3) Determine the value of R_1 and R_f from pass band gain of the filter $A_f = 1 + (R_f/R_1)$ $2 = 1 + (R_f/R_1)$ therefore $R_f = R_1$ to select $A_f = 2$ let $R_f = R_1 = 22\text{K}\Omega$ and $R_L = 10\text{K}\Omega$ 4) Calculate the practical gain in dB using $\text{Gain(dB)} = 20\log(V_o/V_{in})$. Theoretical gain given as $V_o/V_{in} = A_f / \sqrt{1+(f/f_H \text{ or } f_L)^2}$ $A_f = \text{Pass Band Gain}$ $f = \text{i/p frequency}$ $f_H = \text{upper cut off frequency of LPF}$ $f_L = \text{Lower cut off frequency of HPF}$ Design problem: Design a BPF to pass a band of 1KHZ to 10KHZ with a passband gain of 4. 1) Select the highest cut – off frequency of LPF as $f_H = 10\text{KHZ}$ and lowest cut-off frequency of HPF as $f_L = 1\text{KHZ}$. 2) Design the HPF first by taking $f_L = 1 \text{KHZ}$. Assume the value of $C < 1 \mu\text{F}$. Let $C_H = 0.1 \mu\text{F}$ 3) Calculate R_H from the expression $f_L = 1 / 2 \pi R_H C_H$ Therefore $R_H = 1 / 2 \pi f_L C_H$ $= 1 / 2 \times \pi \times 1 \times 10^3 \times 0.1 \times 10^{-6}$ $= 1.59$ $R_H = 1.5\text{K}\Omega$ (std) 4) Then design the LPF by taking $f_H = 10 \text{KHZ}$. Assume the value of $C < 1 \mu\text{F}$. Let $C_L = 0.01 \mu\text{F}$ 5) Calculate R_L from the expression $f_H = 1 / 2 \pi R_L C_L$ Therefore $R_L = 1 / 2\pi f_L C_L$</p>				

		<p> $= 1 / 2 \times \pi \times 10 \times 10^3 \times 0.01 \times 10^{-6}$ $= 1.59$ $R_L = 1.5 \text{K}\Omega$ (std) 6) Calculate the values of R_f and R_1 with the use of pass band gain. Overall pass band gain of BPF = $4 = 2(\text{HPF}) \times 2(\text{LPF})$ Therefore for both HPF and LPF , the value of $R_f = R_1$ to obtain an individual pass band gain of 2. $A_f = 1 + (R_f/R_1) = 2$ (for HPF) $A_f = 1 + (R_f/R_1) = 2$ (for LPF) Let $R_f = R_1 = 22 \text{K}\Omega$ 7) Q of the filters is calculated as $f_C / \text{BW} = f_C / (f_H - f_L)$ where $f_C = \sqrt{f_H f_L}$ is centre frequency $= \sqrt{10 \times 10^3 \times 1 \times 10^3}$ $= 3162.2 \text{HZ}$ $f_C = 3.16 \text{KHZ}$ 8) Cascade HPF and then LPF to form BPF. Calculate the practical gain in dB using $20 \log(V_O/V_{in})$ and theoretical gain as $V_O/V_{in} = A_f \frac{1}{\sqrt{1+(f/f_L)^2}} \times \frac{1}{\sqrt{1+(f/f_H)^2}}$ Where A_{ft} = total passband gain </p>
10	Graphs, Outputs	<p>EXPECTED GRAPH:</p>
11	Results & Analysis	<p>Design high pass filters for 1KHz cut off frequency to verify the frequency response characteristic and (c) band pass filters for 1KHz-10KHz cut off frequencies to verify the frequency response characteristic.</p>
12	Application Areas	<p>Active filters are used in communication systems for suppressing noise, in audio systems , biomedical instruments to interface psychological sensors with diagnostic equipments and data logging.</p>
13	Remarks	

14	Faculty Signature with Date	
----	-----------------------------	--

Experiment 08: Op – Amp Based Function Generator to Generate Sine, Square and Triangular Waves

-	Experiment No.:	3	Marks	Date Planned	Date Conducted																																								
1	Title	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency.																																											
2	Course Outcomes	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency using lic hardware kit.																																											
3	Aim	To design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency.																																											
4	Material Equipment Required	<table border="1"> <thead> <tr> <th>SI NO</th> <th>Name</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Regulated Dual Power Supply</td> <td>0-20V</td> <td>1</td> </tr> <tr> <td>2</td> <td>Resistors</td> <td>1.5KΩ(1),22KΩ(2),10KΩ(1)</td> <td>4</td> </tr> <tr> <td>3</td> <td>Capacitors</td> <td>0.1μF, 0.01μF</td> <td>2</td> </tr> <tr> <td>4</td> <td>CRO</td> <td>-</td> <td>1</td> </tr> <tr> <td>5</td> <td>Multimeter</td> <td>-</td> <td>1</td> </tr> <tr> <td>6</td> <td>ICμA741</td> <td>-</td> <td>1</td> </tr> <tr> <td>7</td> <td>Patch Chords</td> <td>-</td> <td></td> </tr> <tr> <td>8</td> <td>LIC Trainer Kit</td> <td>-</td> <td>1</td> </tr> <tr> <td>9</td> <td>Stepdown Transformer</td> <td></td> <td></td> </tr> </tbody> </table>				SI NO	Name	Range	Quantity	1	Regulated Dual Power Supply	0-20V	1	2	Resistors	1.5KΩ(1),22KΩ(2),10KΩ(1)	4	3	Capacitors	0.1μF, 0.01μF	2	4	CRO	-	1	5	Multimeter	-	1	6	ICμA741	-	1	7	Patch Chords	-		8	LIC Trainer Kit	-	1	9	Stepdown Transformer		
SI NO	Name	Range	Quantity																																										
1	Regulated Dual Power Supply	0-20V	1																																										
2	Resistors	1.5KΩ(1),22KΩ(2),10KΩ(1)	4																																										
3	Capacitors	0.1μF, 0.01μF	2																																										
4	CRO	-	1																																										
5	Multimeter	-	1																																										
6	ICμA741	-	1																																										
7	Patch Chords	-																																											
8	LIC Trainer Kit	-	1																																										
9	Stepdown Transformer																																												
5	Theory, Formula, Principle, Concept	<p>THEORY:</p> <p>Function generator generates waveforms such as sine, triangular, square waves and so on of different frequencies and amplitudes. The circuit shown in Fig 8.1 is a simple circuit which generates square waves and triangular waves simultaneously. Here the first section is a square wave generator and second section is an integrator. When square wave is given as input to integrator it produces triangular wave.</p>																																											
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<p>PROCEDURE:</p> <ol style="list-style-type: none"> 1.Connect the circuit as per the circuit diagram shown above. 2.Bias the op – amp with supply voltage of +12V and -12V 2.Obtain square wave at Vo1 and Triangular wave at Vo2 as shown in Fig 8.1. 3. Observe the output waveforms in CRO. 																																											
7	Block, Circuit, Model Diagram, Reaction Equation, Expected Graph	<p>CIRCUIT DIAGRAM:</p>																																											

		Fig 8.1 Function Generator
8	Observation Table, Look-up Table, Output	
9	Sample Calculations	<p>DESIGN : Let $V_{opp} = 7v$ and frequency of oscillation $f_0 = 2KHZ$. $V_{sat} = 12 - 1 = 11V$ $V_{opp} = 2 \times (R_2/R_3) \times V_{sat}$ $7 = 2 \times (R_2/R_3) \times 11$ $R_2/ R_3 = 7/ (2 \times 11)$ $= 0.318$ $R_3 = 3.14 \times R_2$ Let $R_2 = 10K\Omega$ $R_3 = 3.14 \times 10K\Omega$ $R_3 = 31.4K\Omega$ $= 33K\Omega$ (Standard value)</p> <p>Frequency of oscillation $f_0 = R_3 / 4 \times R_1 \times C_1 \times R_2$ Let $C_1 = 0.01\mu F$ $2 \times 10^3 = 33K\Omega / 4 \times R_1 \times 0.01 \times 10^{-6} \times 10 \times 10^3$ $R_1 = 41.25K\Omega$ $= 39K\Omega$ (Standard value)</p>
10	Graphs, Outputs	<p>WAVEFORM:</p> <p>(a) Output at V_{o1}</p> <p>(b) output at V_{o2}</p>
11	Results & Analysis	Designed and realized an op – amp based function generator to generate sine, square and triangular waves of 2KHZ frequency
12	Application Areas	Use in signal/function generator.
13	Remarks	
14	Faculty Signature with Date	

Experiment 09:R – 2R ladder DAC

-	Experiment No.:	9	Marks	Date Planned	Date Conducted
1	Title	Design and realization of R – 2R ladder DAC			
2	Course Outcomes	Design and realize of R – 2R ladder DAC using lic hardware kit.			

3	Aim	To design and realization of R – 2R ladder DAC																																								
4	Material Equipment Required	<table border="1"> <thead> <tr> <th>SI NO</th> <th>Name</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Regulated Dual Power Supply</td> <td>0-20V</td> <td>1</td> </tr> <tr> <td>2</td> <td>Resistors</td> <td>1.5KΩ(1),22KΩ(2),10KΩ(1)</td> <td>4</td> </tr> <tr> <td>3</td> <td>Capacitors</td> <td>0.1μF, 0.01μF</td> <td>2</td> </tr> <tr> <td>4</td> <td>CRO</td> <td>-</td> <td>1</td> </tr> <tr> <td>5</td> <td>Multimeter</td> <td>-</td> <td>1</td> </tr> <tr> <td>6</td> <td>ICμA741</td> <td>-</td> <td>1</td> </tr> <tr> <td>7</td> <td>Patch Chords</td> <td>-</td> <td></td> </tr> <tr> <td>8</td> <td>LIC Trainer Kit</td> <td>-</td> <td>1</td> </tr> <tr> <td>9</td> <td>Stepdown Transformer</td> <td></td> <td></td> </tr> </tbody> </table>	SI NO	Name	Range	Quantity	1	Regulated Dual Power Supply	0-20V	1	2	Resistors	1.5K Ω (1),22K Ω (2),10K Ω (1)	4	3	Capacitors	0.1 μ F, 0.01 μ F	2	4	CRO	-	1	5	Multimeter	-	1	6	IC μ A741	-	1	7	Patch Chords	-		8	LIC Trainer Kit	-	1	9	Stepdown Transformer		
SI NO	Name	Range	Quantity																																							
1	Regulated Dual Power Supply	0-20V	1																																							
2	Resistors	1.5K Ω (1),22K Ω (2),10K Ω (1)	4																																							
3	Capacitors	0.1 μ F, 0.01 μ F	2																																							
4	CRO	-	1																																							
5	Multimeter	-	1																																							
6	IC μ A741	-	1																																							
7	Patch Chords	-																																								
8	LIC Trainer Kit	-	1																																							
9	Stepdown Transformer																																									
5	Theory, Formula, Principle, Concept	<p>THEORY:</p> <p>Real world signals are analog. Digital systems that interface with the real world do so using analog-to-digital converters (ADC). Conversion back to analog is accomplished using digital-to- analogue converters (DAC). The R-2R ladder network is commonly used for Digital to Analog conversions.</p> <p>In basic N bit R-2R resistor ladder network the digital inputs or bits range from the most significant bit (MSB) to the least significant bit (LSB). The bits are switched between either 0V or VR and depending on the state and location of the bits Vo will vary between 0V and VR . The MSB causes the greatest change in output voltage and the LSB causes the smallest.</p> <p>The R-2R ladder is inexpensive and relatively easy to manufacture since only two resistor values are required. It is fast and has fixed output impedance R. In R-2R ladder type D to A converter, only two values of resistor is used (i.e.R and 2R). Hence it is suitable for integrated circuit fabrication. The typical values of R are from 2.5KΩ to 10KΩ. In this output voltage is a weighted sum of digital inputs. Since the resistive ladder is a linear network, the principle of super position can be used to find the total analog output voltage for a particular digital input by adding the output voltages caused by the individual digital inputs.The output voltage is linearly proportional to the digital input and the range can be adjusted by changing the reference voltage VR</p>																																								
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<p>PROCEDURE:</p> <ol style="list-style-type: none"> 1)Wire the R/2R ladder 4 bit DAC circuit . 2)Bias the op – amp with supply voltage of +12V and -12V 3) Reference voltage VR is set as 5V . 4) Find the output voltage Vo for different combinations of digital binary inputs from 0000 to 1111. 5)Compare the calculated values with observed values and plot DAC characteristics. 																																								
7	Block, Circuit, Model Diagram, Reaction Equation, Expected Graph	<p>CIRCUIT DIAGRAM:</p>																																								

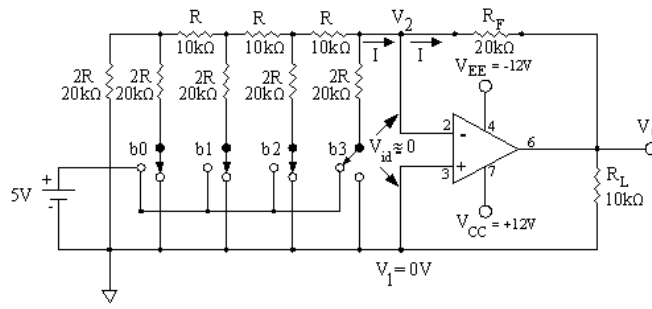


Fig 9.1 4 -

Ladder Digital To Analog Converter

Bit R- 2R

8 Observation Table, Look-up Output Table,

Decimal Value	Binary Input	Theoretical Value	Practical Value
0	0000	0	
1	0001	-0.625	
2	0010	-1.25	
3	0011	-1.875	
4	0100	-2.50	
5	0101	-3.125	
6	0110	-3.750	
7	0111	-4.375	
8	1000	-5	
9	1001	-5.625	
10	1010	-6.25	
11	1011	-6.875	
12	1100	-7.50	
13	1101	-8.125	
14	1110	-8.875	
15	1111	-9.375	

9 Sample Calculations

DESIGN:

For gain = $R_f / R = 2$
 $R_f = 2R = 20K\Omega$

$R_f = 2R$

Let $R = 10K\Omega$

then R_f

CALCULATIONS:

Output Voltage is given by

$$V_o = - (V_R / 16) * (R_f / R) * (b_0 + 2b_1 + 4b_2 + 8b_3)$$

where, $V_R = 5V$, b_3 (MSB bit) and b_0 (LSB bit) then
 Resolution = $FS / (2^n - 1)$, where n = no of digital inputs
 V_{FS} = Value of analog output when digital input is 1111.

		• Resolution = $0.625 = \text{Value of LSB bit.}$
10	Graphs, Outputs	
11	Results & Analysis	Designed and realized 4-bit R – 2R ladder DAC
12	Application Areas	DAC are used in data acquisition system.
13	Remarks	
14	Faculty Signature with Date	

Experiment 10: Two Bit Flash ADC.

-	Experiment No.:	10	Marks	Date Planned	Date Conducted	
1	Title	Realization of Two bit Flash ADC.				
2	Course Outcomes	Realize of Two bit Flash ADC using lic hardware kit.				
3	Aim	To realization of Two bit Flash ADC.				
4	Material Equipment Required	/	SI NO	Name	Range	Quantity
			1	Regulated Dual Power Supply	0-20V	1
			2	Resistors	1.5K Ω (1),22K Ω (2),10K Ω (1)	4
			3	Capacitors	0.1 μ F, 0.01 μ F	2
			4	CRO	-	1
			5	Multimeter	-	1
			6	IC μ A741	-	1
			7	Patch Chords	-	
			8	LIC Trainer Kit	-	1
			9	Stepdown Transformer		
5	Theory, Formula, Principle, Concept	<p>THEORY:</p> <p>Flash ADC is also called as parallel ADC. Its response is very fast. It converts analog signal into digital signal using parallel set of comparators. As its conversion time is very fast it is called as flash. ADC. Reference ladder (voltage divider) consists of $2N$ equal size resistors. N – bit flash ADC consist of parallel combination of $2N-1$ comparators. Outputs of all comparators are connected to an encoder.</p> <p>Analog voltage is applied to non inverting terminals of all comparators using a single line. Reference voltage is applied to inverting terminals of comparators using divider circuit. Each comparator produces digital output in the form of 1 or 0. If unknown analog voltage is greater than reference voltage comparator produces high logic. If analog voltage is less than reference voltage then comparator produces low logic i.e 0. Thus all parallel comparator produces digital representation of analog voltage in the form of zero and one. These outputs of comparator are then applied to the fast encoder. Encoder converts those zeros and ones into binary number and produces digital binary output.</p>				
6	Procedure,	PROCEDURE:				

Program, Activity, Algorithm, Pseudo Code

- 1) Do the connection as per the 2-bit flash ADC circuit.
- 2) Bias the op-amp with supply voltage of +12V and -12V
- 3) Reference voltage V_R is set as 3V.
- 4) Apply the analog input signal of $V_p = 3V$ from function generator to ADC. Check the digital output voltage V_o for different values of analog voltage values.

7 Block, Circuit, Model Diagram, Reaction Equation, Expected Graph

CIRCUIT DIAGRAM WITH SIMULATED OUTPUT:

8 Observation Table, Look-up Table, Output

ADC TABLE:

Analog Voltage in volts	Comparator Output			Digital(Encoder) Output	
	A	B	C	D1	D0
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	1	1	0
3	1	1	1	1	1

9 Sample Calculations

10	Graphs, Outputs	-
11	Results & Analysis	Realized Two bit Flash ADC.
12	Application Areas	<u>ADC</u> are used in data acquisition system.
13	Remarks	
14	Faculty Signature with Date	

Experiment 11: IC 555 timer Based Pulse Generator

-	Experiment No.:	3	Marks		Date Planned		Date Conducted																																									
1	Title	Design and verify an IC 555 timer based pulse generator for the specified pulse.																																														
2	Course Outcomes	Design and verify an IC 555 timer based pulse generator for the specified pulse using lic hardware kit.																																														
3	Aim	To design and verify an IC 555 timer based pulse generator for the specified pulse.																																														
4	Material Equipment Required	/	<table border="1"> <thead> <tr> <th>SI NO</th> <th>Name</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Regulated Dual Power Supply</td> <td>0-20V</td> <td>1</td> </tr> <tr> <td>2</td> <td>Resistors</td> <td>1,5KΩ(1),22KΩ(2),10KΩ(1)</td> <td>4</td> </tr> <tr> <td>3</td> <td>Capacitors</td> <td>0.1μF, 0.01μF</td> <td>2</td> </tr> <tr> <td>4</td> <td>CRO</td> <td>-</td> <td>1</td> </tr> <tr> <td>5</td> <td>Multimeter</td> <td>-</td> <td>1</td> </tr> <tr> <td>6</td> <td>ICμA741</td> <td>-</td> <td>1</td> </tr> <tr> <td>7</td> <td>Patch Chords</td> <td>-</td> <td></td> </tr> <tr> <td>8</td> <td>LIC Trainer Kit</td> <td>-</td> <td>1</td> </tr> <tr> <td>9</td> <td>Stepdown Transformer</td> <td></td> <td></td> </tr> </tbody> </table>						SI NO	Name	Range	Quantity	1	Regulated Dual Power Supply	0-20V	1	2	Resistors	1,5KΩ(1),22KΩ(2),10KΩ(1)	4	3	Capacitors	0.1μF, 0.01μF	2	4	CRO	-	1	5	Multimeter	-	1	6	ICμA741	-	1	7	Patch Chords	-		8	LIC Trainer Kit	-	1	9	Stepdown Transformer		
SI NO	Name	Range	Quantity																																													
1	Regulated Dual Power Supply	0-20V	1																																													
2	Resistors	1,5KΩ(1),22KΩ(2),10KΩ(1)	4																																													
3	Capacitors	0.1μF, 0.01μF	2																																													
4	CRO	-	1																																													
5	Multimeter	-	1																																													
6	ICμA741	-	1																																													
7	Patch Chords	-																																														
8	LIC Trainer Kit	-	1																																													
9	Stepdown Transformer																																															

5	Theory, Formula, Principle, Concept	<p>THEORY: An Astable Multivibrator or a Free Running Multivibrator is the multivibrator which has no stable states. Its output oscillates continuously between its two unstable states without the aid of external triggering. The time period of each states are determined by Resistor Capacitor (RC) time constant.</p> <p>Monostable Multivibrators or "One-Shot Multivibrators" as they are also called, are used to generate a single output pulse of a specified width, either "HIGH" or "LOW" when a suitable external trigger signal or pulse T is applied.</p>
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<p>PROCEDURE FOR ASTABLE MULTIVIBRATOR:</p> <p>Asymmetrical: Frequency 1 KHz with 0.75 duty cycle.</p> <ol style="list-style-type: none"> 1. Verify the components and patch chords whether they are in good condition. 2. Connect the Astable multivibrator circuit using IC 555 timer as shown in the ckt as per the design. 3. Switch on the DC power supply unit $V_{cc}=12V$. 4. Observer the output waveform at pin no 6 on CRO.(capacitor output) 5. Also observe the output waveform at pin no 3 on CRO.(Multivibrator output) 6. For the capacitor output at pin no 6 , measure the maximum and minimum voltage levels. Verify that $V_{UT} = 2/3V_{cc}$ and $V_{LT} = 1/3 V_{cc}$. 7. Compare the capacitor voltage V_c with output waveform V_o and note that capacitor charges and V_c rises exponentially when output is high. The capacitor C discharges through R_B and the diode and V_c falls exponentially when output is low. 8. Verify the designed value of frequency matches with practical value. <p>Symmetrical: Frequency 1 KHz with 0.50 duty cycle</p> <ol style="list-style-type: none"> 1. Verify the components and patch chords whether they are in good condition. 2. Connect the Astable multivibrator circuit using IC 555 timer as shown in the ckt as per the design. 3. Switch on the DC power supply unit $V_{cc}=12V$. 4. Observer the output waveform at pin no 6 on CRO.(capacitor output) 5. Also observe the output waveform at pin no 3 on CRO.(Multivibrator output) 6. For the capacitor output at pin no 6 , measure the maximum and minimum voltage levels. Verify that $V_{UT} = 2/3V_{cc}$ and $V_{LT} = 1/3 V_{cc}$. 7. Compare the capacitor voltage V_c with output waveform V_o and note that capacitor charges and V_c rises exponentially when output is high. The capacitor C discharges through R_B and the diode and V_c falls exponentially when output is low. 8. Verify the designed value of frequency matches with practical valu <p>PROCEDURE FOR MONOSTABLE MULTIVIBRATOR:</p> <ol style="list-style-type: none"> 1. Verify all the components and patch chords. 2. Connect the Monostable Multivibrator circuit using IC 555-timer as like shown in ckt. 3. Switch on the DC power supply unit $V_{cc}=+5V$ and observe the output waveform at pin no 3 on CRO. Adjust the input pulse amplitude to the designed value and observe the output waveform at pin no 3 on CRO. Measure the output pulse width and compare it with the theoretical value. 4. Adjust the input pulse amplitude to the designed value and observe the output waveform at pin no 3 on CRO. Measure the output pulse width and compare it with the theoretical value. 5. Observe the output waveform at pin no 3 on CRO. Measure the output pulse width and compare it with the theoretical value. 6. Measure the output pulse width and compare it with the theoretical value. 7. Verify whether the output pulse width is equal to the theoretical value. 8. Observe the output waveform at pin no 3 on CRO. Measure the output pulse width and compare it with the theoretical value. <p>Fig 11.2 Symmetric Multivibrator</p> <p>Fig 11.3 Asymmetric Multivibrator</p> <p>Fig 11.1 Monostable Multivibrator</p>
7	Block, Model, Circuit, Diagram,	<p>eriodic input trigger and adjust the input ss the capacitor 'C'. asure its higher and at it is equal to the ractical values and</p> <p>..ll rights reserved.</p>

	Reaction Equation, Expected Graph	
8	Observation Table, Look-up Table, Output	
9	Sample Calculations	<p>DESIGN: Astable Multivibrator: Symmetric: For frequency of 1KHZ and 50% duty cycle. $F = 1\text{KHZ}$ so $T = 1 / F = 1 / (1000) = 1\text{msec}$ $T = T_H + T_L = 0.5\text{msec} + 0.5\text{msec}$ Where T = total period of the cycle T_H = upper threshold time T_L = lower threshold time</p> <p>$T_H = T_L = 0.5\text{msec}$ $R_A = R_B = R$ $T_H = T_L = 0.693RC = 0.5\text{msec}$ Therefore $R = 0.5\text{msec} / (0.693C)$ Let $C = 0.1\mu\text{F}$ $R = 0.5 \times 10^{-3} / (0.693 \times 0.1 \times 10^{-6})$ $= 7.22\text{K}\Omega$ $= 6.8\text{K}\Omega$ (std) So $R_A = R_B = 6.8\text{K}\Omega$</p> <p>Asymmetric : For frequency of 1KHZ and duty cycle of 75%. $T = 1 / F = 1 / 1000 = 1\text{msec}$ Therefore $T = T_H + T_L = 0.75\text{msec} + 0.25\text{msec}$ $T_H = 0.693(R_A + R_B) C = 0.75\text{msec}$ $R_A + R_B = T_H / (0.693 C)$ Let $C = 0.1\mu\text{F}$ $= 0.75 \times 10^{-3} / (0.693 \times 0.1 \times 10^{-6})$ $R_A + R_B = 10.82\text{K}\Omega$</p> <p>$T_L = 0.693 R_B C = 0.25\text{msec}$ $R_B = T_L / (0.693C)$ Let $C = 0.1\mu\text{F}$ $= 0.25 \times 10^{-3} / (0.693 \times 0.1 \times 10^{-6})$ $= 3.6\text{K}\Omega$ $R_B = 3.3\text{K}\Omega$ (std)</p> <p>W.K.T $R_A + R_B = 10.82\text{K}\Omega$ Therefore $R_A = 10.82\text{K}\Omega - R_B$ $= 10.82\text{K}\Omega - 3.3\text{K}\Omega$ $= 7.49\text{K}\Omega$ $R_A = 6.8\text{K}\Omega$ (std)</p> <p>Monostable:</p>

		<p>For time delay of 1msec or frequency of 1KHZ</p> $T = 1.1RC$ <p>Let $C = 0.1\mu F$</p> $R = T / (1.1C) = 1 \times 10^{-3} / (1.1 \times 0.1 \times 10^{-6})$ $= 9.09K\Omega$ $= 10K\Omega \text{ (std)}$
10	Graphs, Outputs	<div style="display: flex; justify-content: space-around;"> <div style="text-align: center;"> <p>Symmetric Multivibrator</p> </div> <div style="text-align: center;"> <p>Asymmetric Multivibrator</p> </div> </div> <div style="text-align: center; margin-top: 20px;"> <p>Monostable Multivibrator</p> </div>
11	Results & Analysis	<p>Designed an</p> <p>a) Astable Multivibrator using IC 555 timer to generate a clock signal of</p> <p>i) Frequency 1 KHz with 0.75 duty cycle. (Asymmetrical) ii) Frequency 1 KHz with 0.50 duty cycle. (Symmetrical)</p> <p>b) To design a Monostable Multivibrator using IC 555 (timer).</p>
12	Application Areas	Use in frequency divider, pulse width modulation ,linear ramp generator and voltage controlled oscillator.
13	Remarks	
14	Faculty Signature with Date	

Experiment 12: Fixed Voltage Power Supply (voltage regulator) using IC Regulators 78 Series and 79 Series.

-	Experiment No.:	3	Marks	Date Planned	Date Conducted												
1	Title	Designing of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series.															
2	Course Outcomes	Design of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series using lic hardware kit.															
3	Aim	To designing of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series.															
4	Material Equipment Required	/	<table border="1" style="width: 100%;"> <thead> <tr> <th>SI NO</th> <th>Name</th> <th>Range</th> <th>Quantity</th> </tr> </thead> <tbody> <tr> <td>1</td> <td>Regulated Dual Power Supply</td> <td>0-20V</td> <td>1</td> </tr> <tr> <td>2</td> <td>Resistors</td> <td>1.5KΩ(1), 22KΩ(2)</td> <td>4</td> </tr> </tbody> </table>			SI NO	Name	Range	Quantity	1	Regulated Dual Power Supply	0-20V	1	2	Resistors	1.5KΩ(1), 22KΩ(2)	4
SI NO	Name	Range	Quantity														
1	Regulated Dual Power Supply	0-20V	1														
2	Resistors	1.5KΩ(1), 22KΩ(2)	4														

),10KΩ(1)	
		3	Capacitors	0.1μF, 0.01μF	2
		4	CRO	-	1
		5	Multimeter	-	1
		6	ICμA741	-	1
		7	Patch Chords	-	
		8	LIC Trainer Kit	-	1
		9	Stepdown Transformer		

5 Theory, Formula, Principle, Concept


THEORY:
 A voltage regulator is a circuit that supplies a constant voltage regardless of changes in load current and input voltage. IC voltage regulators are versatile, relatively inexpensive and are available with features such as programmable output, current/voltage boosting, internal short circuit current limiting, thermal shunt down and floating operation for high voltage applications.

The 78XX series consists of three-terminal positive voltage regulators with seven voltage options. These IC's are designed as fixed voltage regulators and with adequate heat sinking can deliver output currents in excess of 1A.

The 79XX series of fixed output voltage regulators are complements to the 78XX series devices. These negative regulators are available in same seven voltage options. Typical performance parameters for voltage regulators are line regulation, load regulation, temperature stability and ripple rejection.

6 Procedure, Program, Activity, Algorithm, Pseudo Code

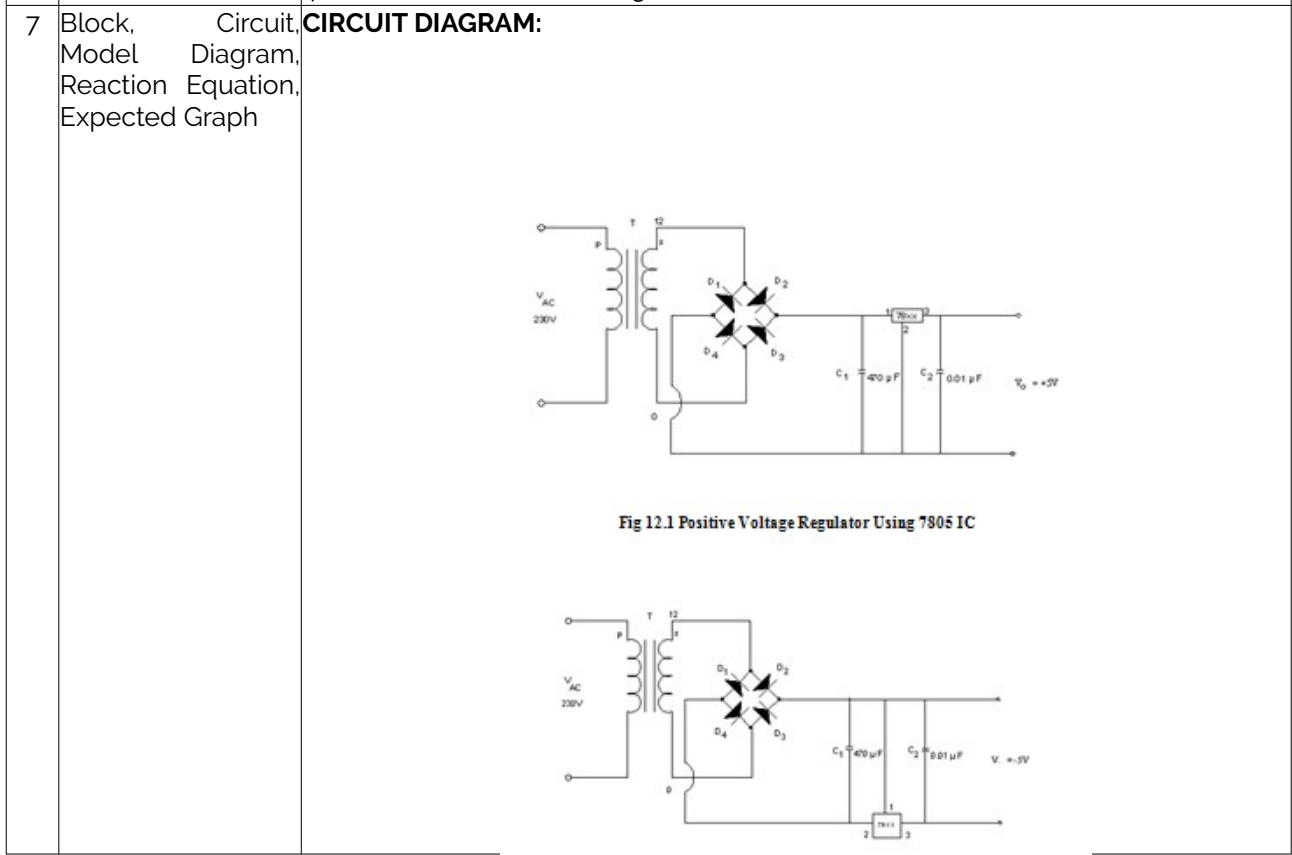PROCEDURE:
 1)Do the connection as per the circuit diagram.
 2)Vary the load resistance. But start applying from 100Ω.
 3)Note down the current and Vo for different values of RL
 4)Check that Vo should be 5V for different values of RL.



8	Observation Table, Look-up Table, Output	<p>For 7805 Regulator</p> <table border="1"> <thead> <tr> <th>Load Resistance(RL) in Ω</th> <th>Load Current in mA</th> <th>Output voltage in volts</th> </tr> </thead> <tbody> <tr><td>100</td><td></td><td></td></tr> <tr><td>200</td><td></td><td></td></tr> <tr><td>300</td><td></td><td></td></tr> <tr><td>400</td><td></td><td></td></tr> <tr><td>500</td><td></td><td></td></tr> <tr><td>600</td><td></td><td></td></tr> <tr><td>700</td><td></td><td></td></tr> <tr><td>800</td><td></td><td></td></tr> <tr><td>900</td><td></td><td></td></tr> <tr><td>1000</td><td></td><td></td></tr> </tbody> </table> <p>For 7905 Regulator</p> <table border="1"> <thead> <tr> <th>Load Resistance(RL) in Ω</th> <th>Load Current in mA</th> <th>Output voltage in volts</th> </tr> </thead> <tbody> <tr><td>100</td><td></td><td></td></tr> <tr><td>200</td><td></td><td></td></tr> <tr><td>300</td><td></td><td></td></tr> <tr><td>400</td><td></td><td></td></tr> <tr><td>500</td><td></td><td></td></tr> <tr><td>600</td><td></td><td></td></tr> <tr><td>700</td><td></td><td></td></tr> <tr><td>800</td><td></td><td></td></tr> <tr><td>900</td><td></td><td></td></tr> <tr><td>1000</td><td></td><td></td></tr> </tbody> </table>	Load Resistance(RL) in Ω	Load Current in mA	Output voltage in volts	100			200			300			400			500			600			700			800			900			1000			Load Resistance(RL) in Ω	Load Current in mA	Output voltage in volts	100			200			300			400			500			600			700			800			900			1000		
Load Resistance(RL) in Ω	Load Current in mA	Output voltage in volts																																																																		
100																																																																				
200																																																																				
300																																																																				
400																																																																				
500																																																																				
600																																																																				
700																																																																				
800																																																																				
900																																																																				
1000																																																																				
Load Resistance(RL) in Ω	Load Current in mA	Output voltage in volts																																																																		
100																																																																				
200																																																																				
300																																																																				
400																																																																				
500																																																																				
600																																																																				
700																																																																				
800																																																																				
900																																																																				
1000																																																																				
9	Sample Calculations	<p>DESIGN: $V_{inrms} = 12V$ $V_{odc} = 2V_m/\pi = 10.8v = 10v$ $I_{odc} = 100mA$ $R_L (min) = V_{odc}/I_{odc} = 100\Omega$ Let $R_f = 10\Omega$ $Ripple = \gamma = V_{orms} / V_{odc} = 0.48$ Let $\gamma = 6\% = 0.06$, $F = 50HZ$ and $R_L = 100 \Omega$ WKT $\gamma = 1/4\sqrt{3} F C_1 R_L$, $C_1 = 470\mu F$ and let $C_2 = 0.01\mu F$</p>																																																																		
10	Graphs, Outputs																																																																			
11	Results & Analysis	Designed and verified fixed voltage power supply (voltage regulator) using IC regulators 7805 for +5V and 7905 for -5V.																																																																		

12	Application Areas	Regulators are used in developing regulated DC power supply.
13	Remarks	
14	Faculty Signature with Date	

F. Content to Experiment Outcomes

1. TLPA Parameters

Table 1: TLPA – Example Course

Expt-#	Course Content or Syllabus (Split module content into 2 parts which have similar concepts)	Content Teaching Hours	Blooms' Learning Levels for Content	Final Blooms' Level	Identified Action Verbs for Learning	Instruction Methods for Learning	Assessment Methods to Measure Learning
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>E</i>	<i>F</i>	<i>G</i>	<i>H</i>
1	Design and verify a precision full wave rectifier. Determine the performance parameters.	3	L4	L4	Analyze	Experiment	Internal Assessment Test
2	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non - inverting configuration for a given gain.	3	L4	L4	Analyze	Experiment	Internal Assessment Test
3	Design and verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency.	3	L4	L4	Analyze	Experiment	Internal Assessment Test
4	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP).	3	L4	L4	Analyze	Experiment	Internal Assessment Test
5	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector.	3	L3	L3	Analyze	Experiment	Internal Assessment Test
6	Design and verify the operation's of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator.	3	L4	L4	Analyze	Experiment	Internal Assessment Test
7	Design and realize an op – amp based first order Butterworth (a) Low pass (b) High pass and (c) Band pass filters for a given cut off	3	L4	L4	Analyze	Experiment	Internal Assessment Test

	frequency frequencies to verify the frequency response characteristic.							
8	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency.	3	L4	L4	Analyze	Experiment	Internal Assessment Test	
9	Design and realization of R – 2R ladder DAC	3	L4	L4	Analyze	Experiment	Internal Assessment Test	
10	Realization of Two bit Flash ADC.	3	L3	L3	Analyze	Experiment	Internal Assessment Test	
11	Design and verify an IC 555 timer based pulse generator for the specified pulse.	3	L4	L4	Analyze	Experiment	Internal Assessment Test	
12	Designing of Fixed voltage power supply (voltage regulator) using IC regulators 78 series and 79 series.	3	L4	L4	Analyze	Experiment	Internal Assessment Test	

2. Concepts and Outcomes:

Table 2: Concept to Outcome – Example Course

Expt - #	Learning or Outcome from study of the Content or Syllabus	Identified Concepts from Content	Final Concept	Concept Justification (What all Learning Happened from the study of Content / Syllabus. A short word for learning or outcome)	CO Components (1.Action Verb, 2.Knowledge, 3.Condition / Methodology, 4.Benchmark)	Course Outcome Student Should be able to ...
A	I	J	K	L	M	N
1	Design and verify a precision full wave rectifier. Determine the performance parameters.	Rectification	Rectification	Determination of efficiency of designed precision full wave rectifier for given input and output signal amplitude.	1.Design and verify 2.OP-Amp as a precision full wave rectifier 3.using lic hardware kit.	Design and verify OP-Amp as a precision full wave rectifier using lic hardware kit.
1	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non - inverting configuration for a given gain.	Frequency Response	Frequency Response	Designing of inverting and non - inverting amplifier using op amp for a given gain. Analysis of frequency response of inverting and non inverting amplifier.	1.Design and realize 2.analysis of the frequency response of an op – amp amplifier under inverting and non - inverting configuration for a given gain 3.using lic hardware kit.	Design and realize to analyse the frequency response of an op – amp amplifier under inverting and non - inverting configuration for a given gain using lic hardware kit.
2	Design and	Sinosoidal	Sinosoidal	Designing and	1.Design and verify	Design and verify the output

	verify the output waveform of an op – amp RC phase shift oscillator for a desired frequency.	signal Generation	signal Generation	verifying the output of an op amp RC phase shift oscillator for a given frequency.	2.the output waveform of an op – amp RC phase shift oscillator for a desired frequency 3.using lic hardware kit.	waveform of an op – amp RC phase shift oscillator for a desired frequency using lic hardware kit.
2	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP).	Square/ Rectangular Wave Generation	Square/ Rectangular Wave Generation	Generation of Square/Rectangular wave for a given UTP and LTP of Schmitt trigger circuit using an op – amp .	1.Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP) 3.using lic hardware kit.	Design and realize Schmitt trigger circuit using an op – amp for desired upper trip point (UTP) and lower trip point (LTP) using lic hardware kit.
3	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector.	Voltage Comparison	Voltage Comparison	Generating square wave by comparing signal with given Vref using voltage comparator or ZCD.	1.Verify t 2. operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector 3.using lic hardware kit.	Verify the operation of an op – amp as (a) voltage comparator circuit and (b) zero crossing detector using lic hardware kit.
3	Design and verify the operation's of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator .	Airthmatic Operation	Airthmatic Operation	Performing arithmetic operations, using op amp, such as addition, subtraction, integration and differentiation.	1.Design and verify 2. the operation's of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator 3.using lic hardware kit.	Design and verify the operation's of op – amp as an (a) adder (b) subtractor (c) integrator and (d) differentiator using lic hardware kit.
4	Design and realize an op – amp based first order Butterworth (a) Low pass (b) High pass and (c) Band pass filters for a given cut off frequency frequencies to verify the frequency response	Active filtration	Active filtration	Frequency response of designed LPF,HPF AND BPF for given cut off frequency.	1.Design and realize 2.op – amp based first order Butterworth (a) Low pass (b) High pass and (c) Band pass filters for a given cut off frequency frequencies to verify the frequency response characteristic 3.using lic hardware kit.	Design and realize an op – amp based first order Butterworth (a) Low pass (b) High pass and (c) Band pass filters for a given cut off frequency frequencies to verify the frequency response characteristic using lic hardware kit.

	characteristic.					
4	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency.	Different Signal Generation	Different Signal Generation	Generation of square, triangular and sin wave for a given frequency using op amp.	1.Design and realize a function generator to generate sine, square and triangular waves of desired frequency 3.using lic hardware kit.	Design and realize an op – amp based function generator to generate sine, square and triangular waves of desired frequency using lic hardware kit.
5	Design and realization of R – 2R ladder DAC	Digital to Analog Conversion	Digital to Analog Conversion	Design and verification of R-2R ladder DAC for given gain.	1.Design and realize R – 2R ladder DAC 3.using lic hardware kit.	Design and realize of R – 2R ladder DAC using lic hardware kit.
5	Realization of Two bit Flash ADC.	Analog to Digital Conversion	Analog to Digital Conversion	Verification of 2 bit flash ADC	1.Realize 2.Two bit Flash ADC 3.using lic hardware kit.	Realize of Two bit Flash ADC using lic hardware kit.
	Design and verify an IC 555 timer based pulse generator for the specified pulse.	Pulse Generation	Pulse Generation	Square wave trigger pulse generation for given frequency using 555 timer.	1.Design and verify IC 555 timer based pulse generator for the specified pulse 3. using lic hardware kit.	Design and verify an IC 555 timer based pulse generator for the specified pulse using lic hardware kit.

