

Ref No:

Sri Krishna Institute of Technology, Bengaluru-560090



## COURSE PLAN

Academic Year - 2019-2020

Academic Evaluation and Monitoring Cell

Program:	BE- Electrical and Electronics Engineering
Semester:	5
Course Code:	17EEL58
Course Title:	Power Electronics
Credit/L-T-P:	3/0-1-2
Total Contact Hours:	36
Course Plan Author:	Chaitra A S

#29, Hesaragatta Main Road, Chimney Hills  
 Chikkabanavara Post Bengaluru – 560090, Karnataka, India  
 Phone / Fax :080-23721477/28392221/23721315  
 Web: [www,skit.org](http://www,skit.org), e-mail:

## Table of Contents

<b>A. LABORATORY INFORMATION.....</b>	<b>4</b>
1. Laboratory Overview.....	4
2. Laboratory Content.....	4
3. Laboratory Material.....	5
4. Laboratory Prerequisites.....	5
5. Content for Placement, Profession, HE and GATE.....	5
<b>B. Laboratory Instructions.....</b>	<b>6</b>
1. General Instructions.....	6
2. Laboratory Specific Instructions.....	6
<b>C. OBE PARAMETERS.....</b>	<b>6</b>
1. Laboratory Outcomes.....	6
2. Laboratory Applications.....	7
3. Mapping And Justification.....	8
4. Articulation Matrix.....	8
5. Curricular Gap and Experiments.....	9
6. Experiments Beyond Syllabus.....	9
<b>D. COURSE ASSESSMENT.....</b>	<b>10</b>
1. Laboratory Coverage.....	10
2. Continuous Internal Assessment (CIA).....	10
<b>E. EXPERIMENTS.....</b>	<b>11</b>
Experiment 01 : Structure of C program.....	11
Experiment 02 : Keywords and identifiers.....	12
Experiment 03 : .....	13
Experiment 04 : .....	13
<b>F. Content to Experiment Outcomes.....</b>	<b>14</b>
1. TLPA Parameters.....	14
2. Concepts and Outcomes.....	15

## INSTRUCTIONS TO TEACHERS

- Classroom / Lab activity shall be started after taking attendance.
- Attendance shall only be signed in the classroom by students.
- Three hours attendance should be given to each Lab.
- Use only Blue or Black Pen to fill the attendance.
- Attendance shall be updated on-line & status discussed in DUGC.
- No attendance should be added to late comers.
- Modification of any attendance, over writings, etc is strictly prohibited.
- Updated register is to be brought to every academic review meeting as per the COE.

## 17EEL58 : POWER ELECTRONICS LAB

### A. LABORATORY INFORMATION

#### 1. Lab Overview

Degree:	B.E	Program:	EE
Year / Semester :	3 / 5	Academic Year:	2019
Course Title:	Power Electronics Lab	Course Code:	17EEL58
Credit / L-T-P:	3 / 0-1-2	SEE Duration:	180 Minutes
Total Contact Hours:	36 Hrs	SEE Marks:	60 Marks
CIA Marks:	40	Assignment	1 / Module
Course Plan Author:	Chaitra A S	Sign	Dt :
Checked By:		Sign	Dt :

#### 2. Lab Content

Unit	Title of the Experiments	Lab Hours	Concept	Blooms Level
1	Static Characteristics of SCR.	3	Performance of SCR	L3 Apply
2	Static Characteristics of MOSFET and IGBT	3	Performance of MOSFET & IGBT	L3 Apply
3	Characteristic of TRIAC	3	Performance of TRIAC	L3 Apply
4	SCR turn on circuit using synchronized UJT relaxation oscillator	3	UJT Triggering method	L3 Apply
5	SCR digital triggering circuit for a single phase-controlled rectifier and ac voltage regulator.	3	Digital Triggering Method	L4 Analyze
6	Single phase controlled full wave rectifier with R and R -L loads.	3	Rectification	L4 Analyze
7	AC voltage controller using TRIAC and DIAC combination connected to R and RL loads.	3	Voltage Control	L4 Analyze
8	Speed control of dc motor using single semi converter.	3	Speed Control	L4 Analyze
9	Speed control of stepper motor.	3	Speed Control	L5 Evaluate
10	Speed control of universal motor using ac voltage regulator	3	Speed Control	L4 Analyze
11	Speed control of a separately excited D.C. Motor using an IGBT or MOSFET chopper.	3	Speed Control	L4 Analyze

12	Design of Snubber circuit.	3	Snubber Protection	L5 Evaluate3
----	----------------------------	---	--------------------	--------------

### 3. Lab Material

Unit	Details	Available
1	Text books	
	Power Electronics: Circuits Devices and Applications BY Mohammad H Rashid, Pearson 4th Edition, 2014.	In Lib
2	Reference books	
1.	Power Electronics: Converters, Applications and Design Ned Mohan et al Wiley 3rd Edition, 2014	In dept
2.	Power Electronics BY Daniel W Hart, McGraw Hill, 1 st Edition, 2011	
3	Elements of Power Electronics, Philip T Krein, Oxford, Indian Edition, 2008	
3	Others (Web, Video, Simulation, Notes etc.)	Not Available

### 4. Lab Prerequisites:

-	-	Base Course:	-	-	
SNo	Course Code	Course Name	Topic / Description	Sem	Remarks
1	15ELN15	Basic Electronics	1. Knowledge on Basic working	2	-
2	15EE34	Analog Electronic Circuits	FET, MOSFET Construction, working, Characteristics	3	-

Note: If prerequisites are not taught earlier, GAP in curriculum needs to be addressed. Include in Remarks and implement in B.5.

### 5. General Instructions

SNo	Instructions	Remarks
1	Keep the lab neatly. Maintain silence.	
2	Maintain your lab observation and lab manual.	
3	Prepare your experiment in well advance.	
4	Check the power supply before use.	
5	Maintain discipline in the lab.	
6	After completion of your experiment switch off the power supply.	
7	Observation book and Lab record are compulsory.	
8	Students should report to the concerned lab as per the time table.	
9	After completion of the experiment, certification of the concerned staff in-charge in the observation book is necessary.	
10	Student should bring a notebook of 100 pages and should enter the readings /observations into the notebook while performing the experiment.	

### 6. Lab Specific Instructions

SNo	Specific Instructions	Remarks
1	Check for all the connections of the circuit and scope connections before powering the circuit, to avoid shorting or any ground looping, that may lead to electrical shocks or damage of equipment	

2	Check any connections for shorting two different voltage levels	
3	Check if you have connected load at the output	
4	Double check your wiring and circuit connections	
5	Apply low voltages or low power to check proper functionality of circuits while switching ON the circuit.	
6	Once functionality is proven, increase voltages or power, stopping at frequent levels to check for proper functioning of circuit or for any components is hot or for any electrical noise that can affect the circuit's operation.	
7	Reduce the voltage or power slowly till it comes to zero.	
8	Switch of all the power supplies and remove the power supply connections.	
9	Avoid using long wires, that may get in your way while making adjustments or changing leads.	
10	Keep high voltage parts and connections out of the way from accidental touching and from any contacts to test equipment or any parts, connected to other voltage levels	

## B. OBE PARAMETERS

### 1. Lab / Course Outcomes

#	COs	Teach. Hours	Concept	Instr Method	Assessment Method	Blooms' Level
1	Obtain the static characteristic of SCR and their performance in terms of voltage & current.	10	Performance of SCR	Demonstrate	Unit Test, Viva Voce	L3
2	Compute static characteristics of MOSFET & IGBT and obtain their performance in terms of voltage & current.	06	Performance of MOSFET & IGBT	Demonstrate	Assignment	L3
3	Compute static characteristics of TRIAC and obtain their performance in terms of voltage & current.	07	Performance of TRIAC	Demonstrate	Assignment and unit Test	L3
4	To generate triggering pulses using UJT relaxation oscillator.	03	UJT Triggering method	Demonstrate	Assignment	L3
5	Generator triggering pulses using SCR digital trigger circuit using single phase controlled rectifier.	03	Digital Triggering Method	Demonstrate	Unit test	L4
6	Analyze the performance of a single phase full wave controlled rectified connected to R & RL load.	03	Rectification	Demonstrate	Assignment	L4
7	Analyze the performance of AC voltage controller applied to R & RL load using TRIAC and DIAC.	03	Voltage Control	Demonstrate	Assignment and unit Test	L4
8	Control the speed of DC motor using semi converter by varying firing angle.	03	Speed Control	Demonstrate	Assignment Viva Voce	L4
9	Control the speed of stepper motor.	03	Speed Control	Demonstrate	Assignment Viva Voce	L5
10	Control the speed of universal motor using controlled rectifier.	03	Speed Control	Demonstrate	Assignment Viva Voce	L4
11	Control the speed of a separately excited DC motor using MOSFET chopper by	03	Speed Control	Demonstrate	Assignment	L4

	varying duty cycle of the thyristor.					
12	Design the snubber circuit for the protection of power circuit from faults.	03	Snubber Protection	Demonstrate	Assignment Unit Test	L5
-	<b>Total</b>	<b>36</b>	-	-	-	-

Note: Identify a max of 2 Concepts per unit. Write 1 CO per concept.

## 2. Lab Applications

SNo	Application Area	CO	Level
1	SCR are used in Industrial application such as induction heating, dielectric heating and lamp dimming.	CO1	L3
2	SCR are used in static AC /DC circuit breakers, control rectifiers, tap changers	CO1	L3
3	Transistors are used in low power logic gates, DC motor drives, AC motor drives	CO2	L3
4	Transistors are used in isolation circuit such as opto-couplers and pulse transformers.	CO2	L3
5	TRIAC's are used in AC switches, starter circuit for lamps.	CO3	L3
6	UJT is used as a triggering device for SCR's, sawtooth generators, phase control and timing circuits.	CO4	L3
7	AC voltage controllers are used in cyclo converters, matrix converters, Electric welding.	CO5	L4
8	Control rectifiers are used in speed control of DC motor, Universal motors, lamp dimming.	CO6	L4
9	AC voltage controllers are used in power generation, power transmission, electric heating, induction heating.	CO7	L5
10	Control rectifiers are used in speed control of DC motor, Universal motors, lamp dimming.	CO8	L4
11	Stepper motors are used for precise positioning with a motor such as hard disc drives, robotics, antennas, telescopes etc	CO9	L4
12	Universal motors are used in portable power tools and equipments, house hold applications.	CO10	L4
13	Choppers are used in railway traction, battery charges, switched capacitance filters, variable frequency drives, class D electronic amplifiers, battery operated electric cars.	CO11	L4
14	Snubber circuits are used across the relays and switches to prevent arcing.	CO12	L5

Note: Write 1 or 2 applications per CO.

## 3. Articulation Matrix

### (CO – PO MAPPING)

#	Course Outcomes COs	Program Outcomes												Level		
		PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12			
15EEL58.1	Obtain the static characteristic of SCR and their performance in terms of voltage & current.	2.5	2.5													L3
15EEL58.2	Compute static characteristics of MOSFET & IGBT and obtain their performance in terms of voltage & current.	2.5	2.5													L3
15EEL58.3	Compute static characteristics of	2.5	2.5													L3

	TRIAC and obtain their performance in terms of voltage & current.													
15EEL58.4	To generate triggering pulses using UJT relaxation oscillator.	2.5	2.5							2.5				L3
15EEL58.5	Generator triggering pulses using SCR digital trigger circuit using single phase control rectifier.	2.5	2.5							2.5				L4
15EEL58.6	Analyze the performance of a single phase full wave controlled rectified connected to R & RL load.	2.5	2.5							2.5				L4
15EEL58.7	Analyze the performance of AC voltage controller applied to R & RL load using TRIAC and DIAC.	2.5	2.5							2.5				L4
15EEL58.8	Control the speed of DC motor using semi converter by varying firing angle.	2.5	2.5							2.5				L4
15EEL58.9	Control the speed of stepper motor.	2.5	2.5							2.5				L5
15EEL58.10	Control the speed of universal motor using controlled rectifier.	2.5	2.5							2.5				L4
15EEL58.11	Control the speed of a separately excited DC motor using MOSFET chopper by varying duty cycle of the thyristor.	2.5	2.5							2.5				L4
15EEL58.12	Design the snubber circuit for the protection of power circuit from faults.	2.5	2.5	2.5										L5
<b>15EEL58.</b>	Average													

Note: Mention the mapping strength as 1, 2, or 3

#### 4. Mapping Justification

Mapping		Mapping Level	Justification
CO	PO	-	-
CO1	PO1	L1	Knowledge on semiconductor materials, internal structure of a SCR and characteristics of SCR.
CO1	PO2	L2	Identify the latching current and holding current to obtain the performance and characteristics of SCR
CO2	PO1	L1	Knowledge on semiconductor materials, internal structure of a MOSFET, IGBT and characteristics of MOSFET and IGBT.
CO2	PO2	L4	Analyse the output and transfer characteristics of IGBT and MOSFET to obtain the performance and characteristics of IGBT and MOSFET.
CO3	PO1	L1	Knowledge on semiconductor materials, internal structure of a TRIAC and characteristics of TRIAC.
CO3	PO2	L4	Analyse the static characteristics of TRIAC to obtain the performance in terms of voltage and current.
CO4	PO1	L1	Knowledge on UJT, oscillator is required to generate triggering pulses.
CO4	PO2	L4	Analyse the UJT firing circuit to generate firing signals.
CO4	PO9	L3	Projects can be done on UJT firings circuits.
CO5	PO1	L1	Knowledge on SCR, single phase control rectifier and digital circuit is required to produce the triggering pulses.

CO5	PO2	L4	Analyse the digital firing circuit to trigger the SCR in power circuit.
CO5	PO9	L3	Projects or internship on digital firing circuit.
CO6	PO1	L1	Knowledge on SCR and single phase control rectifier is required to produce the triggering pulses.
CO6	PO2	L2	Identify the different types of control rectifiers for different loading conditions.
CO6	PO9	L3	Projects or internship on control rectifier.
CO7	PO1	L1	Knowledge on SCR, single phase AC voltage controller, TRIAC and DIAC is required.
CO7	PO2	L4	Analyze the performance of AC voltage controller applied to R & RL load using TRIAC and DIAC.
CO7	PO9	L3	Projects or internship on AC voltage controller for control of AC operated instruments.
CO8	PO1	L1	Knowledge on DC motor and different types of DC motor is required for the control of speed of DC motor.
CO8	PO2	L4	Analysis of of semi converter by varying the firing angle to control the speed of DC motor.
CO8	PO9	L3	Projects or internship on application where speed of DC motor is varied.
CO9	PO1	L1	Knowledge on stepper motor is required for the control of speed of stepper motor.
CO9	PO2	L4	Analysis of stepper motor by varying the stepper motor with different inputs and to control the speed of DC motor.
CO9	PO9	L3	Projects or internship on application where speed of stepper motor is varied.
CO10	PO1	L1	Knowledge on Universal motor and different types of motor is required for the control of speed of the motor.
CO10	PO2	L4	Analysis of controlled rectifier by varying the firing angle to control the speed of universal motor.
CO10	PO9	L3	Projects or internship on application where speed of universal motor is varied.
CO11	PO1	L1	Knowledge on DC motor and different types of DC motor is required for the control of speed of DC motor.
CO11	PO2	L4	Analysis of chopper by varying the duty cycle to control the speed of DC motor.
CO11	PO9	L3	Projects or internship on application where speed of DC motor is varied.
CO12	PO1	L1	Knowledge on current and voltage protection is required for the design of protection circuit.
CO12	PO2	L4	Analysis of snubber circuit for over voltage protection.
CO12	PO3	L3	Design of snubber circuit for over voltage protection

Note: Write justification for each CO-PO mapping.

## 5. Curricular Gap and Content

SNo	Gap Topic	Actions Planned	Schedule Planned	Resources Person	PO Mapping
1					

Note: Write Gap topics from A.4 and add others also.

## 6. Content Beyond Syllabus

SNo	Gap Topic	Actions Planned	Schedule Planned	Resources Person	PO Mapping
1					
2					
3					



Note: Anything not covered above is included here.

## C. COURSE ASSESSMENT

### 1. Course Coverage

Unit	Title	Teaching Hours	No. of question in Exam							CO	Levels
			CIA-1	CIA-2	CIA-3	Asg-1	Asg-2	Asg-3	SEE		
1	Static Characteristics of SCR.	03	1	-	-	-	-	-	1	CO1	L3
2	Static Characteristics of MOSFET and IGBT	03	1	-	-	-	-	-	1	CO2	L3
3	Characteristic of TRIAC	03	1	-	-	-	-	-	1	CO3	L3
4	SCR turn on circuit using synchronized UJT relaxation oscillator	03	1	-	-	-	-	-	1	CO4	L3
5	SCR digital triggering circuit for a single phase-controlled rectifier and ac voltage regulator.	03	-	1	-	-	-	-	1	CO5	L4
6	Single phase controlled full wave rectifier with R and R-L loads.	03	-	1	-	-	-	-	1	CO6	L4
7	AC voltage controller using TRIAC and DIAC combination connected to R and RL loads.	03	-	1	-	-	-	-	1	CO7	L4
8	Speed control of dc motor using single semi converter.	03	-	1	-	-	-	-	1	CO8	L4
9	Speed control of stepper motor.	03	-	-	1	-	-	-	1	CO9	L5
10	Speed control of universal motor using ac voltage regulator	03	-	-	1	-	-	-	1	CO10	L4
11	Speed control of a separately excited D.C. Motor using an IGBT or MOSFET chopper.	03	-	-	1	-	-	-	1	CO11	L4
12	Design of Snubber circuit.	03	-	-	1	-	-	-	1	CO12	L5
-	<b>Total</b>	<b>60</b>	<b>4</b>	<b>4</b>	<b>4</b>	<b>5</b>	<b>5</b>	<b>5</b>	<b>12</b>	-	-

Note: Write CO based on the theory course.

### 2. Continuous Internal Assessment (CIA)

Evaluation	Weightage in Marks	CO	Levels
CIA Exam – 1	30	CO1, CO2, CO3, CO4	L3, L3,L3,L3
CIA Exam – 2	30	CO5, CO6, CO7, CO8	L4, L4, L4, L4
CIA Exam – 3	30	CO9, CO10, CO11, CO12	L5, L4, L4,L5
Assignment - 1	05	CO1, CO2, CO3, CO4	L3, L3,L3,L3
Assignment - 2	05	CO5, CO6, CO7, CO8	L4, L4, L4, L4
Assignment - 3	05	CO9, CO10, CO11, CO12	L5, L4, L4,L5
Other Activities – define – Slip test		CO1 to CO9	L2, L3, L4 . .

<b>Final CIA Marks</b>	<b>40</b>	<b>-</b>	<b>-</b>
------------------------	-----------	----------	----------

<b>SNo</b>	<b>Description</b>	<b>Marks</b>
1	Observation and Weekly Laboratory Activities	05 Marks
2	Record Writing	10 Marks for each Expt
3	Internal Exam Assessment	25 Marks
4	Internal Assessment	15 Marks
5	SEE	80 Marks
-	<b>Total</b>	<b>100 Marks</b>

## D. EXPERIMENTS


### Experiment 01 : Static Characteristics of SCR

-	<b>Experiment No.:</b>	1	<b>Marks</b>		<b>Date Planned</b>		<b>Date Conducted</b>	
1	Title	Static Characteristics of SCR						
2	Course Outcomes	Obtain the static characteristic of SCR and their performance in terms of voltage & current.						
3	Aim	1. To obtain V-I characteristics of SCR for different gate currents. 2. To obtain holding current and latching current experimentally.						
4	Material / Equipment Required	Lab Manual SCR-TYN612 Dual power supply Milli ammeter-0-10mA,0-100mA Voltmeter-0-300V Rheostat- 1Kohms						
5	Theory, Formula, Principle, Concept	<p>Thyristors or silicon controlled rectifiers, SCR are find many uses in electronics, and in particular for power control. These devices have even been called the workhorse of high power electronics.</p> <p>Thyristors are able to switch large levels of power are accordingly they used in a wide variety of different applications. Thyristors even finds uses in low power electronics where they are used in many circuits from light dimmers to power supply over voltage protection.</p> <p>The term SCR or silicon controlled rectifier is often used synonymously with that of thyristor - the SCR or silicon controlled rectifier is actually a trade name used by General Electric.</p> <p>The thyristor or silicon controlled rectifier, SCR is a device that has a number of unusual characteristics. It has three terminals: Anode, cathode and gate, reflecting thermionic valve / vacuum tube technology. As might be expected the gate is the control terminal while the main current flows between the anode and cathode.</p> <p>As can be imagined from its circuit symbol shown below, the device is a "one way device" giving rise to the GE name for it the silicon controlled rectifier.</p>						


Therefore when the device is used with AC, it will only conduct for a maximum of half the cycle.

In operation, the thyristor or SCR will not conduct initially. It requires a certain level of current to flow in the gate to "fire" it. Once fired, the thyristor will remain in conduction until the voltage across the anode and cathode is removed - this obviously happens at the end of the half cycle over which the thyristor conducts. The next half cycle will be blocked as a result of the rectifier action. It will then require current in the gate circuit to fire the SCR again.

- |   |  |   |
|---|--|---|
| 6 | Procedure, Program, Activity, Algorithm, Pseudo Code | <ul style="list-style-type: none"> <li>• Connections are made as shown in the circuit diagram.</li> <li>• Gate current <math>I_G</math> is set at different values (3-4.5 mA) by varying the gate supply voltage.</li> <li>• The V-I curve is obtained by slowly varying anode supply voltage. (Anode, current will be very small till breakdown point is reached. At breakdown there is a sudden flow of anode current and the voltage across SCR drops down to a low value approximately, less than 1 V).</li> <li>• The latching current <math>I_L</math> is obtained by noting down anode current immediately after the SCR starts conducting. Also note down the breakdown voltage, <math>V_{BD}</math>.</li> <li>• The holding current <math>I_H</math> is obtained by decreasing the anode voltage. At some point anode current suddenly drops to zero. The current at which this happens is the holding current.</li> <li>• The procedure is repeated for different gate currents.</li> </ul> |
|---|--|---|

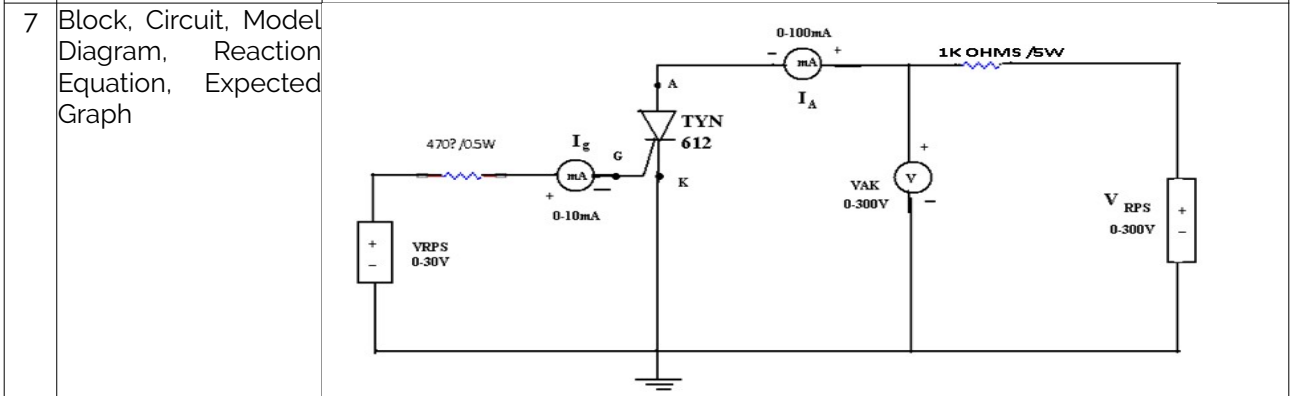



8	Observation Table, Look-up Table, Output	<table border="1"> <tr> <td><math>V_{AK}</math> (V)</td> <td><math>I_A</math> (mA)</td> </tr> <tr> <td><math>I_{G1}</math> (mA)</td> <td></td> </tr> <tr> <td><math>I_{G2}</math> (mA)</td> <td></td> </tr> <tr> <td><math>V_{AK}</math> (V)</td> <td><math>I_A</math> (mA)</td> </tr> </table>	$V_{AK}$ (V)	$I_A$ (mA)	$I_{G1}$ (mA)		$I_{G2}$ (mA)		$V_{AK}$ (V)	$I_A$ (mA)
$V_{AK}$ (V)	$I_A$ (mA)									
$I_{G1}$ (mA)										
$I_{G2}$ (mA)										
$V_{AK}$ (V)	$I_A$ (mA)									

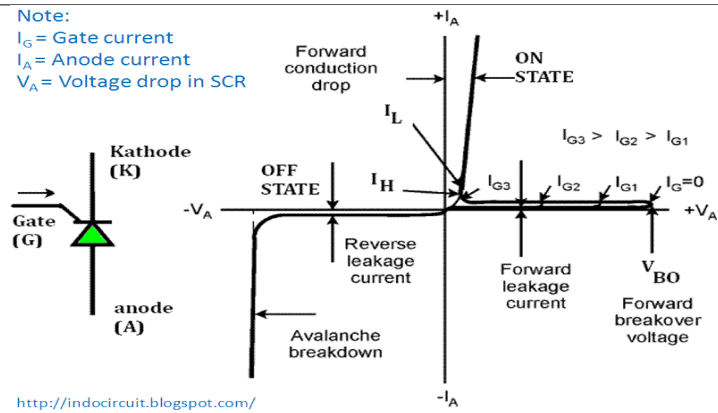9	Sample Calculations	
10	Graphs, Outputs	<p>Note:  <math>I_G</math> = Gate current  <math>I_A</math> = Anode current  <math>V_A</math> = Voltage drop in SCR</p>  <p><a href="http://indocircuit.blogspot.com/">http://indocircuit.blogspot.com/</a></p>
11	Results & Analysis	
12	Application Areas	<ul style="list-style-type: none"> <li>• SCR are used in Industrial application such as induction heating, dielectric heating and lamp dimming.</li> <li>• SCR are used in static AC /DC circuit breakers, control rectifiers, tap changers</li> </ul>
13	Remarks	
14	Faculty Signature with Date	

### Experiment 02 : Static Characteristics of MOSFET and IGBT

-	Experiment No.:	2	Marks	Date Planned	Date Conducted	
1	Title	Static Characteristics of MOSFET and IGBT				
2	Course Outcomes	Compute static characteristics of MOSFET & IGBT and obtain their performance in terms of voltage & current.				
3	Aim	1) To obtain the output characteristics. 2) To plot the drain current $I_D$ as a function of drain to source voltage $V_{DS}$ with gate to source voltage $V_{GS}$ as parameter. 3) To obtain the transfer characteristics. 4) To plot the drain current $I_D$ against gate to source voltage $V_{GS}$ . 5) To find trans conductance from transfer characteristics.				
4	Material Equipment Required	/ Lab Manual MOSFET-IRF540 IGBT-IGRP40u Voltmeter-0-50V,0-10V,0-100V Ammeter-0-100A,0-50mA Dual Power Supply-2 Resistor-100Ohms, 1KOhms, 470ohms				
5	Theory, Formula, Principle, Concept	The <b>MOSFET</b> (Metal Oxide Semiconductor Field Effect Transistor) transistor is a semiconductor device which is widely used for switching and amplifying electronic signals in the electronic devices. The MOSFET is a core of integrated circuit and it can be designed and fabricated in a single chip because of these very small sizes. The MOSFET is a four terminal device with source(S), gate (G),				

		<p>drain (D) and body (B) terminals. The body of the MOSFET is frequently connected to the source terminal so making it a three terminal device like field effect transistor. The MOSFET is very far the most common transistor and can be used in both analog and digital circuits.</p> <p>The <b>Insulated Gate Bipolar Transistor</b> also called an <b>IGBT</b> for short, is something of a cross between a conventional <i>Bipolar Junction Transistor</i>, (BJT) and a <i>Field Effect Transistor</i>, (MOSFET) making it ideal as a semiconductor switching device. The <i>IGBT Transistor</i> takes the best parts of these two types of common transistors, the high input impedance and high switching speeds of a MOSFET with the low saturation voltage of a bipolar transistor, and combines them together to produce another type of transistor switching device that is capable of handling large collector-emitter currents with virtually zero gate current drive.</p> <p>The <i>Insulated Gate Bipolar Transistor</i>, (IGBT) combines the insulated gate (hence the first part of its name) technology of the MOSFET with the output performance characteristics of a conventional bipolar transistor, The advantage gained by the insulated gate bipolar transistor device over a BJT or MOSFET is that it offers greater power gain than the standard bipolar type transistor combined with the higher voltage operation and lower input losses of the MOSFET. In effect it is an FET integrated with a bipolar transistor in a form of Darlington type configuration.</p>
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<p><b>1.OUTPUT CHARACTERISTICS</b></p> <ol style="list-style-type: none"> <li>1. Circuit connections are made as shown in the figure.</li> <li>2. Keep the gate voltage constant say 3.2V, 3.3V, 3.4V.</li> <li>3. Vary the drain voltage from (0 to 30V) volts in steps of 0.5V and obtain the drain currents.</li> <li>4. Each time note down the drain current and drain voltage.</li> <li>5. Repeat the above procedure for different gate voltages.</li> <li>6. Plot the drain current Vs drain voltage.</li> <li>7. Calculate the <math>R_{DS}</math> from the graph.</li> </ol> <p><b>2.TRANSFER CHARACTERISTICS</b></p> <ol style="list-style-type: none"> <li>1. Keep the drain voltage as constant as say 5V,10V and 12V.</li> <li>2. Vary the gate voltage in steps of 0.1V from 3.0V to 3.8V.</li> <li>3. Each time obtain the drain current.</li> <li>4. Repeat the above procedure for different drain voltages.</li> <li>5. Plot the curve for <math>I_D</math> Vs <math>V_{GS}</math>.</li> <li>6. From the graph find the Trans conductance (<math>G_M</math>).</li> </ol>

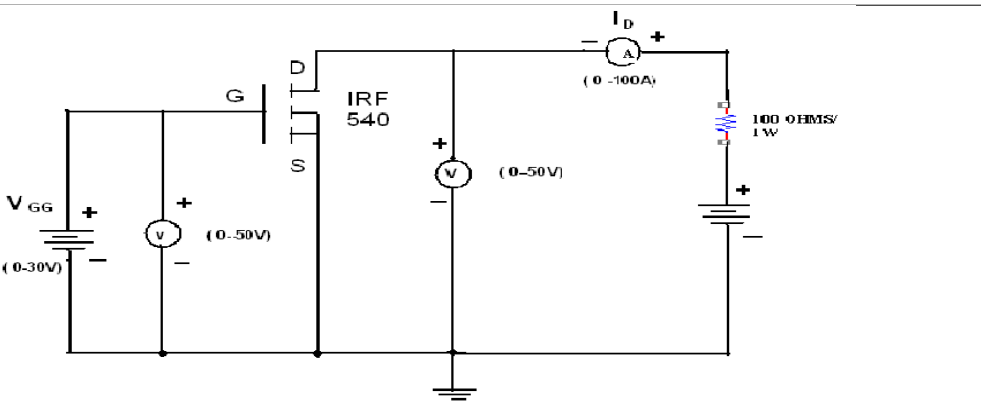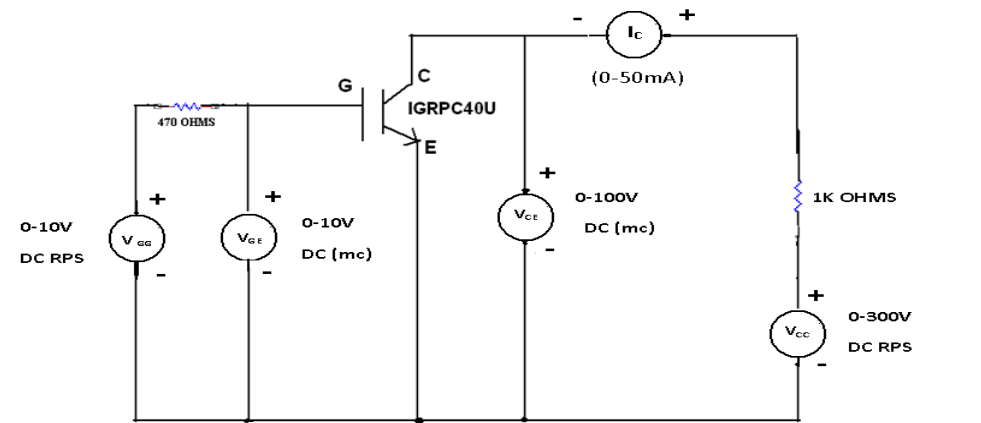7	Block, Model, Reaction Equation, Expected Graph	 <p>(a) MOSFET Characteristics</p>  <p>(b) IGBT Characteristics</p>																								
8	Observation Table, Look-up Table, Output	<p>Output characteristics</p> <table border="1" data-bbox="446 1155 1421 1323"> <thead> <tr> <th><math>V_{DS}</math> In volts</th> <th><math>V_{GS}</math> in volts</th> <th><math>I_D</math> in mA</th> </tr> </thead> <tbody> <tr> <td>5V</td> <td></td> <td></td> </tr> <tr> <td>10V</td> <td></td> <td></td> </tr> <tr> <td>12V</td> <td></td> <td></td> </tr> </tbody> </table> <p>Transfer Characteristics</p> <table border="1" data-bbox="446 1438 1421 1606"> <thead> <tr> <th><math>V_{GS}</math> In volts</th> <th><math>V_{DS}</math> in volts</th> <th><math>I_D</math> in mA</th> </tr> </thead> <tbody> <tr> <td>3.2V</td> <td></td> <td></td> </tr> <tr> <td>3.3V</td> <td></td> <td></td> </tr> <tr> <td>3.4V</td> <td></td> <td></td> </tr> </tbody> </table>	$V_{DS}$ In volts	$V_{GS}$ in volts	$I_D$ in mA	5V			10V			12V			$V_{GS}$ In volts	$V_{DS}$ in volts	$I_D$ in mA	3.2V			3.3V			3.4V		
$V_{DS}$ In volts	$V_{GS}$ in volts	$I_D$ in mA																								
5V																										
10V																										
12V																										
$V_{GS}$ In volts	$V_{DS}$ in volts	$I_D$ in mA																								
3.2V																										
3.3V																										
3.4V																										
9	Sample Calculations																									
10	Graphs, Outputs	Drain Characteristics																								


		<p>Transfer characteristics</p>
11	Results & Analysis	The output as well transfer characteristics for MOSFET are obtained and the corresponding graphs as per aim are plotted.
12	Application Areas	<ul style="list-style-type: none"> <li>• Transistors are used in low power logic gates, DC motor drives, AC motor drives.</li> <li>• Transistors are used in isolation circuit such as opto-couplers and pulse transformers.</li> </ul>
13	Remarks	
14	Faculty Signature with Date	

### Experiment 03 : Characteristics of TRIAC

-	Experiment No.:	3	Marks	Date Planned	Date Conducted	
1	Title	Characteristics of TRIAC				
2	Course Outcomes	Compute static characteristics of TRIAC and obtain their performance in terms of voltage & current.				
3	Aim	To draw <b>V-I</b> characteristics of TRIAC for different values of Gate Currents.				
4	Material Equipment Required	Lab Manual TRIAC-BT136 Voltmeter-0-30V Ammeter-0-30A Resistors-1Kohms,100ohms Dual power supply				
5	Theory, Formula, Principle, Concept	A Triac is a high-speed solid-state device that can switch and control AC power in both directions of a sinusoidal waveform. "Triode AC Switch" or <b>Triac</b> for short which is also a member of the thyristor family that be used as a solid state power switching device but more importantly it is a "bidirectional" device. In other words, a <i>Triac</i> can be triggered into conduction by both positive and negative voltages applied to its Anode and with both positive and negative trigger pulses applied to its Gate terminal making it a two-quadrant switching				

		<p>Gate controlled device.</p> <p>A <b>Triac</b> behaves just like two conventional thyristors connected together in inverse parallel (back-to-back) with respect to each other and because of this arrangement the two thyristors share a common Gate terminal all within a single three-terminal package. Since a triac conducts in both directions of a sinusoidal waveform, the concept of an Anode terminal and a Cathode terminal used to identify the main power terminals of a thyristor are replaced with identifications of: <math>MT_1</math>, for <i>Main Terminal 1</i> and <math>MT_2</math> for <i>Main Terminal 2</i> with the Gate terminal G referenced the same.</p>
<p>6</p>	<p>Procedure, Program, Activity, Algorithm, Pseudo Code</p>	<ol style="list-style-type: none"> <li>1. Connections are made as shown in the circuit diagram</li> <li>2. Adjust the value of <math>I_g</math> to zero or some minimum value</li> <li>3. By varying the voltage <math>V_{mt2mt1}</math> from 0 to 10 volts with a step of 2 volts, note down corresponding values of <math>I_1</math></li> <li>4. Now apply the gate voltage gradually, until SCR fires, then note down the values of <math>I_g</math> and also the values of <math>I_1</math> and <math>V_{mt2mt1}</math>.</li> <li>5. Increase <math>V_m</math> to some value and note down <math>I_1</math> and <math>V_{mt2mt1}</math>.</li> <li>6. Reduce gate voltage to zero, observe ammeter reading by reducing <math>V_m</math> which gives the values of <math>I_h</math> (holding current) at the point at which, current suddenly drops to zero</li> <li>7. Repeat the steps 2, 3, 4, 5 &amp; 6 for different values of break over voltages</li> <li>8. Plot a graph of <math>V_{mt1mt2}</math> v/s <math>I_1</math></li> <li>9. Repeat the steps 1, 2, 3, 4, 5, 6 &amp; 7 for different modes</li> <li>10. Compare sensitivity of TRIAC and comment on sensitivities.</li> <li>11. Refer same design procedure for selection of <math>R_L</math> and <math>R_g</math> as that of SCR.</li> <li>12. Follow the same procedure as that of SCR experiment to find latching current.</li> </ol>
<p>7</p>	<p>Block, Model, Circuit, Diagram, Reaction Equation, Expected Graph</p>	<p>(a) MODE 1</p>



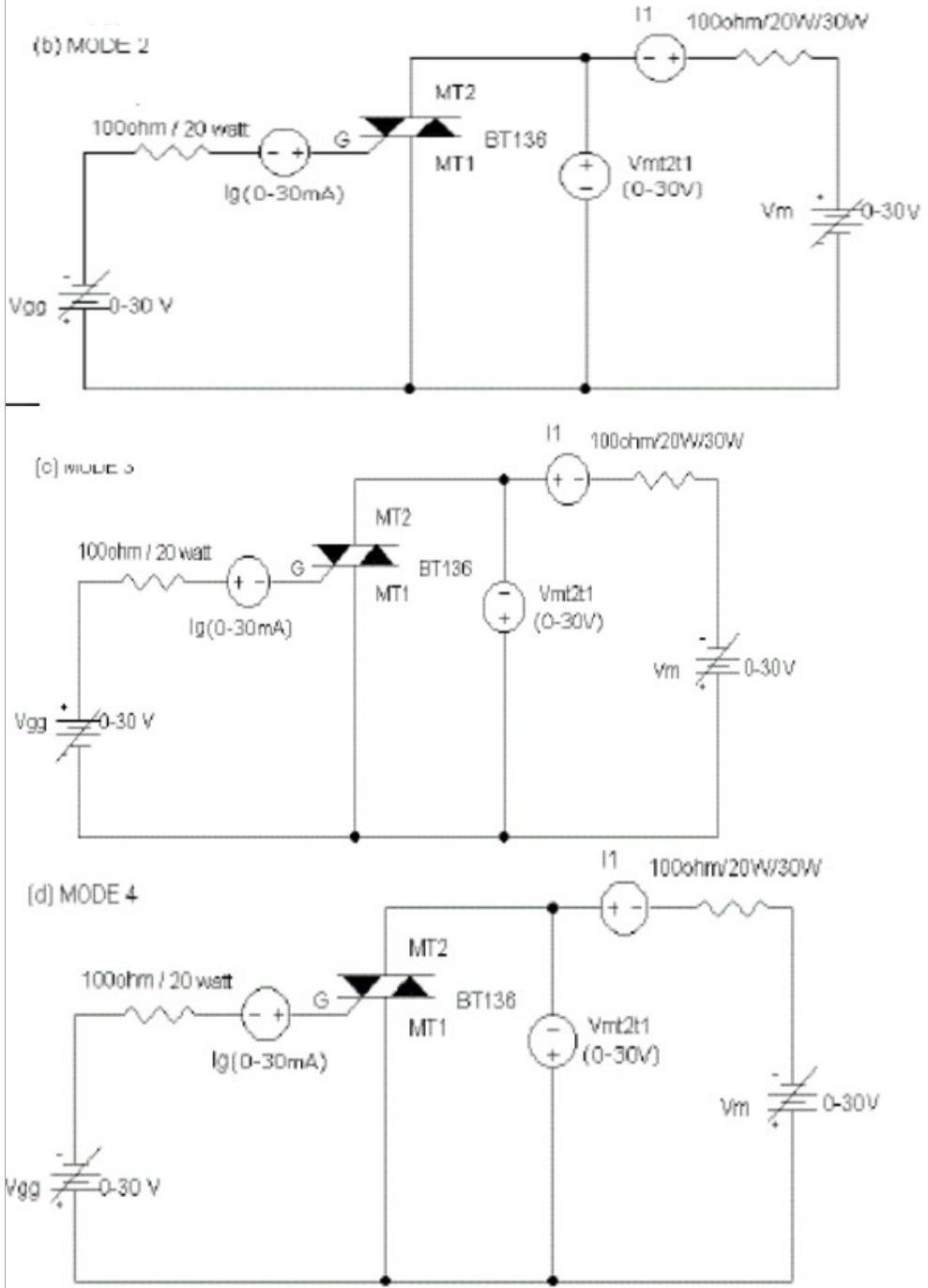

8 Observation Table, Look-up Table, Output

For Forward Bias

Sl.No	Voltage(V)	Current(mA)


For Reverse Bias

		Sl.No	Voltage(V)	Current(mA)	
9	Sample Calculations				
10	Graphs, Outputs	<p style="text-align: center;"><i>V-I Characteristic of a Triac</i></p>			
11	Results & Analysis	The V-I characteristics of TRIAC is plotted on the graph which is true according to theory.			
12	Application Areas	TRIAC's are used in AC switches, starter circuit for lamps.			
13	Remarks				
14	Faculty Signature with Date				

**Experiment 04 : SCR turn on circuit using synchronized UJT relaxation Oscillator**

-	Experiment No.:	4	Marks		Date Planned		Date Conducted	
1	Title	SCR turn on circuit using synchronized UJT relaxation Oscillator						
2	Course Outcomes	To generate triggering pulses using UJT relaxation oscillator.						
3	Aim	1.To obtain triggering pulses of sufficient amplitude and width using UTJ. 2. SCR triggering circuit using the pulses obtained in (1).						
4	Material Equipment Required	/ Lab Manual UJT relaxation circuit module SCR power circuit						
5	Theory, Formula, Principle, Concept	A synchronized UJT triggered circuit using an UJT is shown in the figure. Diode Rectifier converts input ac to dc. Resistor R limits the circuit current to a suitable value for the zener diode and UJT. Zener diode 'Z' functions to clip the rectified voltage to a standard level. The zener voltage $V_z$ is applied to the RC charging circuit. Charging of capacitor C is at a rate determined by R1 and R3. When voltage across the capacitor, $V_c$ reaches the unijunction threshold voltage $\eta V_{z}$ , the UJT junction breaks down and the capacitor C discharges through the primary of pulse transformer. As the current is in the form of pulse, windings of the pulse transformer have pulse voltages at their secondary terminals and can turn on the SCR. As the charging rate of capacitor varies by varying R3, firing angle can be controlled by varying R3. Firing angle can be controlled in a range of 0 to 180°.						

<p>6</p>	<p>Procedure, Program, Activity, Algorithm, Pseudo Code</p>	<ol style="list-style-type: none"> <li>1. The circuit connections are made as shown for half wave firing circuit for thyristor and observe the wave form across load. Bt varying the potentiometer R observe the wave form on CRO at different points.</li> <li>2. Connect CRO across load terminals.</li> <li>3. Connect voltmeter 0-50V dc across load terminals to get <math>V_{dc}</math>.</li> <li>4. The potentiometer pf triggering circuit is kept at minimum.</li> <li>5. Check the circuit connections and power on the trainer kit.</li> <li>6. Slowly vary the potentiometer of triggering circuit clockwise to obtain output on CRO and measure the angle.</li> <li>7. Vary the potentiometer of triggering circuit to get different angle. Obtain the reading of <math>\alpha</math> and <math>I_{dc}</math> and <math>V_{dc}</math> in ammeter and voltmeter and tabulate the readings of <math>\alpha</math>, <math>I_{dc}</math> &amp; <math>V_{dc}</math> for different firing angles.</li> <li>8. Repeat the above procedure for R and L load connected together, <math>R=100\Omega</math> and <math>L=10mH</math> which are provided on the panel.</li> <li>9. Tabulate the readings for R &amp; L load for different <math>\alpha</math>, <math>I_{dc}</math> &amp; <math>V_{dc}</math></li> <li>10. Connect free wheeling diode across load terminals and observe the waveforms.</li> </ol> <p style="text-align: center;"><math>V_{dc} = \frac{V_m(1+\cos\alpha)}{2\pi}</math>      For R load</p>
<p>7</p>	<p>Block, Model, Circuit, Diagram, Reaction Equation, Expected Graph</p>	

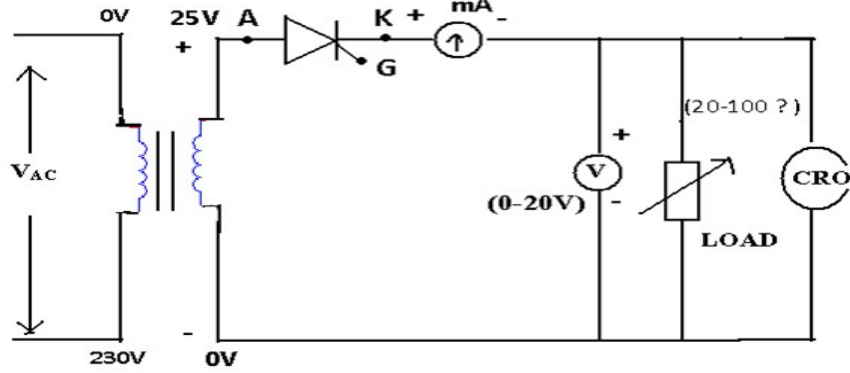


8 Observation Table, Look-up Table, Output

$\alpha$	$\pi - \alpha$	$V_{dc}$	$I_{dc}$	$R_L$	$V_{dc}(th)$	$I_{dc}(th)$

9 Sample Calculations

10 Graphs, Outputs

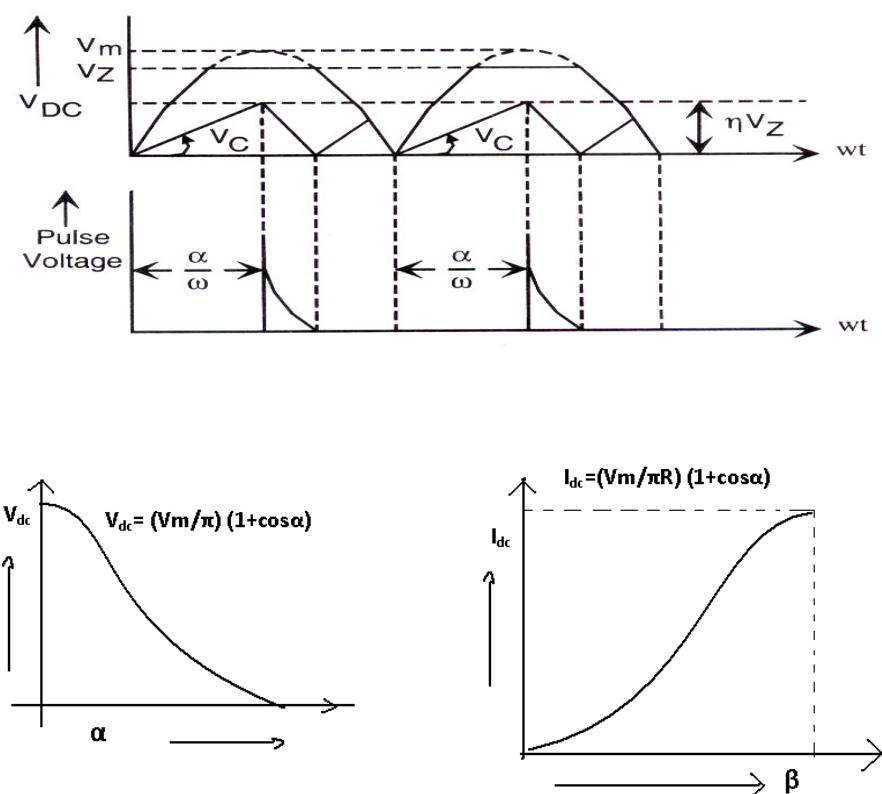

11 Results & Analysis

Wave forms are observed and verified.


12 Application Areas

UJT is used as a triggering device for SCR's, sawtooth generators, phase control and timing circuits

13	Remarks	
14	Faculty Signature with Date	

**Experiment 05 : SCR Digital triggering circuit for a single phase controlled rectifier and AC voltage controller**

-	Experiment No.:	5	Marks		Date Planned		Date Conducted
1	Title	SCR Digital triggering circuit for a single phase controlled rectifier and AC voltage controller					
2	Course Outcomes	Generator triggering pulses using SCR digital trigger circuit using single phase controlled rectified AC Voltage controller					
3	Aim	To generate the firing signals for thyristor/TRIAC'S using digital circuits.					
4	Material Equipment Required	Lab Manual Digital Firing circuit Transformer- 240V/12V SCR-2 Resistor-100ohms CRO Voltmeter-0-20V Ammeter					
5	Theory, Formula, Principle, Concept						
6	Procedure, Program, Activity, Algorithm, Pseudo Code	The circuit connection is made as per the circuit diagram. 1.Connect CRO across Load terminals for channel-1 to see the load wave forms 2. Connect voltmeter 0-50V DC across load terminals A&B to get $V_{DC}$ . 3.Connect triggering circuit output $G_1$ to $G_1$ of triggering circuit . $K_1$ to $G_2$ , $K_2$ to $K_2$ of triggering circuit terminals. 4. Check the circuit connections and power on the trainer kit. 5.Vary the logic switches from 0001 to 1111(15) and vary the firing angle. 6. Tabulate the readings for $\alpha$ , $I_{dc}$ and $V_d$ .					
7	Block, Model Diagram, Reaction Equation, Expected Graph	<p>(a) Block diagram of digital firing circuit</p>					

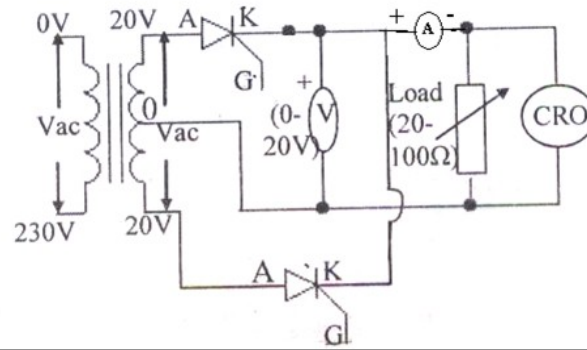


8 Observation Table, Look-up Table, Output

$\alpha$	$\beta = (\pi - \alpha)$	$V_{dc}$	$V_{dc} (Th)$	$I_{dc} (mA)$

9 Sample Calculations

10 Graphs, Outputs

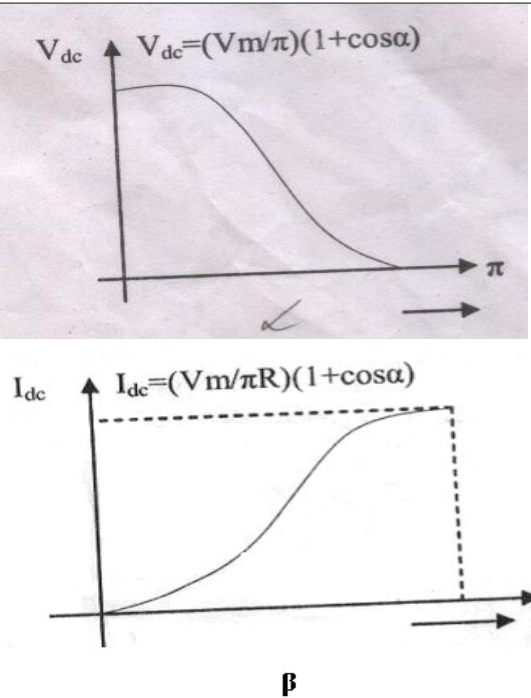

11 Results & Analysis

12 Application Areas

13 Remarks

14 Faculty Signature with Date

Firing signals for thyristors using digital circuits are verified.


AC voltage controllers are used in cyclo converters, matrix converters, Electric welding

## Experiment 06 : Single Phase Controlled full wave rectifier with R and RL loads

-	Experiment No.:	6	Marks		Date Planned		Date Conducted	
1	Title	Single Phase Controlled full wave rectifier with R and RL loads						
2	Course Outcomes	Analyze the performance of a single phase full wave controlled rectified connected to R & RL load						
3	Aim	<ol style="list-style-type: none"> <li>1. To plot <math>V_{DC}</math> Vs firing angle <math>\alpha</math> for R-load.</li> <li>2. To plot <math>V_{DC}</math> Vs conduction angle for R-l load.</li> <li>3. To observe load voltage and SCR wave form on a CRO.</li> <li>4. To observe the effect of FWD (Free wheeling diode) on load voltage wave form.</li> </ol>						
4	Material Equipment Required	Lab Manual SCR-4 No Ammeter Voltmeter Rheostat Inductor Freewheeling Diode Triggering circuit CRO						
5	Theory, Formula, Principle, Concepts	<p>In the period <math>0 &lt; t &lt; \pi/\omega</math>, the SCRs T1 and T2 are forward biased and the SCRs T3 and T4 are reverse biased. Then current through the load and voltage drop across the load are zero. Let the SCRs T1 and T2 be triggered at an angle of <math>\alpha</math> (<math>0 &lt; \alpha &lt; \pi/\omega</math>). Then the supply terminals are connected to the load through the SCRs and the current starts flowing through the load via SCRs T1 and T2. Therefore the supply voltage appears across the load with a drop of R and the voltage drop across the SCRs is zero when they are conducting (SCR is assumed ideal). In the period <math>(\pi/\omega &lt; t &lt; 2\pi/\omega)</math>; the SCRs T1 and T2 are reversed biased hence cannot conduct and T3 and T4 are forward biased. When they are triggered at an angle of <math>(\pi+\alpha)/\omega</math> (<math>0 &lt; (\pi+\alpha)/\omega &lt; 2\pi/\omega</math>). Then the supply terminals are connected to the load through the SCRs and the current starts flowing through the load via SCRs T3 and T4. Therefore the supply voltage appears across the load with a drop R and the voltage drop across the SCRs is zero when they are conducting (SCR is assumed ideal). These SCRs continue to conduct up to <math>2\pi/\omega</math>. Again during the third positive Half cycle supply is positive and SCRs T1 and T2 are forward biased, if we give triggering SCRs start conducting and this cycle repeats</p>						
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<p>The circuit connection is made as per the circuit diagram.</p> <ol style="list-style-type: none"> <li>1. Connect CRO across Load terminals A and B for channel-1 to see the load wave forms</li> <li>2. Connect voltmeter 0-50V DC across load terminals A&amp;B to get <math>V_{DC}</math>.</li> <li>3. Connect triggering circuit output <math>G_1</math> to <math>G_1</math> of triggering circuit. <math>K_1</math> to <math>G_2</math>, <math>K_2</math> to <math>K_2</math>, <math>G_3</math> to <math>G_3</math>, <math>K_3</math> to <math>K_3</math>, <math>G_4</math> to <math>G_4</math> and <math>K_4</math> to <math>K_4</math> of triggering circuit terminals.</li> <li>4. The potentiometer of triggering circuit is kept at minimum.</li> <li>5. Check the circuit connections and power on the trainer kit.</li> <li>6. Slowly vary the potentiometer of triggering circuit clockwise, to obtain output on CRO</li> <li>7. To measure the angle the input 0 to 25V AC from triggering circuit transformer output (C&amp;D) to CRO channel II.</li> </ol>						

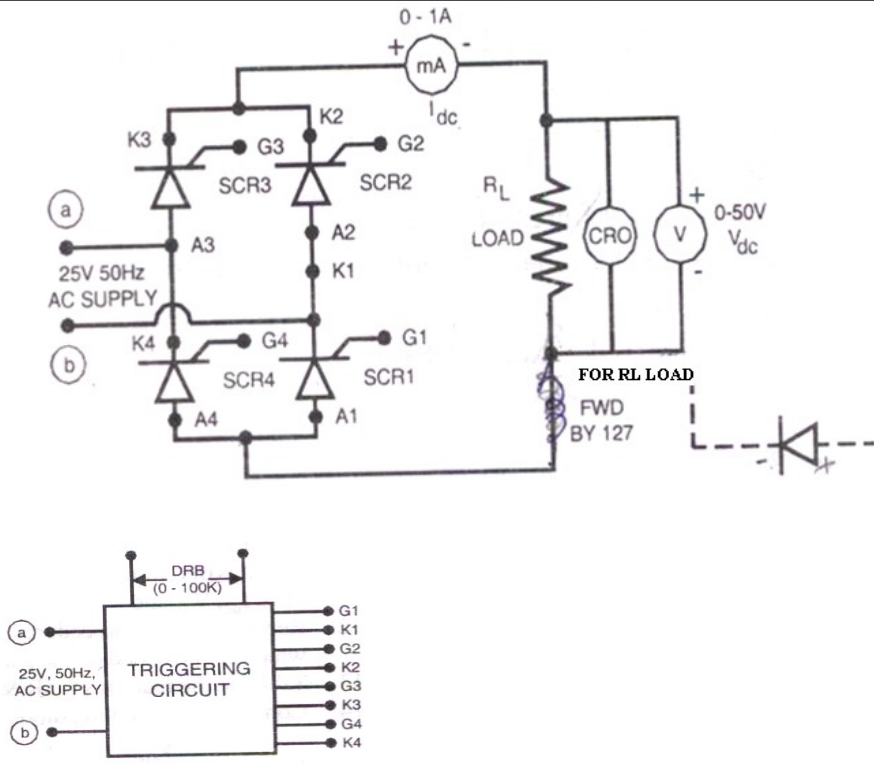8. Align the two output waveforms on CRO.  
 9. Vary the potentiometer of triggering circuit to get different angle and obtain the readings of  $\alpha$  (angle) and  $I_{dc}$  and  $V_{dc}$  in Ammeter and voltmeter and tabulate the readings of  $\alpha$ ,  $I_{dc}$  and  $V_{dc}$  and  $\pi - \alpha$  for different firing angles.  
 10. Repeat the above procedure for R and L load connected together,  $R=100\Omega$  and  $L=10mH$  which are provided on the panel.  
 11. Tabulate the readings for R and L loads for different  $\alpha$ ,  $I_{dc}$  and  $V_{dc}$ .  
 12. Connect free wheeling diode across load terminals and observe the waveforms.  $V_{dc} = V_m \frac{\pi}{\pi + \cos \alpha}$  for R load and R-L load with FWD.  $V_{dc} = 2 V_m (\cos \alpha) / \pi$  for R-L load.  
 13. Verify the values of  $V_{dc}$  and  $I_{dc}$  theoretically.

7 Block, Circuit, Model Diagram, Reaction Equation, Expected Graph



8 Observation Table, Look-up Table, Output

(a) For R-Load			
$\alpha$			
$V_L$ in V			
$I_{dc}$ in mA			
$\pi - \alpha$			
$V_L$ (Th)			
(B) For R-L Load			
$\alpha$			
$V_L$ in V			




<b><math>I_{dc}</math> in mA</b>			
<b><math>\Pi-\alpha</math></b>			
<b><math>V_L</math> (Th)</b>			

9 Sample Calculations

10 Graphs, Outputs


(a) For R- Load

**FOR R - LOAD :**

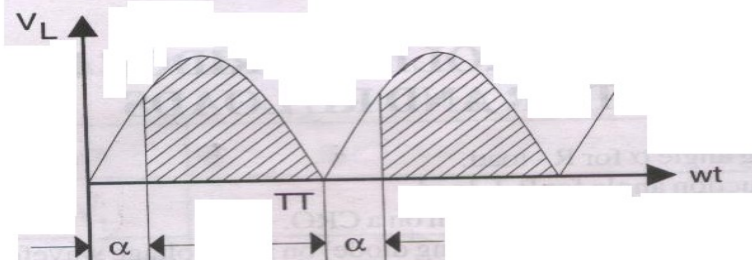


(b) For R-L Load

**WAVEFORM FOR R - L LOAD :**

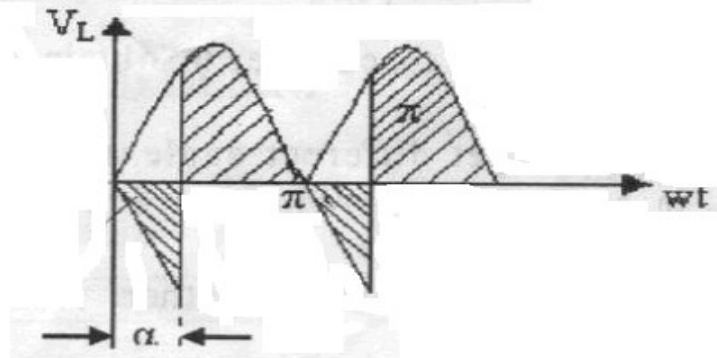

Expected Graph

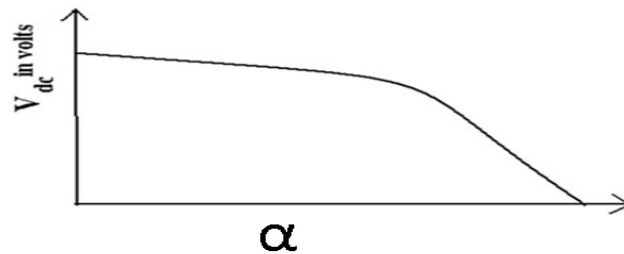

11	Results & Analysis	Firing angles and conduction angles are obtained from R and R-L load and graphs are plotted.
12	Application Areas	Control rectifiers are used in speed control of DC motor, Universal motors, lamp dimming
13	Remarks	
14	Faculty Signature with Date	



### Experiment 07 : AC voltage Controller using TRIAC and DIAC combination

-	Experiment No.:	7	Marks		Date Planned		Date Conduct ed	
1	Title	AC voltage Controller using TRIAC and DIAC combination						
2	Course Outcomes	Analyze the performance of AC voltage controller applied to R & RL load using TRIAC and DIAC.						
3	Aim	<ol style="list-style-type: none"> <li>To observe variation of intensity of light</li> <li>To plot load current Vs delay angle <math>\alpha</math>.</li> <li>To plot load voltage Vs conduction angle <math>(\pi - \alpha)</math>.</li> </ol>						
4	Material Equipment Required	/ Lab Manual Lamp Voltmeter-0-20V Ammeter-0-500mA TRIAC-BT136 DIAC-BR100 DRB 0-10K						
5	Theory, Formula, Principle, Concept							
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<ol style="list-style-type: none"> <li>Connections are made as show in the circuit diagram.</li> <li>DRB resistance is varied in steps. At each step values of load current &amp; voltage are noted down corresponding delay angle and conduction angle are measured on CRO.</li> <li>The variation of intensity of light is observed for variations in R.</li> <li>Plot the graph of <math>I_L</math> (rms) Vs delay angle <math>\alpha</math> and <math>V_L</math> (rms) Vs conduction angle are drawn.</li> </ol>						

7	Block, Circuit, Model Diagram, Reaction Equation, Expected Graph																					
8	Observation Table, Look-up Table, Output	<table border="1" style="width: 100%; text-align: center;"> <thead> <tr> <th><math>\alpha</math></th> <th><math>V_L</math></th> <th><math>\pi - \alpha</math></th> <th><math>I_L</math></th> <th><math>V_L(TH)</math></th> </tr> </thead> <tbody> <tr> <td> </td> <td> </td> <td> </td> <td> </td> <td> </td> </tr> <tr> <td> </td> <td> </td> <td> </td> <td> </td> <td> </td> </tr> <tr> <td> </td> <td> </td> <td> </td> <td> </td> <td> </td> </tr> </tbody> </table>	$\alpha$	$V_L$	$\pi - \alpha$	$I_L$	$V_L(TH)$															
$\alpha$	$V_L$	$\pi - \alpha$	$I_L$	$V_L(TH)$																		
9	Sample Calculations																					
10	Graphs, Outputs	<p>Expected Waveform</p>																				
11	Results & Analysis	The above experiment is performed successfully and corresponding graphs are obtained. Intensity of the light is obtained.																				
12	Application Areas	AC voltage controllers are used in power generation, power transmission, electric heating, induction heating.																				
13	Remarks																					
14	Faculty Signature with Date																					

## Experiment 08 : Speed Control of DC Motor using single semi Converter

-	Experiment No.:	8	Marks	Date Planned	Date Conducted	
1	Title	Speed Control of DC Motor using single semi Converter				
2	Course Outcomes	Control the speed of DC motor using semi converter by varying firing angle.				
3	Aim	<ol style="list-style-type: none"> <li>1. To observe the variations of speed of dc motor</li> <li>2. To plot load current Vs delay angle <math>\alpha</math></li> <li>3. To plot load voltage Vs conduction angle <math>\beta</math></li> <li>4. To observe the effect of free wheeling diode on load voltage waveform</li> </ol>				
4	Material Equipment Required	/ Lab Manual DC Motor Ammeter Voltmeter Semi converter				
5	Theory, Formula, Principle, Concept	<p>In the period <math>0 &lt; t &lt; \pi/\omega</math>; the SCRs T1 and Diode D1 are forward biased and the SCR T2 and Diode D2 are reverse biased. Then current through the load and voltage drop across the load are zero. Let the SCR T1 be triggered at an angle of <math>\alpha</math> (<math>0 &lt; \alpha &lt; \pi/\omega</math>). As the Diode D1 is already conducting the supply terminals are connected to the load through the SCR and Diode, the current starts flowing through the load via SCR T1 and Diode D1. Therefore the supply voltage appears across the load, the voltage drop across the SCR and the Diode is zero when they are conducting (SCR, Diode are assumed ideal). Soon after <math>\pi/\omega</math> load voltage tends to reverse, Free wheeling Diode gets forward biased and starts conducting. The load, or output current is transferred from T1, D1 to FWD. As SCR T1 is reverse biased at <math>t = \pi/\omega +</math> current flows through FWD and T1 is turned off. The load terminals are short circuited through FWD therefore load voltage is zero during <math>[\pi/\omega &lt; t &lt; (\pi + \alpha) / \omega]</math>. During the period <math>(\pi/\omega &lt; t &lt; 2\pi/\omega)</math>; T2 and Diode D2 are forward biased. When T2 is triggered at an angle of <math>(\pi + \alpha) / \omega</math>, <math>[0 &lt; 33(\pi + \alpha) / \omega &lt; 2\pi/\omega]</math>, then the FWD is reverse biased and is turned off. During this period supply terminals are connected to the load through the SCR and the Diode D2, the load current shifts from FWD to T2 and D2. Therefore the supply voltage appears across the load. The voltage drop across the SCR and Diode is zero when they are conducting (SCR, Diode are assumed ideal). SCR T2 and Diode D2 continue to conduct up to <math>2\pi/\omega</math>. For the next half cycle the load current is transferred from T2 and D2 to the FWD and SCR T1 and Diode D1 are forward biased, if we give triggering SCR starts conducting and this cycle repeats.</p>				
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<ol style="list-style-type: none"> <li>1. Connections are made as shown.</li> <li>2. DRB resistance is varied in steps and at each step rms values of load current &amp; load volt are noted.</li> <li>3. At each setting of DRB. The speed in rpm is also measured using a tachometer.</li> <li>4. The speed variation is observed for variation in DRB resistance.</li> <li>5. graphs of speed Vs Irms &amp; N Vs Vrms are plotted</li> </ol>				

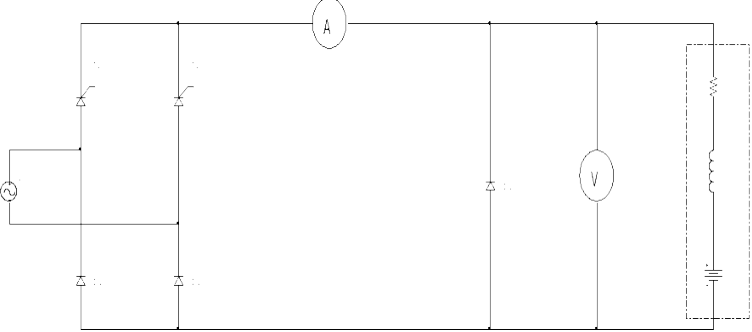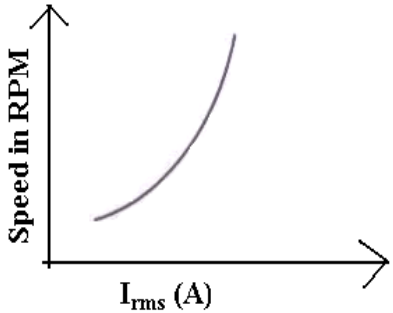7	Block, Model, Reaction, Expected Graph										
8	Observation Table, Look-up Table, Output	<table border="1" data-bbox="451 554 1328 831"> <thead> <tr> <th data-bbox="451 554 776 648">Speed in RPM</th> <th data-bbox="776 554 1078 648"><math>V_{RMS}</math> (V)</th> <th data-bbox="1078 554 1328 648"><math>I_{RMS}</math> (A)</th> </tr> </thead> <tbody> <tr> <td data-bbox="451 648 776 743"> </td> <td data-bbox="776 648 1078 743"> </td> <td data-bbox="1078 648 1328 743"> </td> </tr> <tr> <td data-bbox="451 743 776 831"> </td> <td data-bbox="776 743 1078 831"> </td> <td data-bbox="1078 743 1328 831"> </td> </tr> </tbody> </table>	Speed in RPM	$V_{RMS}$ (V)	$I_{RMS}$ (A)						
Speed in RPM	$V_{RMS}$ (V)	$I_{RMS}$ (A)									
9	Sample Calculations										
10	Graphs, Outputs	<p><b>EXPECTED WAVEFORMS:</b></p> 									
11	Results & Analysis	The variation of speed of AC motor is observed and corresponding graphs are plotted									
12	Application Areas	Control rectifiers are used in speed control of DC motor, Universal motors, lamp dimming.									
13	Remarks										
14	Faculty Signature with Date										


### Experiment 09 : Speed Control of Stepper Motor

-	Experiment No.:	9	Marks	Date Planned		Date Conducted	
1	Title	Speed Control of Stepper Motor					
2	Course Outcomes	Control the speed of stepper motor.					
3	Aim	To observe variation of speed control of DC Stepper motor					

4	Material Equipment Required	<ol style="list-style-type: none"> <li>1. Permanent magnet, Bifilar wound, two phase</li> <li>2. steps per revolution: 200</li> <li>3. step angle: <math>1.8^\circ \pm 0.1^\circ</math> non-cumulative</li> <li>4. No of loads :6</li> <li>5. 1 kg cm =0.1 Nm=13.9 Z-in</li> </ol>
5	Theory, Formula, Principle, Concept	<p>Every motor converts power. Electric motors convert electricity into motion. Stepper motors convert electricity into rotation. Not only does a stepper motor convert electrical power into rotation, but it can be very accurately controlled in terms of how far it will rotate and how fast.</p> <p>Stepper motors are so named because each pulse of electricity turns the motor one step. Stepper motors are controlled by a driver, which sends the pulses into the motor causing it to turn. The number of pulses the motor turns is equal to the number of pulses fed into the driver. The motor will spin at a rate that is equal to the frequency of those same pulses.</p> <p>Stepper motors are very easy to control. Most drivers are looking for 5 volt pulses which just so happen to be the voltage level of most integrated circuits. You merely need to design a circuit to output pulses or use one of ORIENTAL MOTOR's pulse generators.</p> <p>One of the most remarkable features of stepper motors is their ability to position very accurately. This will be covered in depth later on. Stepper motors are not perfect, there are always some little inaccuracies. ORIENTAL MOTOR's standard stepper motors have an accuracy of <math>\pm 3</math> arc minutes (<math>0.05^\circ</math>). The remarkable feature of steps motors, though, is that this error does not accumulate from step to step. When a standard stepper motor travels one step it will go <math>1.8^\circ \pm 0.05^\circ</math>. If the same motor travels one million steps, it will travel <math>1,800,000^\circ \pm 0.05^\circ</math>. The error does not accumulate.</p> <p>Stepper motors can respond and accelerate quickly. They have low rotor inertia that can get up to speed quickly. For this reason stepper motors are ideal for short, quick moves.</p>
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<ol style="list-style-type: none"> <li>1. The circuit connections are made as shown</li> <li>2. connect +ve supply connected RS to green terminals</li> <li>3. connect - blue pin to blue terminal                  Red pin to red terminal     control winding                  Yellow pin to yellow terminal     of stepper motor                  Black pin to black terminal</li> <li>4. Connect the terminals of firing circuit from logic controller to MOSFET gate terminal as shown below.             <ol style="list-style-type: none"> <li>A. For clockwise direction G1 to G1                        G2 to G2                        G3 to G3                        G4 to G4</li> <li>B. For anticlockwise direction G1 to G4                        G2 to G3                        G3 to G2                        G4 to G1</li> </ol> </li> <li>5. Stepper motor rotates at <math>1.8^\circ \pm 0.1^\circ</math> for each step non cumulative.</li> <li>6. The frequency of logic switches is measured at any one gate o/p terminal.</li> <li>7. The actual frequency is given by <math>4 * \text{measured frequency}</math></li> <li>8. The RPM measured are noted down N-m</li> </ol>

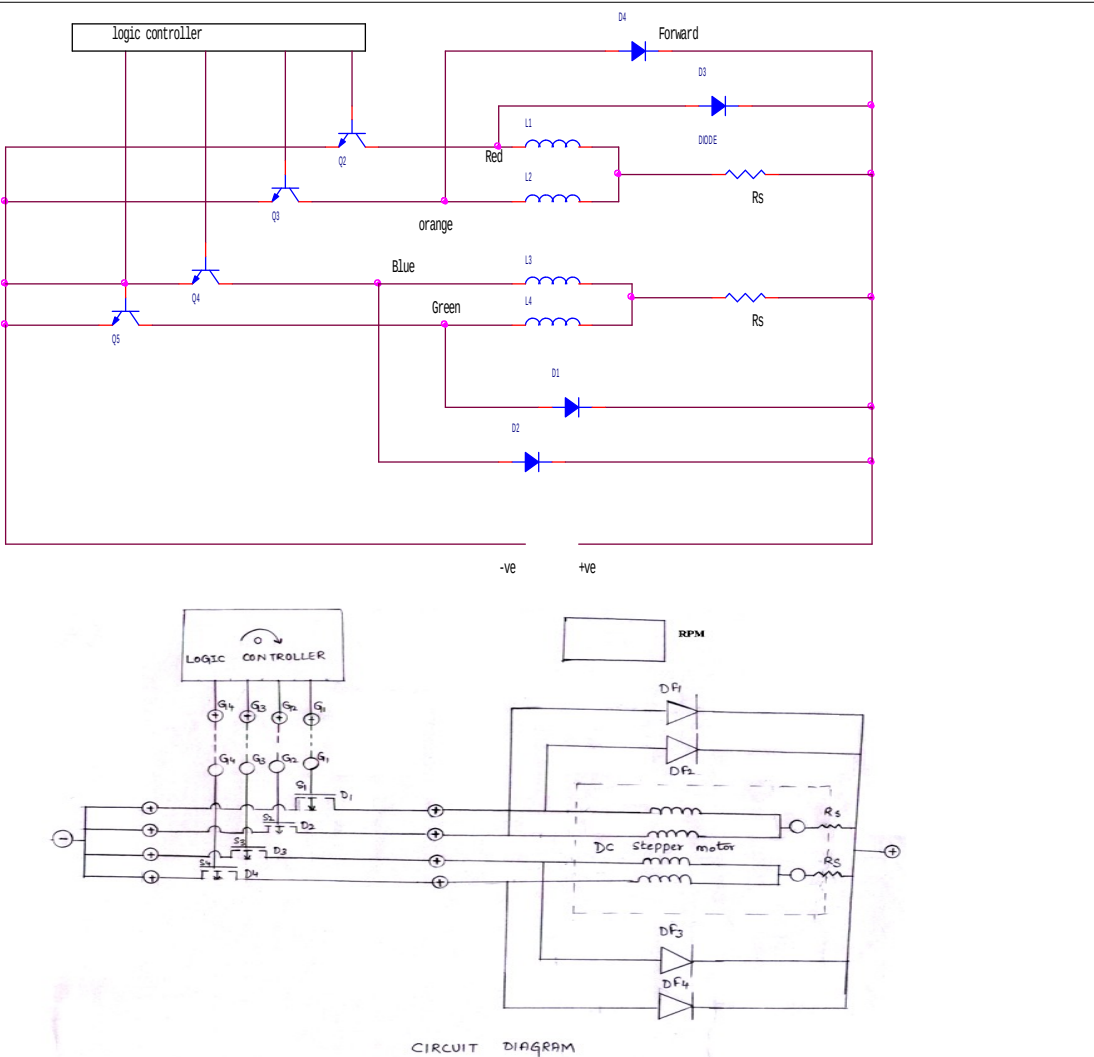9. The speed can also be calculated as follow N-actual.

7 Block, Model, Reaction Equation, Expected Graph



8 Observation Table, Look-up Table, Output

Frequency	Speed in RPM	N actual (Theoretical) RPM	Time in sec

9 Sample Calculations

F=Frequency  
 Step per revolution=200  
 RPM Actual=  $(4 \cdot F \cdot 60) / 200$  in rotation / min.

10 Graphs, Outputs



EXPECTED WAVEFORMS:

		<p>The diagram shows four pulse trains labeled G<sub>1</sub>, G<sub>2</sub>, G<sub>3</sub>, and G<sub>4</sub>. Each pulse train has a period T. Below the pulses is a graph with the vertical axis labeled 'N in RPM' and the horizontal axis labeled 'Frequency in Hz'. A straight line is drawn on the graph, indicating a linear relationship between speed and frequency.</p>
11	Results & Analysis	The variation of speed control of DC stepper motor so observed.
12	Application Areas	Stepper motors are used for precise positioning with a motor such as hard disc drives, robotics, antennas, telescopes etc
13	Remarks	
14	Faculty Signature with Date	

### Experiment 10 : Speed Control of universal motor using AC voltage regulator

-	Experiment No.:	10	Marks		Date Planned		Date Conducted	
1	Title	Speed Control of universal motor using AC voltage regulator						
2	Course Outcomes	Control the speed of universal motor using controlled rectifier or AC voltage controller						
3	Aim	1. To observe the variations of speed of AC Motor 2. To plot speed Vs RMS current and speed Vs rms volt.						
4	Material Equipment Required	/ Lab Manual						
5	Theory, Formula, Principle, Concept							
6	Procedure, Program, Activity, Algorithm, Pseudo Code	1. Connections are made as shown. 2. DRB resistance is varied in steps and at each step rms values of load current & load volt are noted. 3. At each setting of DRB. The speed in rpm is also measured using a tachometer. 4. The speed variation is observed for variation in DRB resistance.						

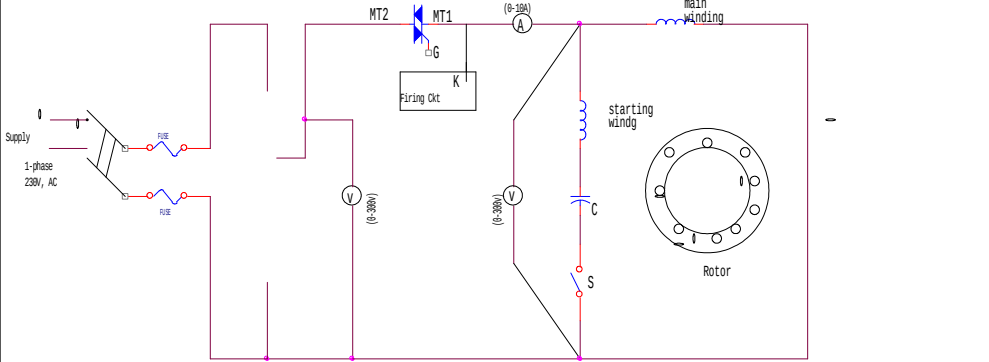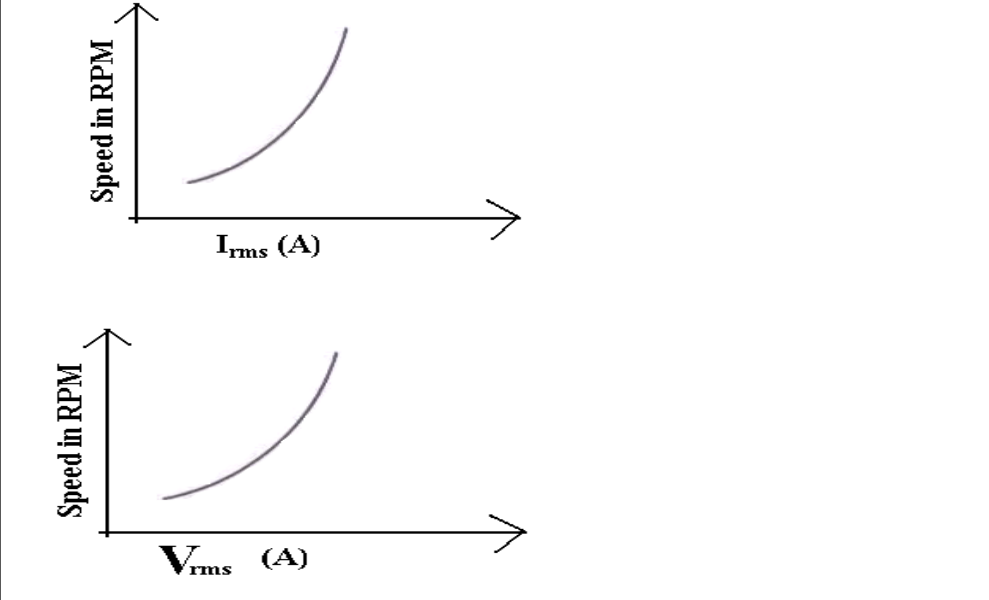

7	Block, Model, Reaction Equation, Expected Graph	<p>5. graphs of speed Vs <math>I_{rms}</math> &amp; N Vs <math>V_{rms}</math> are plotted</p> 
8	Observation Table, Look-up Table, Output	
9	Sample Calculations	
10	Graphs, Outputs	<p>Expected waveforms:</p> 
11	Results & Analysis	The variation of speed of AC motor is observed and corresponding graphs are plotted
12	Application Areas	Universal motors are used in portable power tools and equipments, house hold applications.
13	Remarks	
14	Faculty Signature with Date	

**Experiment 11 : Speed control of separately excited DC motor using an IGBT or MOSFET chopper**

-	Experiment No.:	11	Marks	Date	Date	
---	-----------------	----	-------	------	------	--

				Planned	Conducted
1	Title	Speed control of separately excited DC motor using an IGBT or MOSFET chopper			
2	Course Outcomes	Control the speed of a separately excited DC motor using MOSFET chopper by varying duty cycle of the thyristor.			
3	Aim	To construct a chopper circuit and study its time ratio (TRC) controls.			
4	Material Equipment Required	/Lab Manual MOSFET chopper Module DC Motor			
5	Theory, Formula, Principle, Concept	$(\delta) = (T_{ON} / T)$			
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<ol style="list-style-type: none"> <li>1. Circuit connections are made as shown in the circuit in the diagram by connecting field of the motor to field supply of the chopper power unit and armature of the motor to load points in the chopper.</li> <li>2. The gate and source terminal of the power switch /MOSFET is connected to the respective firing signal.</li> <li>3. Keep input DC voltage at 100 to 200v</li> <li>4. Check all the connections and confirm whether the connections made are correct before switching on the equipment.</li> <li>5. Switch on the chopper unit and also DC power supply to the chopper.</li> <li>6. Keeping frequency constant vary duty cycle of corresponding load voltage for each step.</li> <li>7. The output waveforms are seen on the CRO.</li> <li>8. Tabulated load speed of the motor for different duty cycles.</li> </ol>			
7	Block, Circuit, Model Diagram, Reaction Equation, Expected Graph				
8	Observation Table, Look-up Table, Output	LOAD VOLTAGE	CURRENT (A)	SPEED IN RPM	DUTY CYCLE IN % <b>δ</b>
9	Sample Calculations				
10	Graphs, Outputs				

11	Results & Analysis	DC chopper is constructed and its performance is studied.
12	Application Areas	Choppers are used in railway traction, battery charges, switched capacitance filters, variable frequency drives, class D electronic amplifiers, battery operated electric cars.
13	Remarks	
14	Faculty Signature with Date	

## Experiment 12 : Design of Snubber circuit

-	Experiment No.:	12	Marks		Date Planned		Date Conducted	
1	Title	Design of Snubber circuit						
2	Course Outcomes	Design the snubber circuit for the protection of power circuit from faults						
3	Aim	<b>Design of Snubber Circuit.</b>						
4	Material Equipment Required	/ Lab Manual SCR Resistor Capacitor						
5	Theory, Formula, Principle, Concept	$dv/dt = 0.632V_s/R_s C_s$ Where $R_s C_s$ is the Snubber time constant. $R_s = V_s / I_{TD}$ Where $I_{TD}$ is the discharging current of the capacitor. Due to overheating, over voltage, over current or excessive change in voltage or current switching devices and circuit components may fail. From over current they can be protected by placing fuses at suitable locations. Heat sinks and fans can be used to take the excess heat away from switching devices and other components. Snubber circuits are needed to limit the rate of change in voltage or current ( <b>di/dt</b> or <b>dv/dt</b> ) and over voltage during turn-on and turn-off. These are placed across the semiconductor devices for protection as well as to improve the performance. Static <b>dv/dt</b> is a measure of the ability of a thyristor to retain a blocking state under the influence of a voltage transient. These are also used across the relays and switches to prevent arcing.  These are placed across the various switching devices like transistors, thyristors, etc. Switching from ON to OFF state results the impedance of the device suddenly changes to the high value. But this allows a small current to flow through the switch. This induces a large voltage across the device. If this current reduced at faster rate more is the induced voltage across the device and also if the switch is not capable of withstanding this voltage the switch becomes burn out. So auxiliary path is needed to prevent this high induced voltage Similarly when the transition is from OFF to ON state, due to uneven distribution of the current through the area of the switch overheating will takes place and eventually it will be burned. Here also snubber is necessary to reduce the current at starting by making an alternate pat						
6	Procedure, Program, Activity, Algorithm, Pseudo Code	<ol style="list-style-type: none"> <li>Switch S is turned on at <math>t=0</math>, a step voltage is applied across SCR. This voltage will have a high <math>dv/dt</math>. The value of snubber circuit components is calculated by using formula.</li> <li>When SCR is in forward blocking state the capacitor will charge.</li> <li>Therefore voltage across SCR will increase gradually. Thus the rate of change of voltage across SCR is reduced.</li> </ol>						

		4. When SCR is turned on the charged capacitor will discharge through resistance R and SCR. Thus R limits the discharge current of the capacitor and prevents damage of SCR due to over current.																
7	Block, Circuit, Model Diagram, Reaction Equation, Expected Graph	<p>The diagram shows a series circuit. On the left, there is a DC voltage source labeled <math>V_s</math> with a '+' sign at the top and a '-' sign at the bottom. A switch labeled 'S' is connected to the positive terminal. Following the switch, there is a resistor labeled <math>R_s</math> and a capacitor labeled <math>C_s</math> connected in parallel. After the parallel combination, the circuit continues through an SCR (Silicon Controlled Rectifier) and finally a rectangular component labeled 'Load' connected to the negative terminal of the voltage source.</p>																
8	Observation Table, Look-up Table, Output	<p>For <math>dv/dt = \text{-----}</math></p> <table border="1"> <thead> <tr> <th>t=</th> <th>VA</th> </tr> </thead> <tbody> <tr><td> </td><td> </td></tr> <tr><td> </td><td> </td></tr> <tr><td> </td><td> </td></tr> <tr><td> </td><td> </td></tr> <tr><td> </td><td> </td></tr> <tr><td> </td><td> </td></tr> <tr><td> </td><td> </td></tr> </tbody> </table>	t=	VA														
t=	VA																	
9	Sample Calculations																	
10	Graphs, Outputs																	
11	Results & Analysis	For given $dv/dt$ ratings, design a snubber circuit by using the formula and observe the response of the circuit Shown by the graph																
12	Application Areas	Snubber circuits are used across the relays and switches to prevent arcing.																
13	Remarks																	
14	Faculty Signature with Date																	