

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17MAT31

## Third Semester B.E. Degree Examination, Jan./Feb. 2021 Engineering Mathematics – III

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Obtain the Fourier series of  $f(x) = x(2\pi - x)$  in  $0 \leq x \leq 2\pi$ . (08 Marks)
- b. Obtain the Fourier series for the function  $f(x) = \begin{cases} 1 + 4\frac{x}{3} & \text{in } -\frac{3}{2} < x \leq 0 \\ 1 - 4\frac{x}{3} & \text{in } 0 \leq x < \frac{3}{2} \end{cases}$  (06 Marks)
- c. Expand  $f(x) = 2x - 1$  as a Cosine half range Fourier series in  $0 < x < 1$ . (06 Marks)

### OR

- 2 a. Obtain the constant term and the coefficients of the first Cosine and Sine terms in the Fourier expansion of 'y' from the table

x	0	1	2	3	4	5
y	9	18	24	28	26	20

- b. Obtain the Fourier series of  $f(x) = |x|$  in  $-\pi \leq x \leq \pi$ . (06 Marks)
- c. Show that the sine half range series for the function  $f(x) = lx - x^2$  in  $0 < x < l$  is

$$\frac{8l^2}{\pi^3} \sum_0^{\infty} \frac{1}{(2n+1)^3} \sin\left(\frac{2n+1}{l}\pi x\right) \pi x. \quad (06 \text{ Marks})$$

### Module-2

- 3 a. If  $f(x) = \begin{cases} 1 & \text{for } |x| \leq a \\ 0 & \text{for } |x| > a \end{cases}$ , find the infinite Fourier transform of  $f(x)$  and hence evaluate  $\int_0^{\infty} \frac{\sin x}{x} dx$ . (08 Marks)
- b. Find the Fourier Cosine transform of  $e^{-x}$ . (06 Marks)
- c. Solve by using Z-transforms:  $y_{n+2} - 4y_n = 0$ , given  $y_0 = 0$  and  $y_1 = 2$ . (06 Marks)

### OR

- 4 a. Find the Fourier Sine transform of  $\frac{e^{-ax}}{x}$ ,  $a > 0$ . (08 Marks)
- b. Find the Z-transform of  $\sin(3n + 5)$ . (06 Marks)
- c. Find the inverse Z-transform of  $\frac{2z^2 + 3z}{(z+2)(z-4)}$ . (06 Marks)

**Module-3**

- 5 a. Find the coefficient of correlation for the data

x	1	3	4	2	5	8	9	10	13	15
y	8	6	10	8	12	16	16	10	32	32

(08 Marks)

- b. Fit a straight line to the following data

Year	1961	1971	1981	1991	2001
Production ( in tons)	8	10	12	10	16

(06 Marks)

- c. Compute the real root of
- $x \log_{10} x - 1.2 = 0$
- by Regula - Falsi method. Carry out three iterations in (2, 3).

(06 Marks)

**OR**

- 6 a. Obtain the lines of Regression for the following values of x and y

x	1	2	3	4	5
y	2	5	3	8	7

(08 Marks)

- b. Fit an exponential curve of the form
- $y = ae^{bx}$
- for the following data

No. of petals	5	6	7	8	9	10
No. of flowers	133	55	23	7	2	2

(06 Marks)

- c. Find a real root of
- $x \sin x + \cos x = 0$
- near
- $x = \pi$
- . Correct to four decimal places, using Newton - Raphson method.

(06 Marks)

**Module-4**

- 7 a. Given
- $\sin 45^\circ = 0.7071$
- ,
- $\sin 50^\circ = 0.7660$
- ,
- $\sin 55^\circ = 0.8192$
- ,
- $\sin 60^\circ = 0.8660$
- , find
- $\sin 57^\circ$
- using an appropriate interpolation formula.

(08 Marks)

- b. Use Newton's divided difference formula to find
- $f(4)$
- given the data

x	0	2	3	6
f(x)	-4	2	14	158

(06 Marks)

- c. Using Simpsons
- $1/3^{\text{rd}}$
- rule, evaluate
- $\int_0^{\pi/2} \sqrt{\cos \theta} d\theta$
- by dividing
- $[0, \pi/2]$
- into 6 equal parts.

(06 Marks)

**OR**

- 8 a. From the following table find the number of students who have obtained less than 45 marks

Marks	30-40	40-50	50-60	60-70	70-80
No. of Students	31	42	51	35	31

(08 Marks)

- b. Using Lagrange's interpolation formula fit a polynomial of the form
- $x = f(y)$

x	2	10	17
y	1	3	4

(06 Marks)

- c. Evaluate
- $\int_0^1 \frac{x}{1+x^2} dx$
- by Weddle's rule taking seven ordinates.

(06 Marks)

Module-5

- 9 a. Verify Green's theorem in a plane for  $\oint_C (3x^2 - 8y^2)dx + (4y - 6xy)dy$ , where 'C' is the boundary of the region enclosed by  $y = \sqrt{x}$  and  $y = x^2$ . (08 Marks)
- b. Verify Stoke's theorem for  $\vec{F} = (x^2 + y^2)\mathbf{i} - 2xy\mathbf{j}$  taken round the rectangle bounded by the lines  $x = \pm a$ ,  $y = 0$  and  $y = b$ . (06 Marks)
- c. Derive Euler's equation  $\frac{\partial t}{\partial y} - \frac{d}{dx} \left[ \frac{\partial t}{\partial y'} \right] = 0$ . (06 Marks)

OR

- 10 a. Use Gauss divergence theorem to evaluate  $\iiint_S \vec{E} \cdot \hat{n} ds$  over the entire surface of the region above  $xy$  plane bounded by the cone  $z^2 = x^2 + y^2$  the plane  $z = 4$  where  $\vec{F} = 4xz\mathbf{i} + xyz^2\mathbf{j} + 3z\mathbf{k}$ . (08 Marks)
- b. Prove that geodesics of a plane are straight lines. (06 Marks)
- c. Find the extremal of the functional  $\int_0^{\pi/2} (y^2 - y'^2 - 2y \sin x) dx$  under the end conditions  $y(0) = y(\pi/2) = 0$ . (06 Marks)

\*\*\*\*\*

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC32

Third Semester B.E. Degree Examination, Jan./Feb. 2021

## Electronic Instrumentation

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- Define the following with examples : i) Accuracy ii) Precision iii) Resolution  
iv) Significant figures v) Absolute error. (05 Marks)
  - Explain basic DC Ammeter and design multirange ammeter to measure 0-10mA, 0-2mA, 0-50mA having basic meter with full scale deflection of 1mA and internal resistance 100Ω. (10 Marks)
  - Explain true RMS voltmeter with a neat diagram. (05 Marks)

OR

- Write a short note on loading of voltmeter and find :  
i) Voltage across R2 using meter1 and meter2 in the following Fig.Q2(a)(i).

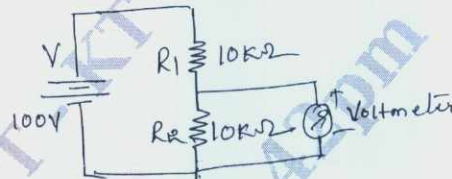


Fig.Q2(a)(i)

- ii) Which meter provides the accurate result?
- iii) Error in the voltmeters.  
Given that meter 1 : 1000Ω/V over range 50V  
meter 2 : 20000Ω/V over range 50V. (10 Marks)
- Explain AC voltmeter with full wave rectifier and compute the value of multiplier for 100Vms input for full wave rectifier voltmeter with basic meter having full scale deflection of 1mA and internal resistance 500Ω. (07 Marks)
- Write a note on measurement error combinations. (03 Marks)

### Module-2

- Explain the basic principle used in ADC. (05 Marks)
  - With the help of neat diagram, explain dual slope integrating type DVM. Mention specifications of DVM. (10 Marks)
  - Explain Digital pH-meter. (05 Marks)

OR

- Explain digital frequency meter with the help of block diagram. (10 Marks)
  - Explain digital Tachometer. (05 Marks)
  - What do you mean by 3½ digit display? Explain. What is the resolution of 3½ digit DDM over IV range and 10V range. (05 Marks)

### Module-3

- Explain the block diagram of CRO. (07 Marks)
  - Explain Digital Storage Oscilloscope. (07 Marks)
  - Explain the working of AF Sine and Square Wave Generator. (06 Marks)

OR

- 6 a. With the help of neat block diagram, explain Function Generator. (08 Marks)  
 b. Explain the working of Standard Signal Generator. (07 Marks)  
 c. Discuss frequency measurements with Lissajous figures. (05 Marks)

**Module-4**

- 7 a. Explain Q-meter with suitable circuit diagram. (08 Marks)  
 b. With neat circuit diagram explain phase meter. (08 Marks)  
 c. Obtain the balance equations for capacitance comparison bridge. (04 Marks)

OR

- 8 a. Explain the Wheat Stone bridge and using Thevenin's theorem, determine the amount of deflection due to unbalance of Wheat Stone bridge. (10 Marks)  
 b. In the following Fig.Q8(b) ratio of  $R_a$  to  $R_b$  is  $1000\Omega$ ,  $R_1 = 5\Omega$ ,  $R_1 = 0.5R_2$ . Find  $R_x$ .

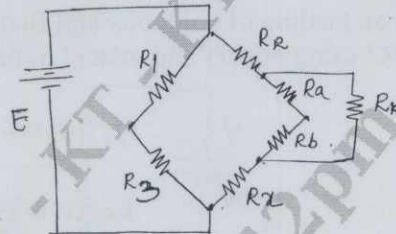


Fig.Q8(b)

- c. Explain Megger circuit. (05 Marks)

**Module-5**

- 9 a. What are the factors to be considered while selecting a better transducer? Explain. (08 Marks)  
 b. Explain LVDT and show characteristic curve along with its applications. (07 Marks)  
 c. Explain Piezoelectric transducer. (05 Marks)

OR

- 10 a. Explain Semiconductor photodiode and transistor. (07 Marks)  
 b. What is resistance thermometer? Explain. (06 Marks)  
 c. A displacement transducer with a shaft stroke of 3.0 inch is applied to the following circuit shown in Fig.Q10(c). The total resistance of potentiometer is  $5K\Omega$ , applied voltage is 5V. When the Wiper is 0.9 inch from B, what is the total output voltage?

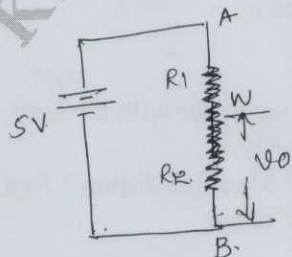


Fig.Q10(c)

(07 Marks)

\*\*\*\*\*

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC33

## Third Semester B.E. Degree Examination, Jan./Feb. 2021 Analog Electronics

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. What is BJT transistor modeling? Obtain the expression for voltage gain,  $Z_{in}$  and  $Z_o$  of CB configuration using AC equivalent circuit with  $r_e$  model. (05 Marks)
- b. Derive the expression for  $A_i$ ,  $A_v$ ,  $Z_i$  and  $Z_o$  for a voltage divider bias circuit of BJT, with unbypassed  $R_E$ , using  $r_e$  equivalent model of BJT. Show the phase relationship between input and output wave form. (10 Marks)
- c. State the characteristic features of Darlington connection. Calculate the DC bias voltages and currents in the circuit.

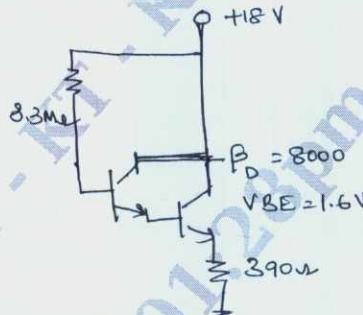


Fig.Q1(c)

(05 Marks)

OR

- 2 a. Give the relation between  $r_e$  parameters and  $h$  parameters. What are the advantages of  $h$  parameters? (05 Marks)
- b. Derive the expressions for current gain, voltage gain, input impedance and output impedance for an emitter follower circuit using approximate hybrid equivalent circuit. (Without the effect of  $r_o$ ). (10 Marks)
- c. For the network shown in Fig.Q2(c), determine  $r_e$ ,  $Z_i$ ,  $Z_o$ ,  $A_v$  (with  $r_o = \infty\Omega$ ) and  $A_v$  (with  $r_o = 50\text{ K}\Omega$ )

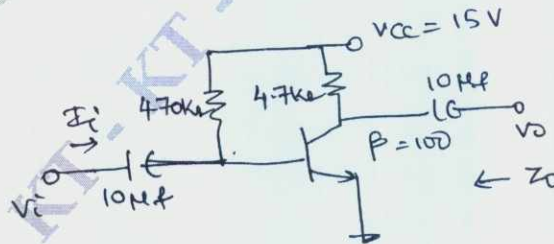


Fig.Q2(c)

(05 Marks)

### Module-2

- 3 a. Explain the construction of N channel JFET. Also explain the drain and transfer characteristics of the JFET. (06 Marks)
- b. With equivalent circuit obtain the expression for  $Z_o$  and  $A_v$  for JFET self bias configuration. (08 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

- c. The fixed bias configuration shown in Fig.Q3(c) has  $V_{GSQ} = -2V$ ,  $I_{DQ} = 5.625 \text{ mA}$  with  $I_{DSS} = 10 \text{ mA}$ ,  $V_P = -8V$  and  $Y_{OS} = 40 \mu S$ . Determine  $g_m$ ,  $r_{ds}$ ,  $Z_o$  and  $A_v$ .

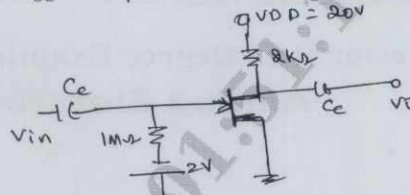


Fig.Q3(c)

(06 Marks)

OR

- 4 a. Differentiate between enhancement and depletion MOSFET. (05 Marks)  
 b. With necessary equivalent circuit, obtain the expression for  $A_v$  for a JFET source follower configuration. (05 Marks)  
 c. Calculate the DC bias, voltage gain, input impedance and output impedance and resulting output voltage for the cascade amplifier shown in Fig.Q4(c). Calculate the load voltage if a 10 KΩ load is connected across the output.

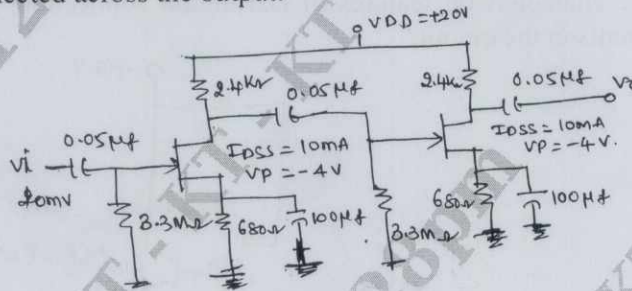


Fig.Q4(c)

(10 Marks)

**Module-3**

- 5 a. Determine the lower cutoff frequency  $f_{LS}$  for the voltage divider bias network using the following parameters:  
 $C_S = 10 \mu f$ ,  $C_E = 20 \mu f$ ,  $C_C = 1 \mu f$ ,  $R_S = 1 \text{ K}\Omega$ ,  $R_1 = 40 \text{ K}\Omega$ ,  $R_2 = 10 \text{ K}\Omega$ ,  $R_E = 2 \text{ K}\Omega$ ,  $R_C = 4 \text{ K}\Omega$ ,  $R_L = 2.2 \text{ K}\Omega$ ,  $\beta = 100$ ,  $r_o = \infty \Omega$ ,  $V_{CC} = 20 \text{ V}$ ,  $r_e = 15.76 \Omega$ . (04 Marks)  
 b. Explain the following: (i) Logarithm (ii) Decibel. With respect to transistor amplifier calculate the overall lower 3 dB and upper 3 dB frequencies for a 3 stage amplifier having an individual  $f_1 = 40 \text{ Hz}$  and  $f_2 = 2 \text{ MHz}$ . (06 Marks)  
 c. Discuss the low frequency response of BJT amplifier and give expression for lower cut off frequency due to  $C_C$ ,  $C_E$  and  $C_S$ . (10 Marks)

OR

- 6 a. Draw the Hybrid  $\pi$  model for the transistor in CE configuration and explain the significance of each component. (06 Marks)  
 b. Describe the Miller effect and derive an equation for Miller input capacitance. (06 Marks)  
 c. Determine the high cutoff frequencies for the network shown in Fig.Q6(c).

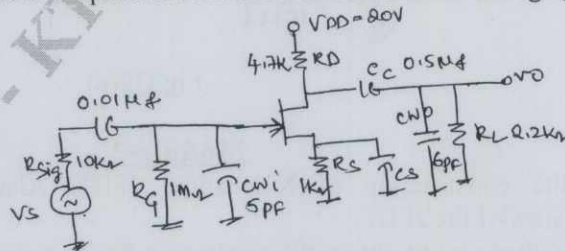


Fig.Q6(c)

(08 Marks)

**Module-4**

- 7 a. With a block diagram, explain the concept of feedback amplifier and derive the expression for  $A_f = \frac{A}{1 + A\beta}$ . (06 Marks)
- b. Derive the expression for  $Z_{if}$  and  $Z_{of}$  for current series feedback amplifier. (08 Marks)
- c. Explain a practical voltage series feedback circuit. (06 Marks)

**OR**

- 8 a. What is an oscillator? Discuss the concept of generating oscillations with the help of Barkhausen criteria. (05 Marks)
- b. With a neat circuit diagram and necessary expressions, explain the Wein bridge oscillator. (10 Marks)
- c. Design a unijunction transistor for a operation at 1 kHz and 150 kHz assuming  $\eta = 0.58$ . (05 Marks)

**Module-5**

- 9 a. Give the definition of power amplifiers and list the types of power amplifiers based on the location of Q point. (05 Marks)
- b. Explain the working of class B complementary symmetry class B push pull amplifier. Obtain an expression for maximum conversion efficiency of this amplifier. (10 Marks)
- c. Calculate the harmonic distortion components for an output signal having fundamental amplitude of 2.5 V, second harmonic amplitude of 0.25 V, third harmonic amplitude of 0.1 V and fourth harmonic amplitude of 0.05 V and also calculate the total harmonic distortion for the amplitude components given above. (05 Marks)

**OR**

- 10 a. With necessary circuit diagram and characteristic curve, explain the class-A transformer coupled amplifier. Show that the maximum efficiency can be expressed as 50%. (10 Marks)
- b. Describe the block diagram of series and shunt type voltage regulators. (05 Marks)
- c. Calculate the output voltage and Zener current in the regulator circuit of Fig.Q10(c) for  $R_L = 5 \text{ K}\Omega$ .

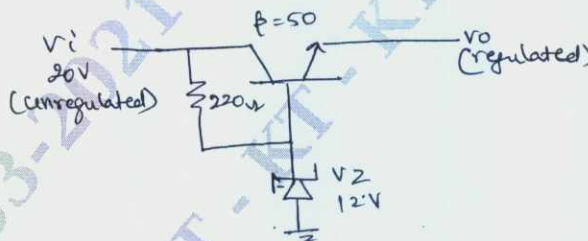


Fig.Q10(c)

(05 Marks)

\*\*\*\*\*



# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC34

## Third Semester B.E. Degree Examination, Jan./Feb. 2021 Digital Electronics

Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

### Module-1

- 1 a. Define the following:
- Combinational circuit
  - Sequential circuit
  - Canonical SOP
  - Canonical POS
  - Prime Implicant
  - Essential prime implicant. (08 Marks)
- b. Express the following equations into decimal notations:
- $H = f(A, B, C) = A'BC + A'BC + ABC$
  - $T = f(a, b, c) = (a + b' + c)(a + b' + c')(a' + b' + c)$  (08 Marks)
- c. Write mirror image version 5-variable K-map. (04 Marks)

### OR

- 2 a. Obtain minimal expression using k-map for the following incompletely specified function  $F(a, b, c, d) = \sum m(0, 1, 4, 6, 7, 9, 15) + \sum d(3, 5, 11, 13)$  and draw circuit diagram using gates. (10 Marks)
- b. Simplify the following using Quine-Mcclusky method  
 $s = f(w, x, y, z) = \sum(1, 3, 13, 15) + \sum d(8, 9, 10, 11)$  (10 Marks)

### Module-2

- 3 a. Explain the analysis and design procedure for combinational circuit with example. (10 Marks)
- b. Implement full subtractor using 3:8 decoder and write truth table. (10 Marks)

### OR

- 4 a. Design full adder using i) 8:1 MUX ii) 4:1 MUX. (10 Marks)
- b. Design 4 to 16 decoder using 3 to 8 decoder. (05 Marks)
- c. Explain look ahead carry adder and give its advantages and disadvantages. (05 Marks)

### Module-3

- 5 a. What is flipflop? Discuss working principle of SR flipflop with its TT and write characteristics equations. (10 Marks)
- b. Sketch timing diagram for JK flipflop and D-flipflop. (05 Marks)
- c. Explain the operation of a switch debouncer built using SR-latch with the help of waveforms. (05 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Explain the working of a master-slave JK flip-flop with timing diagram. Show how race around condition is eliminated. (10 Marks)  
 b. Explain setup time, hold time and propagation delay for timing considerations. (05 Marks)  
 c. Write characteristics equation for D and T flip-flop. (05 Marks)

**Module-4**

- 7 a. Explain with diagram, operation and waveforms Serial In Serial Out (SISO) shift left mode register. (10 Marks)  
 b. Design BCD ripple counter using JK flip-flop. (10 Marks)

OR

- 8 a. Design an synchronous mod 5 counter using JK flip-flop and draw its timing diagram. (10 Marks)  
 b. Explain ring counter with timing sequence. (05 Marks)  
 c. Write a note on Johnson counter. (05 Marks)

**Module-5**

- 9 a. Draw and explain the block diagram of Moore and Mealy model with example and also compare both. (10 Marks)  
 b. Define, present state, next state, state diagram state table and state assignment. (05 Marks)  
 c. Draw and explain Moore JK-flipflop state diagram. (05 Marks)

OR

- 10 a. Analyze the synchronous sequential circuit show below in Fig.Q.10(a).

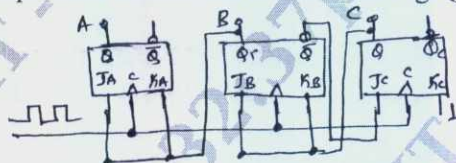


Fig.Q.10(a)

- b. Design a synchronous counter using JK flipflops to count the sequence 0, 1, 2, 4, 5, 6, 0, 1, 2. Use state diagram and state table. (12 Marks)  
 (08 Marks)

\*\*\*\*\*

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC35

## Third Semester B.E. Degree Examination, Jan./Feb. 2021 Network Analysis

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. Define controlled source and mention its types. Also, mention its applications. (05 Marks)  
 b. Using source shift and source transformations, determine the voltage across the current source in Fig Q1(b).

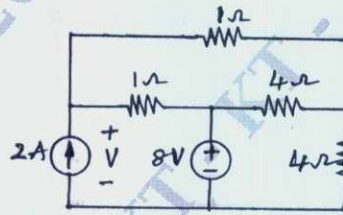


Fig Q1(b)

(05 Marks)

- c. For the circuit of Fig Q1(c), use nodal analysis to determine the voltage labeled  $V_x$ .

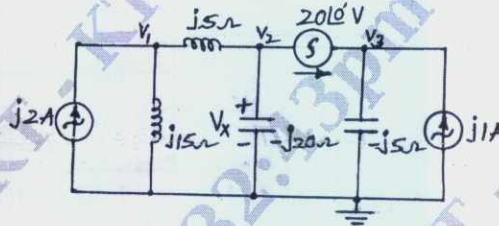


Fig Q1(c)

(10 Marks)

OR

- 2 a. Define and explain supermesh. (04 Marks)  
 b. Use Star-Delta transformations to find the equivalent resistance at AB in Fig Q2(b).

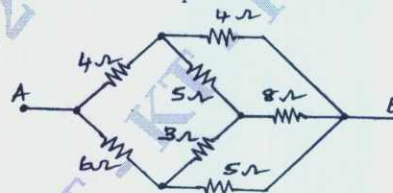


Fig Q2(b)

(06 Marks)

- c. Use Mesh analysis to determine  $V_1$  and the power being supplied by the dependent current source in the circuit shown in Fig Q2(c).

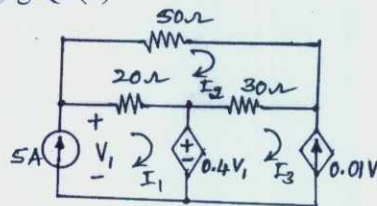


Fig Q2(c)

(10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

**Module-2**

- 3 a. State and explain Millman's theorem for AC circuit. (05 Marks)  
 b. Use superposition on the circuit shown in Fig Q3(b) to find the current  $i_x$ .

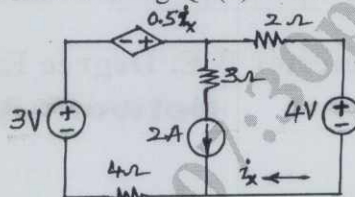


Fig Q3(b)

(05 Marks)

- c. Use Norton's theorem for the circuit of Fig Q3(c) to determine the power absorbed by the 20Ω resistor.

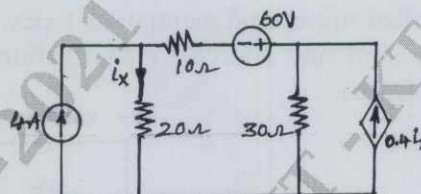


Fig Q3(c)

(10 Marks)

OR

- 4 a. State and prove maximum power transfer theorem for AC voltage source with internal impedance connected to variable impedance. (06 Marks)  
 b. Verify reciprocity theorem for the circuit of Fig Q4(b).

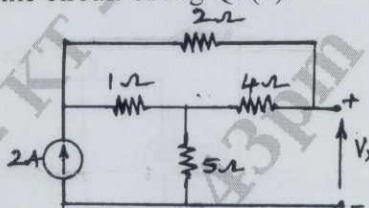


Fig Q4(b)

(04 Marks)

- c. For the circuit of Fig Q4(c), what value of  $R_L$  will absorb a maximum average power, and what is the value of this power?

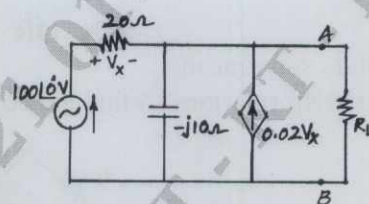


Fig Q4(c)

(10 Marks)

**Module-3**

- 5 a. Explain the behavior of R, L and C elements for transients. Mention their representation at  $t = 0^+$  (06 Marks)  
 b. In the network of the Fig Q5(b), is in the steady state with the switch K closed. At  $t = 0$ , the switch is opened. Find the values of  $v_1$ ,  $v_2$ ,  $\frac{dv_1}{dt}$  and  $\frac{dv_2}{dt}$  at  $t = 0^+$ .

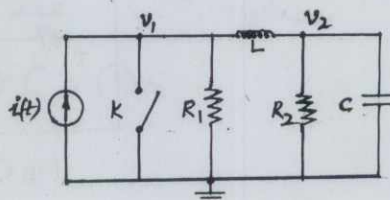


Fig Q5(b)

(08 Marks)

- c. Find the Laplace transform of the waveform shown in Fig Q5(c)

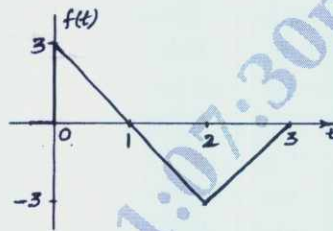


Fig Q5(c)

(06 Marks)

OR

- 6 a. In the network of the Fig Q6(a), a steady state is reached with the switch K open. AT time  $t = 0$ , the switch is closed. Find the values of  $i_1$ ,  $i_2$ ,  $\frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  at  $t = 0^+$ .

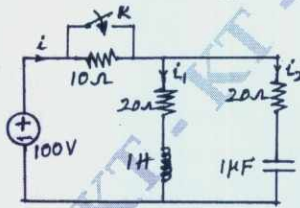


Fig Q6(a)

(10 Marks)

- b. In the network of the Fig Q6(b), the switch K is closed at  $t = 0$  a steady state having previously excited. Draw the transform network and find the current  $i(t)$ , using the Laplace transformation method.

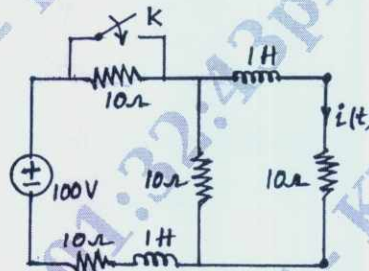


Fig Q6(b)

(10 Marks)

**Module-4**

- 7 a. In a series resonant circuit, show that resonant frequency is equal to the geometric mean of half-power frequencies. (06 Marks)
- b. An R-L-C series circuit of  $8\Omega$  resistance should be designed to have a bandwidth of 50Hz. Determine the values of L and C, so that the system resonates at 250Hz. Also determine the half power frequencies. (06 Marks)
- c. For the network shown in Fig Q7(c), determine the value of C at which it resonates when  $f = 100\text{Hz}$ . Also find the values of  $R_L$  and  $R_C$  at which the circuit resonates at all frequencies.

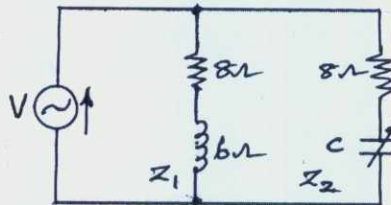


Fig Q7(c)

(08 Marks)

OR

- 8 a. Define the following terms pertaining to a series R-L-C circuit, i) Resonance ii) Quality factor iii) Bandwidth iv) Selectivity. (04 Marks)
- b. A series R-L-C circuit with an input voltage  $5 \angle 0^\circ \text{V}$  resonates at a frequency of  $8400 \text{Hz}$ . The peak value of current is  $500 \text{mA}$  at resonance and the bandwidth is  $120 \text{Hz}$ . Determine the values of R, L, C and cut-off frequencies. (06 Marks)
- c. For the network shown in Fig Q8(c), determine: i) Resonance frequency ii) Input admittance iii) Quality factor iv) Bandwidth and v) half power frequencies.

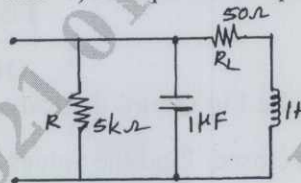


Fig Q8(c)

(10 Marks)

**Module-5**

- 9 a. Obtain Y-parameters in terms of z-parameters. (06 Marks)
- b. Find hybrid parameters for the two part shown in Fig Q9(b). What value of K in the two-part of figure shown will produce reciprocal network.

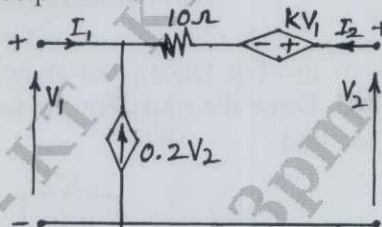


Fig Q9(b)

(06 Marks)

- c. Determine the ABCD parameters for the network of Fig Q9(c).

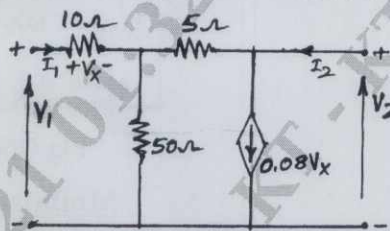


Fig Q9(c)

(08 Marks)

OR

- 10 a. Explain h-parameters with equivalent circuit. Also obtain t-parameters in terms of h-parameters and hence show that  $AD - BC = 1$ . (10 Marks)
- b. Find the Z-parameters and the Y-parameters for the network of Fig Q10(b)

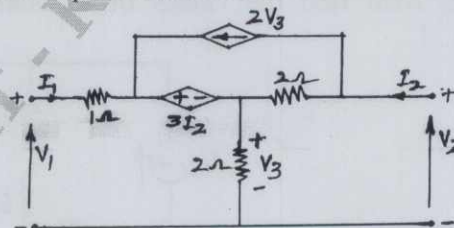


Fig Q10(b)

(10 Marks)

\*\*\*\*\*

# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17EC36

## Third Semester B.E. Degree Examination, Jan./Feb. 2021 Engineering Electromagnetics

Time: 3 hrs.

Max. Marks: 100

**Note:** Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1 a. State and explain Coulomb's Law in vector form. (04 Marks)  
b. Derive the expression for electric field intensity due to infinite line charge. (08 Marks)  
c. Let a point charge  $Q_1 = 25\text{nc}$  be located at  $A(4, -2, 7)$  and a charge  $Q_2 = 60\text{nc}$  be at  $B(-3, 4, -2)$ . Find  $\vec{E}$  at  $C(1, 2, 3)$ . Also find the direction of the electric field. Given  $\epsilon_0 = 8.854 \times 10^{-12}\text{F/M}$ . (08 Marks)

OR

- 2 a. Define electric field intensity and flux density also derive an expression for electric field intensity  $\vec{E}$  at a point due to many charges. (07 Marks)  
b. Point charges of  $50\text{nc}$  each are located at  $A(1, 0, 0)$ ,  $B(-1, 0, 0)$ ,  $C(0, 1, 0)$  and  $D(0, -1, 0)$  find the total force on the charge at A and also find  $\vec{E}$  at A. (08 Marks)  
c. A uniform line charge of infinite length with  $P_L = 40\text{nc/m}$ , lies along the Z-axis. Find  $\vec{E}$  at  $(-2, 2, 8)$  in air. (05 Marks)

### Module-2

- 3 a. State and prove Gauss Law for point charge. (06 Marks)  
b. Define potential difference and absolute potential. (04 Marks)  
c. In the given relation  $D = 4xy\hat{a}_x + 2(x^2 + y^2)\hat{a}_y + 4yz\hat{a}_z \text{ c/m}^2$ . Evaluate both sides of the divergence theorem and find the charge enclosed within the rectangular parallelepiped  $(0 \leq x \leq 2)$ ,  $(0 \leq y \leq 3)$  and  $(0 \leq z \leq 5)\text{m}$ . (10 Marks)

OR

- 4 a. State and prove divergence theorem. (04 Marks)  
b. Derive point form of continuity equation for current. (08 Marks)  
c. A point charge of  $6\text{nc}$  is located at origin in free space, find potential of point P, if P is located at  $(0.2, -0.4, 0.4)$  and  
i)  $V = 0$  at infinity  
ii)  $V = 0$  at  $(1, 0, 0)$   
iii)  $V = 20\text{V}$  at  $(-0.5, 1, -1)$ . (08 Marks)

### Module-3

- 5 a. State and prove uniqueness theorem. (08 Marks)  
b. By applying Laplace equation find the expression for capacitance between the two concentric spheres. Make suitable assumptions. (12 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and/or equations written eg. 42+8 = 50, will be treated as malpractice.

OR

- 6 a. Derive the expressions for Poisson's and Laplace's equation. (04 Marks)  
 b. State and explain Biot – Savart Law. (06 Marks)  
 c. Given the potential field  $V = [Ar^4 + Br^{-4}]\sin 4\phi$  :  
 i) Show that  $\nabla^2 V = 0$   
 ii) Find A and B such that  $V = 10V$  and  $\vec{E} = 500V/m$  at  $P(r = 1, \phi = 22.5^\circ, z = 2)$ . (10 Marks)

Module-4

- 7 a. Derive an expression for magnetic forces on :  
 i) Moving point charge and  
 ii) Differential current element. (10 Marks)  
 b. Two differential current elements,  
 $I_1 \Delta \vec{L}_1 = 10^{-5} \hat{a}_z$  A.M at  $P_1(1, 0, 0)$  and  
 $I_2 \Delta \vec{L}_2 = 10^{-5} (0.6 \hat{a}_x - 2 \hat{a}_y + 3 \hat{a}_z)$  A.M at  $P_2(-1, 0, 0)$   
 are located in free space. Find vector force exerted on  $I_2 \Delta \vec{L}_2 = I_1 \Delta \vec{L}_1$ . (10 Marks)

OR

- 8 a. Drive the magnetic boundary conditions at the interface between the two different magnetic materials. Discuss the conditions. (10 Marks)  
 b. A sq. loop carrying 2mA current is placed in the field of an infinite filament carrying current of 15Amp as shown in Fig.Q8(b). Find the force exerted on the sq loop.

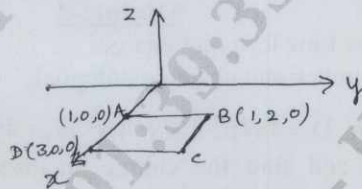


Fig.Q8(b).

(10 Marks)

Module-5

- 9 a. Write a Maxwell's equations in point form and integral form. (06 Marks)  
 b. A uniform plane wave with an intensity of electric field equal to 1 volt/m is travelling in free space. Find the magnitude of the associated magnetic field. (04 Marks)  
 c. State and explain pointing theorem. (10 Marks)

OR

- 10 a. State and explain Faraday's Law of electromagnetic induction. (04 Marks)  
 b. Starting from Maxwell's equation obtain the general wave equations in electric magnetic fields. (08 Marks)  
 c. A UPW with 10MHz frequency has average pointing vector  $1 W/m^2$  if the medium is perfect dielectric with  $\mu_r = 2$ , and  $\epsilon_r = 3$ ,  $\mu_0 = 4\pi \times 10^{-7} H/m$ ,  $\epsilon_0 = 8.854 \times 10^{-12} F/m$  ;  
 Find :  
 i) Velocity  
 ii) Wavelength  
 iii) Intrinsic impedance  
 iv) rms value of electric field. (08 Marks)

\*\*\*\*\*



# CBCS SCHEME

USN

--	--	--	--	--	--	--	--	--	--

17MATDIP31

Third Semester B.E. Degree Examination, Jan./Feb. 2021

## Additional Mathematics - I

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, choosing ONE full question from each module.

### Module-1

- 1
- Find the modulus and amplitude of  $\frac{(1+i)^2}{3+i}$ . (06 Marks)
  - If  $x + \frac{1}{x} = 2 \cos \alpha$ , then prove that  $x^n + \frac{1}{x^n} = 2 \cos n \alpha$ . (07 Marks)
  - Find the fourth roots of  $1 - \sqrt{3}$  and represent them on an argand plane. (07 Marks)

OR

- 2
- If the vectors  $2\hat{i} + \lambda\hat{j} + \hat{k}$  and  $4\hat{i} - 2\hat{j} - 2\hat{k}$  are perpendicular to each other than find the value of  $\lambda$ . (06 Marks)
  - Find the sine of the angle between the vectors  $\vec{a} = \hat{i} + \hat{j} + \hat{k}$  and  $\vec{b} = 2\hat{i} - 3\hat{j} + 2\hat{k}$ . (07 Marks)
  - Find  $\lambda$  such that the vectors  $2\hat{i} - \hat{j} + \hat{k}$ ,  $\hat{i} + 2\hat{j} - 3\hat{k}$  and  $3\hat{i} + \lambda\hat{j} + 5\hat{k}$  are coplanar. (07 Marks)

### Module-2

- 3
- Find the  $n^{\text{th}}$  derivative of  $\cos x \cos 2x \cos 3x$ . (06 Marks)
  - With usual notations prove that  $\tan \phi = r \frac{d\theta}{dr}$ . (07 Marks)
  - Prove that  $\sqrt{1 + \sin 2x} = 1 + x - \frac{x^2}{2} - \frac{x^3}{3} + \frac{x^4}{24} + \dots$  By using Maclaurin's expansion. (07 Marks)

OR

- 4
- If  $u = \tan^{-1} \left( \frac{x^3 + y^3}{x - y} \right)$ , prove that  $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = \sin 2u$ . (06 Marks)
  - If  $u = f \left( \frac{x}{y}, \frac{y}{z}, \frac{z}{x} \right)$ , prove that  $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} + z \frac{\partial u}{\partial z} = 0$ . (07 Marks)
  - If  $u = e^x \cos y$ ,  $v = e^x \sin y$ , find  $J = \frac{\partial(u, v)}{\partial(x, y)}$ . (07 Marks)

### Module-3

- 5
- Evaluate  $\int_0^{\pi} x \cos^6 x \, dx$ . (06 Marks)
  - Evaluate  $\int_0^1 \int_0^1 \frac{dx dy}{\sqrt{(1-x^2)(1-y^2)}}$ . (07 Marks)
  - Evaluate  $\int_0^1 \int_0^2 \int_1^2 x^2 y z \, dx \, dy \, dz$ . (07 Marks)

OR

- 6 a. Evaluate  $\int \sin^6 x \, dx$ . (06 Marks)
- b. Evaluate  $\iint_R (x^2 + y^2) \, dx \, dy$ , where R is the triangle bounded by the lines  $y = 0$ ,  $y = x$  and  $x = 1$ . (07 Marks)
- c. Evaluate  $\int_0^1 \int_0^1 \int_0^1 e^{x+y+z} \, dx \, dy \, dz$ . (07 Marks)

**Module-4**

- 7 a. A particle moves along a curve whose position vector is given by  $\vec{r} = \left(t - \frac{t^3}{3}\right)\hat{i} + t^2\hat{j} + \left(t + \frac{t^3}{3}\right)\hat{k}$ . Find the velocity and acceleration at  $t = 3$ . (06 Marks)
- b. Find the unit normal vector to the surface  $xy + x + zx = 3$  at  $(1, 1, 1)$ . (07 Marks)
- c. Find  $\text{div } \vec{F}$  and  $\text{curl } \vec{F}$ , where  $\vec{F} = \nabla(x^3 + y^3 + z^3 - 3xyz)$ . (07 Marks)

OR

- 8 a. A particle moves so that its position vector is given by  $\vec{r} = \cos wt \hat{i} + \sin wt \hat{j}$ , where  $w$  is a constant. Show that the velocity  $\vec{V}$  is perpendicular to  $\vec{r}$ . (06 Marks)
- b. If  $\vec{F} = (x + y + 1)\hat{i} + \hat{j} - (x + y)\hat{k}$ , show that  $\vec{F} \text{ curl } \vec{F} = 0$ . (07 Marks)
- c. Show that  $\vec{f} = (\sin y + z)\hat{i} + (x \cos y - z)\hat{j} + (x - y)\hat{k}$  is irrotational. Also find  $\phi$  such that  $\vec{f} = \nabla\phi$ . (07 Marks)

**Module-5**

- 9 a. Solve  $\frac{dy}{dx} = 1 + \frac{y}{x} + \left(\frac{y}{x}\right)^2$ . (06 Marks)
- b. Solve  $\frac{dy}{dx} + y \cot x = \sin x$ . (07 Marks)
- c. Solve  $(x^2 + y)dx + (y^3 + x)dy = 0$ . (07 Marks)

OR

- 10 a. Solve  $\frac{dy}{dx} + \frac{y}{x} = y^2x$ . (06 Marks)
- b. Solve  $(y \cos x + \sin y + y) \, dx + (\sin x + x \cos y + x) \, dy = 0$ . (07 Marks)
- c. Solve  $y^2 + x^2 \frac{dy}{dx} = xy \frac{dy}{dx}$ . (07 Marks)

\*\*\*\*\*



7. Which one of the landmark judgment passed by the Supreme Court in respect of Preamble of the Constitution
- a) Beru Bari  
b) Keshavananda Bharathi  
c) Menaka Gandhi  
d) Sonia Gandhi
8. Who is the Neutral person in the affairs of the party politics?
- a) C.M.  
b) Home Minister  
c) Finance Minister  
d) Speaker
9. Indian Constitution guarantees reservation of seats to SC and ST in
- a) Loksabha and Assembly only  
b) Loksabha only  
c) Loksabha and Rajyasabha  
d) Rajyasabha
10. India is referred to as \_\_\_\_\_ under the Indian Constitution
- a) Country  
b) Hindustan  
c) India  
d) Bharat
11. Who will preside over the joint session of both the houses of the parliament
- a) President  
b) Prime Minister  
c) Speaker  
d) Law Minister
12. What is the minimum age for becoming M.P. in Rajyasabha and Loksabha
- a) 18 & 25 years  
b) 25 & 18 years  
c) 35 & 25 years  
d) 30 & 25 years
13. The citizens can enforce their Fundamental Rights before SC under Article
- a) Art 31  
b) Art 32  
c) Art 33  
d) Art 34
14. Who quoted "Child of Today is Citizen of Tomorrow"?
- a) L. Tilak  
b) Jawaharlal Nehru  
c) B.R. Ambedkar  
d) Gandhiji
15. Who quoted "Freedom is my birth right"
- a) L. Tilak  
b) Jawaharlal Nehru  
c) Sardar Patel  
d) Gandhiji
16. No person shall be punished for same offence more than once
- a) Jeopardy  
b) Double Jeopardy  
c) Ex-post facto law  
d) Testimonial compulsion
17. When the Office of The President falls vacant the same must be filled up within
- a) 4 months  
b) 6 months  
c) 12 months  
d) 18 months
18. Which important Human Rights is protected under Article 21
- a) Right to Equality  
b) Right to Life and Personal Liberty  
c) Right to Freedom of Speech  
d) Right to Religion

19. The Rajya Sabha is  
a) Is a Permanent House  
c) Has a life of 5 years  
b) Has a life of 6 years  
d) Has a life of 7 years
20. The Quorum or minimum number of members required to hold the meetings of either houses of the Parliament is  
a) One-tenth  
c) One-third  
b) One-fifth  
d) One-fourth
21. Article 19 provides  
a) 6 freedoms  
c) 8 freedoms  
b) 7 freedoms  
d) 5 freedoms
22. One of the salient features of our Constitution is  
a) It is fully rigid  
c) It is partly rigid and partly flexible  
b) It is fully flexible  
d) None of these
23. Who is the present Speaker of Lok Sabha  
a) Sumithra Mahajan  
c) Om Birla  
b) K.S.Hegde  
d) Venkiah Naidu
24. The Chief Election Commission holds office for a period of  
a) 3 yrs  
c) 5 yrs  
b) 6 yrs  
d) 6 yrs or till he attains the age of 65 years
25. The procedure for amending the Constitution is detailed under  
a) Art 360  
c) Art 352  
b) Art 368  
d) Art 301
26. Writ of Mandamus can be issued on the ground of  
a) Non-performance of public duties  
c) Unlawful occupation of public offence  
b) Unlawful Detention  
d) None of these
27. Engineering Ethics is  
a) A macro ethics  
c) A preventive ethics  
b) Business Ethics  
d) A code of scientific rules based on ethics
28. The use of Intellectual Property of others without permission is referred as  
a) Cooking  
c) Plagiarism  
b) Stealing  
d) Trimming
29. Who appoints the Lieutenant General to Delhi  
a) Prime Minister  
c) President  
b) Home Minister  
d) Vice-President
30. The final interpreter to the Indian Constitution is  
a) Speaker of Lok Sabha  
c) President  
b) Parliament  
d) SC

\*\*\*\*\*