

USN

--	--	--	--	--	--	--	--	--	--

10MAT31

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Engineering Mathematics – III

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, selecting at least TWO questions from each part.

PART – A

- 1 a. Find the Fourier series for the function $f(x) = x + x^2$ over the interval $-\pi \leq x \leq \pi$. Hence deduce that:
- i) $\frac{\pi^2}{12} = \frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \dots$ ii) $\frac{\pi^2}{6} = \frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots$ (07 Marks)
- b. Expand the function $f(x) = x(\pi - x)$ over the interval $(0, \pi)$ in half range Fourier cosine series. (06 Marks)
- c. Find the constant term and the first two harmonics for the function $f(\theta)$ given by the following table: (07 Marks)

θ (in degrees)	0	60	120	180	240	300	360
$f(\theta)$	0.8	0.6	0.4	0.7	0.9	1.1	0.8

- 2 a. Show that the Fourier transform of the function
- $$f(x) = \begin{cases} 1 - x^2, & |x| \leq 1 \\ 0, & |x| > 1 \end{cases} \text{ is } F(\alpha) = \frac{2\sqrt{2}}{\alpha^3 \sqrt{\pi}} (\sin \alpha - \alpha \cos \alpha).$$
- Hence deduce that $\int_0^\infty \frac{\sin x - x \cos x}{x^3} dx = \frac{\pi}{4}$. (07 Marks)
- b. Find the Fourier cosine transform of $f(x) = \frac{1}{1 + x^2}$. (06 Marks)
- c. If the Fourier sine transform of $f(x)$ is given by $F_s(u) = \frac{\pi}{2} e^{-2u}$, find the function $f(x)$. (07 Marks)

- 3 a. Find the various possible solutions of two-dimensional Laplace equation by method of separation of variables. (07 Marks)
- b. Obtain the D'Alembert's solution of the wave equation $u_{tt} = c^2 u_{xx}$ subject to the conditions $u(x, 0) = f(x)$ and $\frac{\partial u}{\partial t}(x, 0) = 0$. (06 Marks)
- c. Solve the one-dimensional heat equation $c^2 u_{xx} = u_t$, $0 < x < \pi$ subject to the conditions $u(0, t) = 0$, $u(\pi, t) = 0$, $u(x, 0) = u_0 \sin x$ where u_0 is a non-zero constant. (07 Marks)

- 4 a. Find a curve of the best fit of the form $y = ax^b$ to the following data: (07 Marks)

x	1	2	3	4	5
y	0.5	2	4.5	8	12.5

- b. For conducting a practical examination, the chemistry department of a college requires 10, 12 and 7 units of 3 chemicals x, y and z respectively. The chemicals are available in 2 types of boxes: Box A and Box B. Box A contains 3, 2 and 1 units of x, y, z respectively and cost Rs.300. Box B contains 1, 2 and 2 units of x, y, z respectively and costs Rs.200. Find how many boxes of each type should be bought by the department so that the total cost is minimum. Solve graphically. (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

c. Solve the following LPP by simplex method:

Maximize $z = 2x_1 + 4x_2 + 3x_3$

Subject to the constraints $3x_1 + 4x_2 + 2x_3 \leq 60$

$2x_1 + x_2 + 2x_3 \leq 40$

$x_1 + 3x_2 + 2x_3 \leq 80$

$x_1, x_2, x_3 \geq 0$

(07 Marks)

PART – B

5 a. Use Newton-Raphson method to find an approximate root of the equation $x \log_{10} x = 1.2$ correct to 5 decimal places that is near 2.5. (07 Marks)

b. Use Relaxation method to solve the following system of linear equations:

$8x + 3y + 2z = 13$

$x + 5y + z = 7$

$2x + y + 6z = 9$

(06 Marks)

c. Find the numerically largest eigen value and the corresponding eigen vector of the matrix

$$A = \begin{bmatrix} 5 & 0 & 1 \\ 0 & -2 & 0 \\ 1 & 0 & 5 \end{bmatrix}$$

by power method taking $X^{(0)} = [1 \ 0 \ 0]^T$. Perform 6 iterations.(07 Marks)

6 a. Find the interpolating polynomial for the function $y = f(x)$ given by $f(0) = 1, f(1) = 2, f(2) = 1, f(3) = 10$. Hence evaluate $f(0.75)$ and $f(2.5)$. (07 Marks)

b. Apply Lagrange's method to find the value of x corresponding to $f(x) = 15$ from the following data: (06 Marks)

x	5	6	9	11
f(x)	12	13	14	16

c. Evaluate $\int_0^1 \frac{dx}{1+x^2}$ by using Simpson's $\frac{3}{8}$ rule dividing the interval (0, 1) into 6 equal parts.

Hence deduce the approximate value of π .

(07 Marks)

7 a. Solve the wave equation $u_{tt} = 4u_{xx}$ subject to the conditions $u(0, t) = 0, u(4, t) = 0, u_t(x, 0) = 0$ and $u(x, 0) = x(4 - x)$ by taking $h = 1, k = 0.5$ upto four steps. (07 Marks)

b. Find the numerical solution of the equation $u_{xx} = u_t$ when $u(0, t) = 0, u(1, t) = 0, t \geq 0$ and

$u(x, 0) = \sin \pi x, 0 \leq x \leq 1$. Carryout computations for two levels taking $h = \frac{1}{3}$ and $k = \frac{1}{36}$.

(07 Marks)

c. Solve Laplace's equation $u_{xx} + u_{yy} = 0$ for the following square mesh with boundary values as shown in the following Fig.Q7(c).

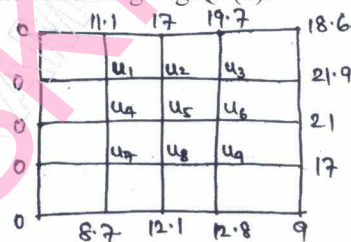


Fig.Q7(c)

(06 Marks)

8 a. Find the z-transform of $5n^2 + 4 \cos \frac{n\pi}{2} - 4^{n+2}$ and $\sinh n\theta$. (06 Marks)

b. Obtain in inverse z-transform of $\frac{z(2z+3)}{(z+2)(z-4)}$. (07 Marks)

c. Using z-transforms, solve $u_{n+2} + 3u_{n+1} + 2u_n = 3^n$ given $u_0 = 0, u_1 = 1$. (07 Marks)

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Analog Electronic Circuits

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

PART - A

- 1 a. Using Shockley's equation, determine the diode current at 25°C for a silicon diode with $I_S = 20 \text{ pA}$ and $V_D = 0.7 \text{ V}$. Find the same when $V_D = 0.5 \text{ V}$. (04 Marks)
- b. Sketch the output waveform for the following circuit shown in Fig. Q1 (b), and plot the transfer characteristics - (06 Marks)

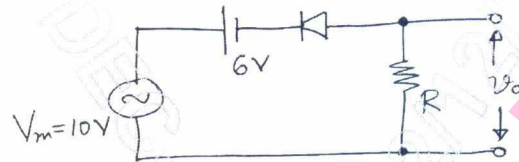


Fig. Q1 (b)

- c. Check the condition for the following circuit shown in Fig. Q1 (c) to work as clamper. Sketch the output waveform. (05 Marks)

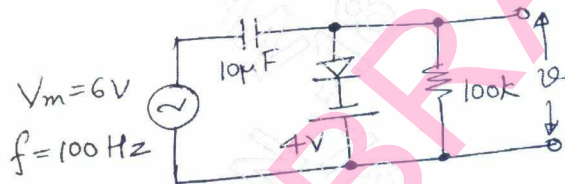


Fig. Q1 (c)

- d. Find the current in the loop, the output voltage, and the power absorbed by each device. (05 Marks)

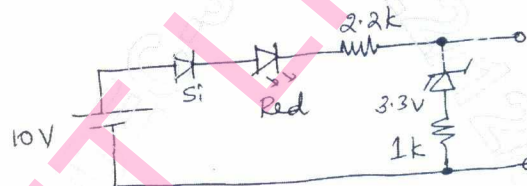


Fig. Q1 (d)

- 2 a. Derive the expression for I_B and V_{CE} of an emitter bias circuit. (04 Marks)
- b. Check the condition for the approximate analysis of the voltage-divider bias circuit and obtain the Q-point using approximate analysis, given : $V_{CC} = +12 \text{ V}$, $\beta = 120$, $R_C = 1.5 \text{ k}\Omega$, $R_E = 620 \Omega$, $R_1 = 33 \text{ k}\Omega$ and $R_2 = 4.7 \text{ k}\Omega$. Mark the Q-point on the DC load - line. (06 Marks)
- c. Determine the values for the following circuit: V_E , I_E , V_{CE} , V_C , I_B and β . (06 Marks)


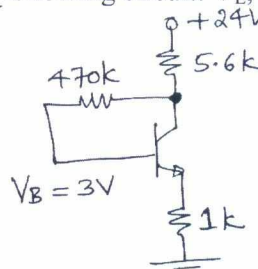


Fig. Q2 (c)

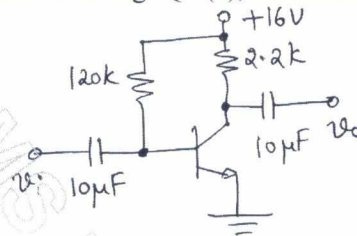- d. Design a fixed bias circuit for $V_{CC} = 10 \text{ V}$, $\beta = 120$, $I_{CQ} = 1.4 \text{ mA}$ and $V_{CEQ} = 5 \text{ V}$. (04 Marks)

- 3 a. Using r_e model, derive the expressions for Z_i , Z_o and A_v of a fixed bias circuit. (06 Marks)
 b. Using exact analysis, determine Z_i , Z_o and A_v for the voltage-divider bias network if $R_1 = 220 \text{ k}\Omega$, $R_2 = 56 \text{ k}\Omega$, $R_C = 6.8 \text{ k}\Omega$, $R_E = 2.2 \text{ k}\Omega$, $\beta = 180$, $r_o = 50 \text{ k}\Omega$ and $V_{CC} = 20\text{V}$. (10 Marks)
 c. For the network shown in Fig. Q3 (c), determine Z_i , Z_o and A_v - (04 Marks)



$h_{fe} = 150$
 $h_{ie} = 2.75 \text{ k}\Omega$
 $h_{oe} = 25 \mu\text{S}$

Fig. Q3 (c)

- 4 a. Explain the frequency response curves for RC-coupled, transformer-coupled and direct-coupled amplifiers, with reasons for the drop in gain. (09 Marks)
 b. Determine the mid-band gain and the lower cut-off frequencies f_{L_s} and f_{L_c} for the voltage-divider bias BJT amplifier with $C_s = 10 \mu\text{F}$, $C_c = 10 \mu\text{F}$, $R_s = 1 \text{ k}\Omega$, $R_1 = 36 \text{ k}\Omega$, $R_2 = 8.2 \text{ k}\Omega$, $R_E = 1.5 \text{ k}\Omega$, $R_C = 4.7 \text{ k}\Omega$, $R_L = 2.2 \text{ k}\Omega$, $\beta = 100$ and $V_{CC} = 20\text{V}$. (11 Marks)

PART - B

- 5 a. For a Darlington connection, derive the expressions for Z_i , Z_o , A_i and A_v . (12 Marks)
 b. Mention the advantages and disadvantages of the negative feedback. (04 Marks)
 c. Calculate the gain, input impedance and output impedance of a voltage-series-feedback amplifier having $A = -300$, $R_i = 1.5 \text{ k}\Omega$, $R_o = 50 \text{ k}\Omega$ and $\beta = -\frac{1}{15}$. (04 Marks)
- 6 a. Enumerate the types of power amplifiers along with their efficiency, conduction angle and Q-point. (05 Marks)
 b. Prove that the maximum efficiency of a class-B power amplifier is 78.5%. (05 Marks)
 c. Calculate the efficiency of the following circuit shown in Fig. Q6 (c), for an input current swing of 10 mA. (05 Marks)

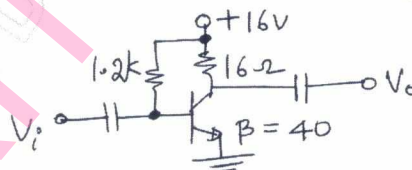


Fig. Q6 (c)

- d. Along with the circuit diagram, explain the working of Class-C amplifier. (05 Marks)
- 7 a. Along with the circuit diagram, explain the working of a BJT phase-shift oscillator. (06 Marks)
 b. Design a Wien-bridge oscillator for $f_0 = 6 \text{ kHz}$, making suitable assumptions. (06 Marks)
 c. Along with proper diagrams, explain the series resonant and parallel resonant crystal oscillators using BJT. (08 Marks)
- 8 a. Explain the operation of JFET amplifier using fixed bias. Draw the JFET small signal model, and derive the expressions for Z_i , Z_o and A_v . (10 Marks)
 b. With necessary circuit diagram, obtain the expressions for Z_i , Z_o and A_v for an E-MOSFET voltage-divider configuration. (10 Marks)

USN

--	--	--	--	--	--	--	--	--	--

10ES33

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Logic Design

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. Represent the canonical minterm forms in decimal notation :
 - i) $f_1 = x\bar{y} + yz$
 - ii) $f_2 = \bar{a}c + bc\bar{d} + ad$. (05 Marks)
- b. Show that $f(a, b, c, d) = \sum m(0, 1, 2, 5, 6, 8, 9, 10, 13, 14) = \pi M(3, 4, 7, 11, 12, 15)$. (08 Marks)
- c. Simplify the following Boolean function and realize the simplified expression using basic gates.
 $f(a, b, c, d, e) = \sum m(0, 1, 4, 8, 9, 11, 15, 16, 24, 26) + dm(10, 20, 22, 23, 25, 27, 31)$. (07 Marks)
- 2 a. Simplify the Boolean function $f(a, b, c, d) = \sum m(0, 1, 2, 7, 8, 9, 10, 13, 15)$ using Quine – Mc Cluskey tabulation method and verify the answer using k-map. (10 Marks)
- b. Simplify the Boolean function $f(a, b, c, d) = \sum m(0, 2, 3, 4, 5, 8, 10, 11) + dm(7, 13, 14)$ using Map entered variable k-map. With “d” as map entered variable, verify the answer using k-map,. (10 Marks)
- 3 a. Design a combinational circuit using basic gates to convert excess 3 binary code to BCD code. (10 Marks)
- b. Implement full adder using decoder. (05 Marks)
- c. Design a 4 to 16 decoder using 3 to 8 decoders. (05 Marks)
- 4 a. Design a 4 bit BCD adder circuit using 7483IC with self correcting circuit. That is a provision to be made in the circuit, in case the sum of BCD exceeds 9. (10 Marks)
- b. Realize the Boolean function $f(a, b, c) = \sum m(0, 1, 4, 5, 6)$ using 4 : 1 mux. (05 Marks)
- c. Explain look – ahead carry adder and give its advantages and disadvantages. (05 Marks)

PART – B

- 5 a. Obtain characteristic equation of a S-R flip-flop. (05 Marks)
- b. Explain the working of an universal shift register. (05 Marks)
- c. Explain the working of a master –slave JK flip-flop with timing diagram for master and slave. Show how race around condition is eliminated. (10 Marks)
- 6 a. Design an asynchronous mod-8 counter using JK flip-flop and draw its timing diagram. (10 Marks)
- b. Explain why asynchronous counter is called ripple counter. (05 Marks)
- c. Explain mealy and Moore sequential circuit models. (05 Marks)

- 7 a. Draw and explain Moore JK flip-flop state diagram. (05 Marks)
 b. For the state machine shown Fig.Q7(b) obtain : i) state table ii) Transition table
 iii) excitation table for JK flip-flop iv) logic diagram. (15 Marks)

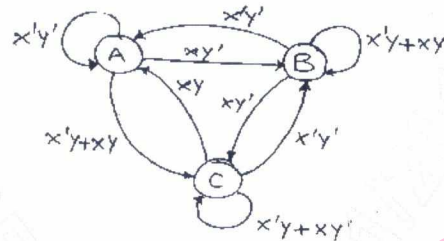


Fig.Q7(b)

- 8 a. Design a cyclic BCD up synchronous counter using τ flip-flops. (10 Marks)
 b. Design a cyclic synchronous counter using D flip-flops to generate a sequence of 5421 code.
 (Hint : 0, 1, 2, 3, 4, 8, 9, 10, 11, 12 0, 1 - - -) sequence. (10 Marks)

USN

--	--	--	--	--	--	--	--	--	--

10ES34

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Network Analysis

Time: 3 hrs.


Max. Marks:100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A

- 1 a. Define the following terms with examples :
 i) Lumped Element ii) Active Element iii) Practical Source. **(03 Marks)**
 b. Find the current I_3 using mesh analysis for the circuit shown in fig.Q1(b), if the circuit is operating at frequency 5000 rad/s. **(07 Marks)**

Fig.Q1(b)

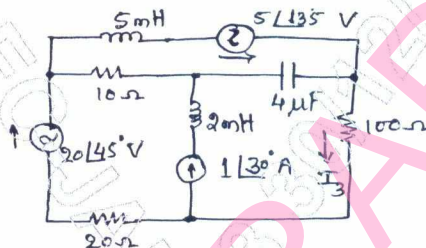


- c. For the circuit shown in fig. Q1(c), find the power delivered by dependent source using node analysis. **(06 Marks)**

Fig.Q1(c)




- d. Find the resistance R_{AB} for the network shown in fig.Q(d), using Δ - Y conversion. **(04 Marks)**

Fig.Q1(d)

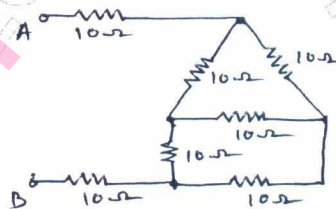


- 2 a. Define the following terms with example :
 i) Graph ii) Tree iii) Co - tree. **(03 Marks)**
 b. For the circuit in fig.Q2(b), write the tie - set matrix using AB, BC and CA or the links of the tree. Obtain the equilibrium equations in matrix from using KVL and calculate all loop currents and branch voltages. **(10 Marks)**


Fig.Q2(b)

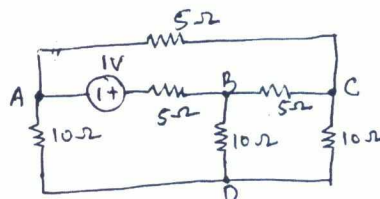

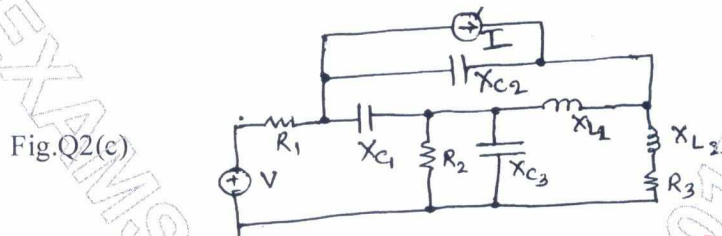
- c. Draw the oriented graph for the circuit shown in fig.Q2(c). Also find fundamental cut – set schedule using X_{c1} , R_2 and X_{L1} or the twigs of the tree. Find admittance matrix also. (04 Marks)



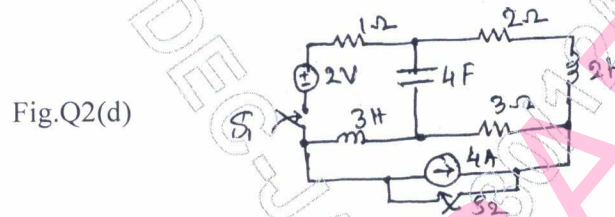
- d. Find the dual of the circuit shown in fig.Q2(d). (03 Marks)



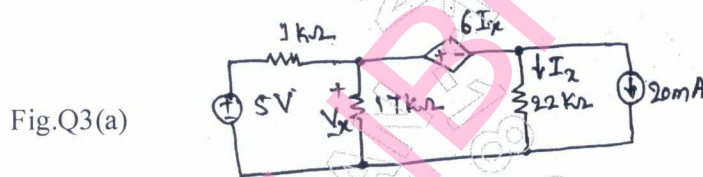- 3 a. Find V_x using superposition for the circuit shown in fig.Q3(a). (08 Marks)




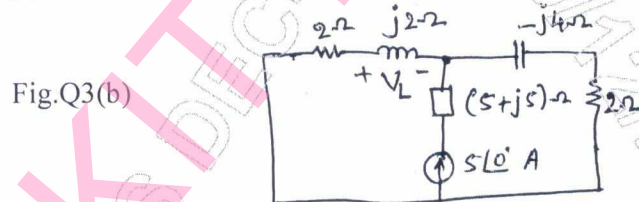- b. Find the voltage V_L across the inductor and verify reciprocity theorem for the circuit shown in Fig.Q3(b). (06 Marks)



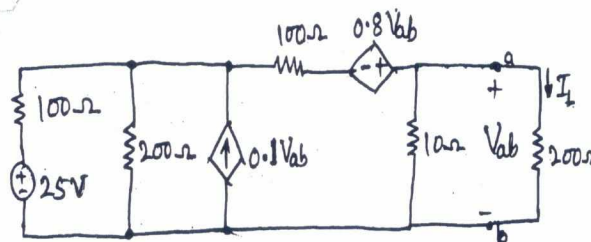- c. State and prove Milliman's theorem. (06 Marks)


- 4 a. Find the Thevenin's equivalent circuit across terminals a & b for the circuit shown in fig.Q4(a). Also find the current I_L using this equivalent circuit. (08 Marks)



- b. State and prove Norton's theorem. (05 Marks)

- c. Find Z_L for maximum power transfer for the circuit shown in fig.Q4(c). And also find the average maximum power absorbed by Z_L . (07 Marks)


Fig.Q4(c)

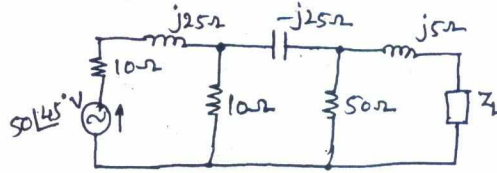

PART - B


- 5 a. For the circuit shown in fig.Q5(a), find the transfer function, resonant frequency half power frequencies, bandwidth and Q - factor. (10 Marks)

Fig.Q5(a)

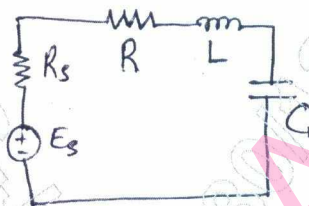


- b. Define the term Q - factor. Using this definition find the Q - factor of an inductor and a capacitor. (05 Marks)
 c. For the network shown in fig.Q5(c), find the value of C for resonance to take place at $\omega = 5000$ rad/s. (05 Marks)

Fig.Q5(c)

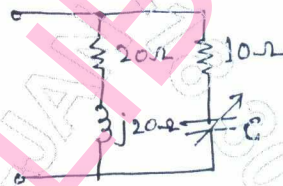


- 6 a. Write a short note on Initial and Final conditions of circuit elements under switching conditions. (06 Marks)
 b. In the circuit shown in fig.Q6(b), the switch S_1 has been open for a long time before closing at $t = 0$. Find $V_c(0^+)$, $i_L(0^+)$, $V_c(\infty)$, $i_L(\infty)$, $\frac{di_L}{dt}(0^+)$ and $\frac{d^2i_L}{dt^2}(0^+)$. (06 Marks)

Fig.Q6(b)

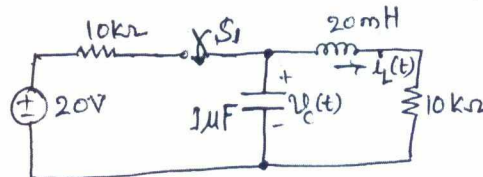


- c. For the circuit shown in fig.Q6(c), calculate $i_L(0^+)$, $\frac{di_L}{dt}(0^+)$, $\frac{d}{dt}V_c(0^+)$, $V_R(\infty)$, $V_c(\infty)$ and $i_L(\infty)$. (08 Marks)


Fig.Q6(c)

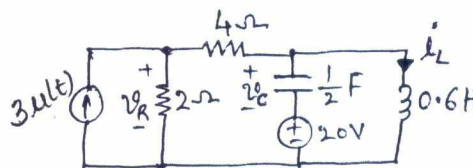

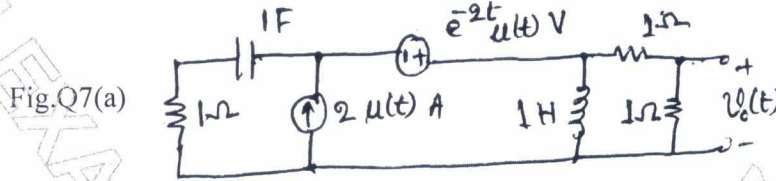
- 7 a. Find $V_o(t)$ of the circuit shown in fig.Q7(a). (10 Marks)



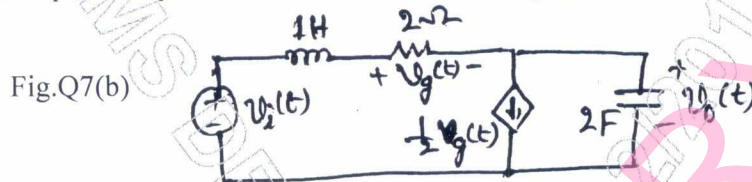
- b. Find the impulse response of the circuit shown in fig.Q7(b). (06 Marks)



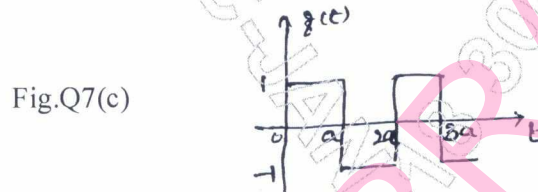
- c. Find the Laplace Transform of non – sinusoidal periodic waveform shown in fig.Q7(c). (04 Marks)



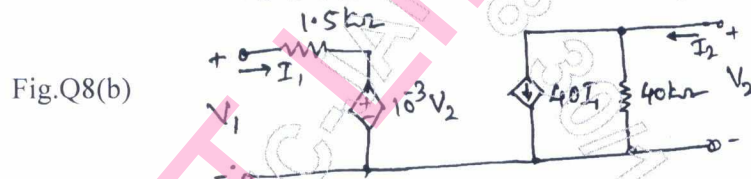- 8 a. Find the Z – transform in terms of Y - parameters. (04 Marks)
 b. For the network shown in fig.Q8(b), find the transmission line parameters. (08 Marks)



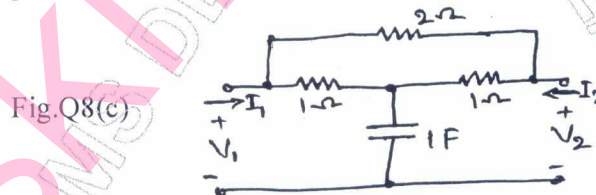- c. Find the h – parameters of the network shown in fig.Q8(c). (08 Marks)



USN

--	--	--	--	--	--	--	--	--	--

10IT35

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Electronic Instrumentation

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting
atleast TWO questions from each part.**

PART – A

- 1 a. The expected value of the voltage across a resistor is 80V. But, the measurement gives a value of 79V. Calculate
 (i) Absolute Error (ii) % Error (iii) Relative Accuracy (iv) % of Accuracy. (05 Marks)
- b. Fig.Q1(b) shows a series circuit of R_1 and R_2 connected to a 100 V dc source. If the voltage across R_2 is to be measured by voltmeters having
 (i) a sensitivity of 1 k Ω /V and (ii) a sensitivity of 20 k Ω /V
 Find which voltmeter will read the accurate value of voltage across R_2 , if both the voltmeters are used on the 50 V range. (10 Marks)

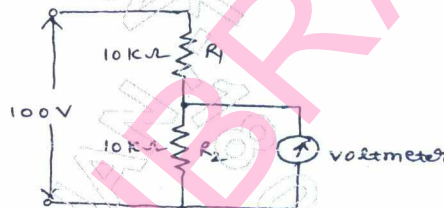


Fig.Q1(b)

- c. Draw the circuit diagram of dc coupled peak voltmeter and illustrate the working principle. Mention the limitations of peak responding voltmeter. (05 Marks)
- 2 a. Discuss about the principle of operation of integrating type DVM with the help of block diagram and associated waveforms. (08 Marks)
- b. With the help of block diagram, explain how a time base with a range of 1 μ s – 1 sec can be generated using fixed frequency crystal oscillator. (05 Marks)
- c. Define the resolution and sensitivity of digital voltmeter. (04 Marks)
- d. Mention the advantages and limitations of Ramp type DVM. (03 Marks)
- 3 a. With the help of block diagram, explain the role of vertical amplifier in deciding the sensitivity and bandwidth of oscilloscope. (08 Marks)
- b. Draw the block diagram of dual beam CRO and illustrate its working principle. (07 Marks)
- c. Discuss the need for delay line in the vertical section of an oscilloscope. (05 Marks)
- 4 a. Explain the working principle of sampling oscilloscope with a neat block diagram and associated waveforms. (10 Marks)
- b. With a neat block diagram and associated waveforms explain the working principle of digital storage oscilloscope. (10 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.
 2. Any revealing of identification, appeal to evaluator and /or equations written eg, 42+8 = 50, will be treated as malpractice.

PART – B

- 5 a. Draw the block diagram of modern laboratory signal generator and explain the function of its constituent blocks. (10 Marks)
- b. Specify the requirements of a pulse which can be generated using pulse generator. (03 Marks)
- c. With a neat block diagram explain how output frequency can be automatically varied over predetermined range using sweep frequency generator. (07 Marks)
- 6 a. Obtain the Thevenin's equivalent circuit of a slightly unbalanced Wheatstone's bridge. Calculate the current through the galvanometer connected between bridge output terminals if the resistance of 3 arms of the bridge is 700Ω each and the resistance of 4th arm of the bridge is 735Ω . (10 Marks)
- b. Derive the expression for unknown capacitance and its leakage resistance in a capacitance comparison bridge. (07 Marks)
- c. Mention the applications of Maxwell bridge and Wein bridge. (03 Marks)
- 7 a. Discuss about the parameters to be considered for any electrical transducer. (05 Marks)
- b. What is a strain gauge? Explain the construction and working principle of semiconductor strain gauge. (06 Marks)
- c. Mention the advantages of thermistor. (04 Marks)
- d. Explain the working principle of variable reluctance type transducer. (05 Marks)
- 8 a. Explain the following with respect to thermocouple:
(i) Seebeck effect
(ii) Thomson effect
(iii) Thermocouple types (07 Marks)
- b. Mention the classification of display devices. (05 Marks)
- c. With a neat sketch explain how RF power can be measured using Bolometer bridge. (08 Marks)

* * * * *

USN

--	--	--	--	--	--	--	--	--	--

10ES36

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Field Theory

Time: 3 hrs.

Max. Marks:100

*Note: Answer FIVE full questions, selecting
at least TWO questions from each part.*

PART – A

- 1
 - a. State and prove gauss law for electrostatics. (06 Marks)
 - b. If $E = (-8xy\hat{a}_x - 4x^2\hat{a}_y + \hat{a}_z)$ V/m. Find the work done in carrying a 6 C charge from A(1, 8, 5) to B(2, 18, 6) along the path $y = 3x + 2$, $z = x + 4$. (06 Marks)
 - c. Four point charges each 20 μC are at A(4, 0, 0), B(-4, 0, 0), C(0, 4, 0), D(0, -4, 0) respectively. Find the force on a 200 μC point charge at (0, 0, 3). (08 Marks)
- 2
 - a. Derive an equation for divergence of flux density in differential form, and hence explain Gauss divergence theorem. (08 Marks)
 - b. A 15 nC point charge is at the origin in free space. Calculate v_1 if point P is located at (2, -3, -1). Also calculate v_1 at P if $v = 0$ at (6, 5, 4). (06 Marks)
 - c. Deduce an expression for energy and energy density in an electro static field. (06 Marks)
- 3
 - a. Using Poisson's equation, obtain the expression for junction potential in a p-n junction. (08 Marks)
 - b. Derive Laplace's equation and hence write the expression for Laplacian of V in cylindrical and spherical co-ordinates. (06 Marks)
 - c. Find E at P(3, 1, 2) for the field of two co-axial conducting cylinders. $V = 50$ V at $r = 2$ m, $V = 20$ V at $r = 3$ m. (06 Marks)
- 4
 - a. Derive an expression for magnetic flux density (\vec{B}) due to straight conductor of finite length. (06 Marks)
 - b. If \vec{H} in a region is $2x\hat{a}_y + (3y - 2)\hat{a}_z$, find the current density at the origin. (06 Marks)
 - c. Given the magnetic field $\vec{H} = 2r^2(z+1)\sin\phi\hat{a}_\phi$, verify Stoke's theorem for the portion of cylindrical surface defined by $r = 2$, $\frac{\pi}{4} < \phi < \frac{\pi}{2}$, $1 < z < 1.5$. (08 Marks)

PART – B

- 5
 - a. Find the magnetic flux density due to long current carrying conductor using vector magnetic potential. (08 Marks)
 - b. Derive the expression for boundary conditions, if the field lines are tangent and normal to the boundary line between two media's in static magnetic field. (06 Marks)
 - c. A solenoid with air core has 2000 turns and a length of 500 mm, core radius 40 mm. Find its inductance. (06 Marks)

- 6 a. Derive the modification of Ampere's circuit law to suit for time varying conditions. (06 Marks)
- b. Explain Maxwell's equations in point and integral form. Establish relationship between conduction current density and displacement current density for the given field $E = E_0 \sin \omega t$ (08 Marks)
- c. Do the fields $E = E_m \sin x \sin t \hat{a}_y$ and $\vec{H} = \frac{E_m}{\mu} \cos x \cos t \hat{a}_z$. Satisfy Maxwell's equations. Verify. (06 Marks)
- 7 a. Derive an expression for electric and magnetic wave equations. (06 Marks)
- b. For an electromagnetic wave propagating in free space, show that $\frac{E}{H} = \eta$. (08 Marks)
- c. Find skin depth and surface resistance of copper conductor at 100 MHz having conductivity $\sigma = 5.8 \times 10^7 \text{ S/m}$ and $\mu_r = 100$. (06 Marks)
- 8 a. Explain the reflection of uniform plane wave with normal incidence at a plane dielectric boundary. (10 Marks)
- b. Write short notes on:
 (i) Reflection co-efficient.
 (ii) Standing wave ratio. (10 Marks)

USN

--	--	--	--	--	--	--	--	--	--

MATDIP301

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018
Advanced Mathematics - I

Time: 3 hrs.

Max. Marks: 100

Note: Answer any FIVE full questions, selecting atleast TWO questions from each part.

PART - A

- 1 a. Find the modulus and amplitude of $\frac{4+2i}{2-3i}$. (06 Marks)
- b. Express the complex number $2+3i+\frac{1}{1-i}$ in the form $a+ib$. (07 Marks)
- c. Simplify $\frac{(\cos 3\theta + i \sin 3\theta)^4 (\cos 4\theta - i \sin 4\theta)^5}{(\cos 4\theta + i \sin 4\theta)^3 (\cos 5\theta + i \sin 5\theta)^{-4}}$. (07 Marks)
- 2 a. Find the n^{th} derivative of $e^{ax} \sin(bx + c)$. (06 Marks)
- b. Find the n^{th} derivative of $\frac{x^2}{2x^2 + 7x + 6}$. (07 Marks)
- c. If $y = e^{a \sin^{-1} x}$, prove that $(1-x^2)y_{n+2} - (2n+1)xy_{n+1} - (n^2+a^2)y_n = 0$. (07 Marks)
- 3 a. If ϕ is the angle between the tangent and radius vector to the curve $r = f(\theta)$ at any point (r, θ) , prove that $\tan \theta = \frac{r d\theta}{dr}$. (06 Marks)
- b. Find the angle of intersection between the curves $r^n = a^n \cos n\theta$ and $r^n = b^n \sin n\theta$. (07 Marks)
- c. Using Maclaurin's series, expand $\tan x$ up to the term containing x^5 . (07 Marks)
- 4 a. If $Z = f(x+ct) + \phi(x-ct)$, prove that $\frac{\partial^2 Z}{\partial t^2} = C^2 \frac{\partial^2 Z}{\partial x^2}$. (06 Marks)
- b. If $u = \sin^{-1} \left(\frac{x^2 + y^2}{x+y} \right)$, prove that $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = \tan u$. (07 Marks)
- c. If $u = f(x-y, y-z, z-x)$, prove that $\frac{\partial u}{\partial x} + \frac{\partial u}{\partial y} + \frac{\partial u}{\partial z} = 0$. (07 Marks)

PART - B

- 5 a. Obtain the reduction formula for $\int \cos^n x dx$. (06 Marks)
- b. Using reduction formula evaluate $\int_0^a \frac{x^7}{\sqrt{a^2 - x^2}} dx$. (07 Marks)
- c. Evaluate $\int_0^1 \int_0^1 e^{x+y} dx dy$. (07 Marks)

- 6 a. Evaluate $\int_0^1 \int_0^2 \int_1^2 x^2 y z \, dx dy dz$. (07 Marks)
- b. Prove that $\beta(m, n) = \frac{\Gamma(m)\Gamma(n)}{\Gamma(m+n)}$. (07 Marks)
- c. Prove that $\Gamma\left(\frac{1}{2}\right) = \sqrt{\pi}$. (06 Marks)
- 7 a. Solve $3e^x \tan y \, dx + (1-e^x) \sec^2 y \, dy = 0$. (06 Marks)
- b. Solve $(2x + 3y + 4)dx + (4x + 6y + 5) \, dy = 0$. (07 Marks)
- c. Solve $\frac{dy}{dx} + y \tan x = \cos x$. (07 Marks)
- 8 a. Solve $\frac{d^2y}{dx^2} + 4\frac{dy}{dx} + 5y = -2 \cos hx$. (06 Marks)
- b. Solve $(D^2 - 4D + 3)y = \sin 3x \cos 2x$. (07 Marks)
- c. Solve $\frac{d^2y}{dx^2} + 4y = x^2 + \cos 2x$. (07 Marks)
