

USN 

--	--	--	--	--	--	--	--	--	--

10MAT31

**Third Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Engineering Mathematics – III**

Time: 3 hrs.

Max. Marks: 100

**Note: Answer any FIVE full questions, selecting at least TWO questions from each part.**

**PART – A**

- 1 a. Find the Fourier series for the function  $f(x) = x + x^2$  over the interval  $-\pi \leq x \leq \pi$ . Hence deduce that:
- i)  $\frac{\pi^2}{12} = \frac{1}{1^2} - \frac{1}{2^2} + \frac{1}{3^2} - \dots$       ii)  $\frac{\pi^2}{6} = \frac{1}{1^2} + \frac{1}{2^2} + \frac{1}{3^2} + \dots$       (07 Marks)
- b. Expand the function  $f(x) = x(\pi - x)$  over the interval  $(0, \pi)$  in half range Fourier cosine series.      (06 Marks)
- c. Find the constant term and the first two harmonics for the function  $f(\theta)$  given by the following table:      (07 Marks)

$\theta$ (in degrees)	0	60	120	180	240	300	360
$f(\theta)$	0.8	0.6	0.4	0.7	0.9	1.1	0.8

- 2 a. Show that the Fourier transform of the function
- $$f(x) = \begin{cases} 1-x^2, & |x| \leq 1 \\ 0, & |x| > 1 \end{cases} \text{ is } F(\alpha) = \frac{2\sqrt{2}}{\alpha^3 \sqrt{\pi}} (\sin \alpha - \alpha \cos \alpha).$$
- Hence deduce that  $\int_0^{\infty} \frac{\sin x - x \cos x}{x^3} dx = \frac{\pi}{4}$ .      (07 Marks)
- b. Find the Fourier cosine transform of  $f(x) = \frac{1}{1+x^2}$ .      (06 Marks)
- c. If the Fourier sine transform of  $f(x)$  is given by  $F_s(u) = \frac{\pi}{2} e^{-2u}$ , find the function  $f(x)$ .      (07 Marks)
- 3 a. Find the various possible solutions of two-dimensional Laplace equation by method of separation of variables.      (07 Marks)
- b. Obtain the D'Alembert's solution of the wave equation  $u_{tt} = c^2 u_{xx}$  subject to the conditions  $u(x, 0) = f(x)$  and  $\frac{\partial u}{\partial t}(x, 0) = 0$ .      (06 Marks)
- c. Solve the one-dimensional heat equation  $c^2 u_{xx} = u_t$ ,  $0 < x < \pi$  subject to the conditions  $u(0, t) = 0$ ,  $u(\pi, t) = 0$ ,  $u(x, 0) = u_0 \sin x$  where  $u_0$  is a non-zero constant.      (07 Marks)

- 4 a. Find a curve of the best fit of the form  $y = ax^b$  to the following data:      (07 Marks)

x	1	2	3	4	5
y	0.5	2	4.5	8	12.5

- b. For conducting a practical examination, the chemistry department of a college requires 10, 12 and 7 units of 3 chemicals x, y and z respectively. The chemicals are available in 2 types of boxes: Box A and Box B. Box A contains 3, 2 and 1 units of x, y, z respectively and cost Rs.300. Box B contains 1, 2 and 2 units of x, y, z respectively and costs Rs.200. Find how many boxes of each type should be bought by the department so that the total cost is minimum. Solve graphically.      (06 Marks)

Important Note : 1. On completing your answers, compulsorily draw diagonal cross lines on the remaining blank pages.  
2. Any revealing of identification, appeal to evaluator and /or equations written eg, 4+2+8 = 50, will be treated as malpractice.

c. Solve the following LPP by simplex method:

Maximize  $z = 2x_1 + 4x_2 + 3x_3$

Subject to the constraints  $3x_1 + 4x_2 + 2x_3 \leq 60$

$2x_1 + x_2 + 2x_3 \leq 40$

$x_1 + 3x_2 + 2x_3 \leq 80$

$x_1, x_2, x_3 \geq 0$

(07 Marks)

**PART – B**

5 a. Use Newton-Raphson method to find an approximate root of the equation  $x \log_{10} x = 1.2$  correct to 5 decimal places that is near 2.5. (07 Marks)

b. Use Relaxation method to solve the following system of linear equations:

$8x + 3y + 2z = 13$

$x + 5y + z = 7$

$2x + y + 6z = 9$

(06 Marks)

c. Find the numerically largest eigen value and the corresponding eigen vector of the matrix

$$A = \begin{bmatrix} 5 & 0 & 1 \\ 0 & -2 & 0 \\ 1 & 0 & 5 \end{bmatrix}$$

by power method taking  $X^{(0)} = [1 \ 0 \ 0]^T$ . Perform 6 iterations. (07 Marks)

6 a. Find the interpolating polynomial for the function  $y = f(x)$  given by  $f(0) = 1, f(1) = 2, f(2) = 1, f(3) = 10$ . Hence evaluate  $f(0.75)$  and  $f(2.5)$ . (07 Marks)

b. Apply Lagrange's method to find the value of  $x$  corresponding to  $f(x) = 15$  from the following data: (06 Marks)

x	5	6	9	11
f(x)	12	13	14	16

c. Evaluate  $\int_0^1 \frac{dx}{1+x^2}$  by using Simpson's  $\frac{3}{8}$  rule dividing the interval (0, 1) into 6 equal parts.

Hence deduce the approximate value of  $\pi$ .

(07 Marks)

7 a. Solve the wave equation  $u_{tt} = 4u_{xx}$  subject to the conditions  $u(0, t) = 0, u(4, t) = 0, u_t(x, 0) = 0$  and  $u(x, 0) = x(4 - x)$  by taking  $h = 1, k = 0.5$  upto four steps. (07 Marks)

b. Find the numerical solution of the equation  $u_{xx} = u_t$  when  $u(0, t) = 0, u(1, t) = 0, t \geq 0$  and

$u(x, 0) = \sin \pi x, 0 \leq x \leq 1$ . Carryout computations for two levels taking  $h = \frac{1}{3}$  and  $k = \frac{1}{36}$ .

(07 Marks)

c. Solve Laplace's equation  $u_{xx} + u_{yy} = 0$  for the following square mesh with boundary values as shown in the following Fig.Q7(c).

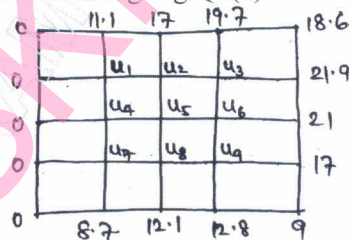


Fig.Q7(c)

(06 Marks)

8 a. Find the z-transform of  $5n^2 + 4 \cos \frac{n\pi}{2} - 4^{n+2}$  and  $\sinh n\theta$ . (06 Marks)

b. Obtain in inverse z-transform of  $\frac{z(2z+3)}{(z+2)(z-4)}$ . (07 Marks)

c. Using z-transforms, solve  $u_{n+2} + 3u_{n+1} + 2u_n = 3^n$  given  $u_0 = 0, u_1 = 1$ . (07 Marks)

\*\*\*\*\*

**Third Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Analog Electronic Circuits**

Time: 3 hrs.

Max. Marks:100

**Note: Answer FIVE full questions, selecting at least TWO questions from each part.**

**PART - A**

- 1 a. Using Shockley's equation, determine the diode current at  $25^\circ\text{C}$  for a silicon diode with  $I_S = 20 \text{ pA}$  and  $V_D = 0.7 \text{ V}$ . Find the same when  $V_D = 0.5 \text{ V}$ . (04 Marks)  
 b. Sketch the output waveform for the following circuit shown in Fig. Q1 (b), and plot the transfer characteristics - (06 Marks)

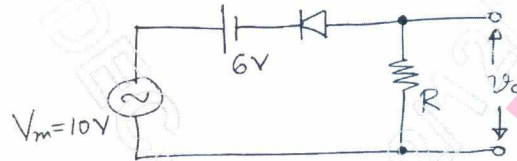


Fig. Q1 (b)

- c. Check the condition for the following circuit shown in Fig. Q1 (c) to work as clamper. Sketch the output waveform. (05 Marks)

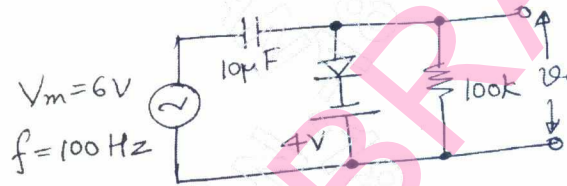


Fig. Q1 (c)

- d. Find the current in the loop, the output voltage, and the power absorbed by each device. (05 Marks)

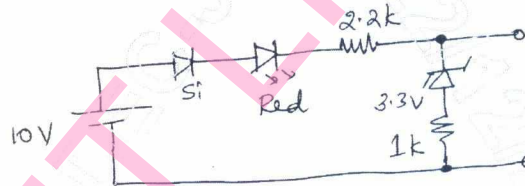


Fig. Q1 (d)

- 2 a. Derive the expression for  $I_B$  and  $V_{CE}$  of an emitter bias circuit. (04 Marks)  
 b. Check the condition for the approximate analysis of the voltage-divider bias circuit and obtain the Q-point using approximate analysis, given :  $V_{CC} = +12 \text{ V}$ ,  $\beta = 120$ ,  $R_C = 1.5 \text{ K}\Omega$ ,  $R_E = 620 \Omega$ ,  $R_1 = 33 \text{ k}\Omega$  and  $R_2 = 4.7 \text{ k}\Omega$ . Mark the Q-point on the DC load - line. (06 Marks)  
 c. Determine the values for the following circuit:  $V_E$ ,  $I_E$ ,  $V_{CE}$ ,  $V_C$ ,  $I_B$  and  $\beta$ . (06 Marks)

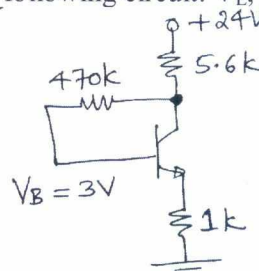


Fig. Q2 (c)

- d. Design a fixed bias circuit for  $V_{CC} = 10 \text{ V}$ ,  $\beta = 120$ ,  $I_{CQ} = 1.4 \text{ mA}$  and  $V_{CEQ} = 5 \text{ V}$ .

(04 Marks)



- 3 a. Using  $r_c$  model, derive the expressions for  $Z_i$ ,  $Z_o$  and  $A_V$  of a fixed bias circuit. (06 Marks)  
 b. Using exact analysis, determine  $Z_i$ ,  $Z_o$  and  $A_V$  for the voltage-divider bias network if  $R_1 = 220 \text{ k}\Omega$ ,  $R_2 = 56 \text{ k}\Omega$ ,  $R_C = 6.8 \text{ k}\Omega$ ,  $R_E = 2.2 \text{ k}\Omega$ ,  $\beta = 180$ ,  $r_o = 50 \text{ k}\Omega$  and  $V_{CC} = 20\text{V}$ . (10 Marks)  
 c. For the network shown in Fig. Q3 (c), determine  $Z_i$ ,  $Z_o$  and  $A_V$  - (04 Marks)

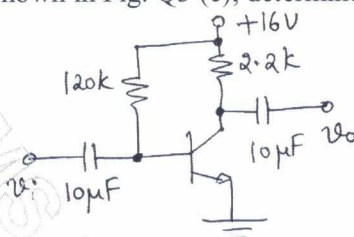


Fig. Q3 (c)

- 4 a. Explain the frequency response curves for RC-coupled, transformer-coupled and direct-coupled amplifiers, with reasons for the drop in gain. (09 Marks)  
 b. Determine the mid-band gain and the lower cut-off frequencies  $f_{L_s}$  and  $f_{L_c}$  for the voltage-divider bias BJT amplifier with  $C_S = 10 \mu\text{F}$ ,  $C_C = 10 \mu\text{F}$ ,  $R_S = 1 \text{ k}\Omega$ ,  $R_1 = 36 \text{ k}\Omega$ ,  $R_2 = 8.2 \text{ k}\Omega$ ,  $R_E = 1.5 \text{ k}\Omega$ ,  $R_C = 4.7 \text{ k}\Omega$ ,  $R_L = 2.2 \text{ k}\Omega$ ,  $\beta = 100$  and  $V_{CC} = 20\text{V}$ . (11 Marks)

### PART - B

- 5 a. For a Darlington connection, derive the expressions for  $Z_i$ ,  $Z_o$ ,  $A_i$  and  $A_V$ . (12 Marks)  
 b. Mention the advantages and disadvantages of the negative feedback. (04 Marks)  
 c. Calculate the gain, input impedance and output impedance of a voltage-series-feedback amplifier having  $A = -300$ ,  $R_i = 1.5 \text{ k}\Omega$ ,  $R_o = 50 \text{ k}\Omega$  and  $\beta = -\frac{1}{15}$ . (04 Marks)
- 6 a. Enumerate the types of power amplifiers along with their efficiency, conduction angle and Q-point. (05 Marks)  
 b. Prove that the maximum efficiency of a class-B power amplifier is 78.5%. (05 Marks)  
 c. Calculate the efficiency of the following circuit shown in Fig. Q6 (c), for an input current swing of 10 mA. (05 Marks)

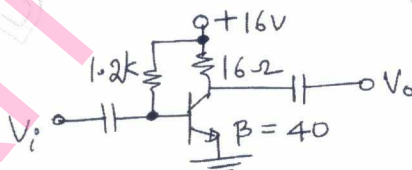


Fig. Q6 (c)

- d. Along with the circuit diagram, explain the working of Class-C amplifier. (05 Marks)
- 7 a. Along with the circuit diagram, explain the working of a BJT phase-shift oscillator. (06 Marks)  
 b. Design a Wien-bridge oscillator for  $f_0 = 6 \text{ kHz}$ , making suitable assumptions. (06 Marks)  
 c. Along with proper diagrams, explain the series resonant and parallel resonant crystal oscillators using BJT. (08 Marks)
- 8 a. Explain the operation of JFET amplifier using fixed bias. Draw the JFET small signal model, and derive the expressions for  $Z_i$ ,  $Z_o$  and  $A_V$ . (10 Marks)  
 b. With necessary circuit diagram, obtain the expressions for  $Z_i$ ,  $Z_o$  and  $A_V$  for an E-MOSFET voltage-divider configuration. (10 Marks)

\*\*\*\*\*

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Logic Design**

Time: 3 hrs.

Max. Marks:100

**Note: Answer any FIVE full questions, selecting  
atleast TWO questions from each part.**

**PART – A**

- 1 a. Represent the canonical minterm forms in decimal notation :
  - i)  $f_1 = x\bar{y} + yz$
  - ii)  $f_2 = \bar{a}c + bc\bar{d} + ad$ . (05 Marks)
- b. Show that  $f(a, b, c, d) = \sum m(0, 1, 2, 5, 6, 8, 9, 10, 13, 14) = \pi M(3, 4, 7, 11, 12, 15)$ . (08 Marks)
- c. Simplify the following Boolean function and realize the simplified expression using basic gates.  
 $f(a, b, c, d, e) = \sum m(0, 1, 4, 8, 9, 11, 15, 16, 24, 26) + dm(10, 20, 22, 23, 25, 27, 31)$ . (07 Marks)
- 2 a. Simplify the Boolean function  $f(a, b, c, d) = \sum m(0, 1, 2, 7, 8, 9, 10, 13, 15)$  using Quine – Mc Cluskey tabulation method and verify the answer using k-map. (10 Marks)
- b. Simplify the Boolean function  $f(a, b, c, d) = \sum m(0, 2, 3, 4, 5, 8, 10, 11) + dm(7, 13, 14)$  using Map entered variable k-map. With “d” as map entered variable, verify the answer using k-map,. (10 Marks)
- 3 a. Design a combinational circuit using basic gates to convert excess 3 binary code to BCD code. (10 Marks)
- b. Implement full adder using decoder. (05 Marks)
- c. Design a 4 to 16 decoder using 3 to 8 decoders. (05 Marks)
- 4 a. Design a 4 bit BCD adder circuit using 7483IC with self correcting circuit. That is a provision to be made in the circuit, in case the sum of BCD exceeds 9. (10 Marks)
- b. Realize the Boolean function  $f(a, b, c) = \sum m(0, 1, 4, 5, 6)$  using 4 : 1 mux. (05 Marks)
- c. Explain look – ahead carry adder and give its advantages and disadvantages. (05 Marks)

**PART – B**

- 5 a. Obtain characteristic equation of a S-R flip-flop. (05 Marks)
- b. Explain the working of an universal shift register. (05 Marks)
- c. Explain the working of a master –slave JK flip-flop with timing diagram for master and slave. Show how race around condition is eliminated. (10 Marks)
- 6 a. Design an asynchronous mod-8 counter using JK flip-flop and draw its timing diagram. (10 Marks)
- b. Explain why asynchronous counter is called ripple counter. (05 Marks)
- c. Explain mealy and Moore sequential circuit models. (05 Marks)

- 7 a. Draw and explain Moore JK flip-flop state diagram. (05 Marks)  
 b. For the state machine shown Fig.Q7(b) obtain : i) state table ii) Transition table  
 iii) excitation table for JK flip-flop iv) logic diagram. (15 Marks)

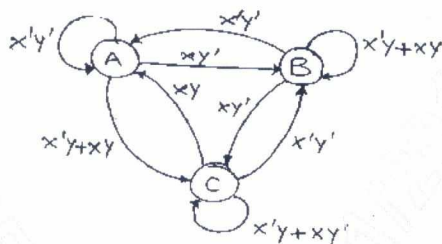


Fig.Q7(b)


- 8 a. Design a cyclic BCD up synchronous counter using  $\tau$  flip-flops. (10 Marks)  
 b. Design a cyclic synchronous counter using D flip-flops to generate a sequence of 5421 code.  
 (Hint : 0, 1, 2, 3, 4, 8, 9, 10, 11, 12 0, 1 - - - - ) sequence. (10 Marks)

\*\*\*\*\*






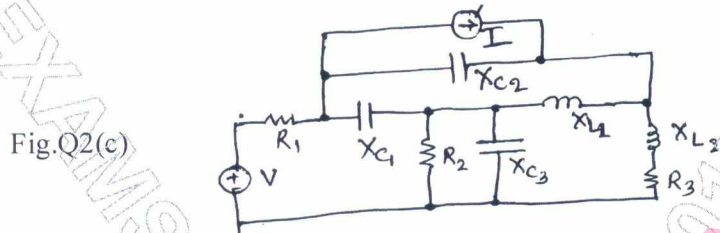
- c. Draw the oriented graph for the circuit shown in fig.Q2(c). Also find fundamental cut – set schedule using  $X_{c1}$ ,  $R_2$  and  $X_{L1}$  or the twigs of the tree. Find admittance matrix also. (04 Marks)



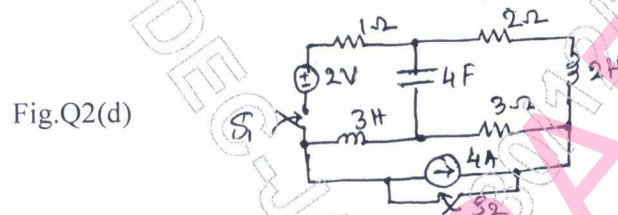
- d. Find the dual of the circuit shown in fig.Q2(d). (03 Marks)



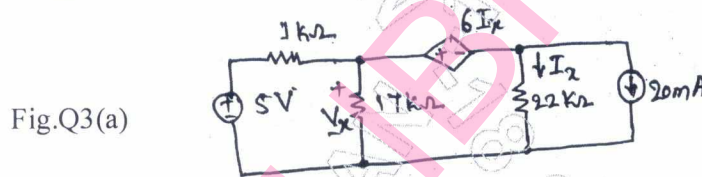- 3 a. Find  $V_x$  using superposition for the circuit shown in fig.Q3(a). (08 Marks)




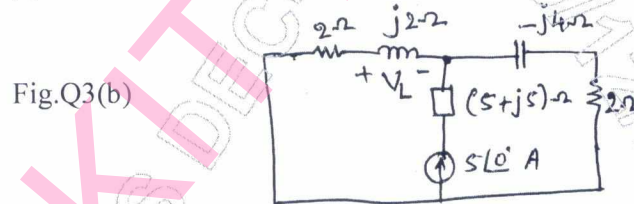- b. Find the voltage  $V_L$  across the inductor and verify reciprocity theorem for the circuit shown in Fig.Q3(b). (06 Marks)



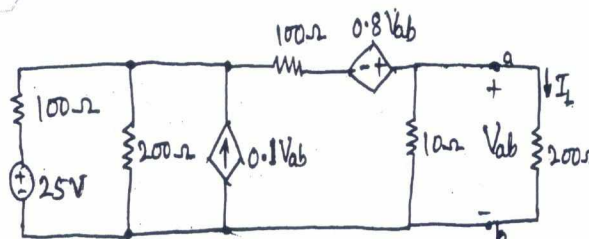- c. State and prove Milliman's theorem. (06 Marks)

- 4 a. Find the Thevenin's equivalent circuit across terminals a & b for the circuit shown in fig.Q4(a). Also find the current  $I_L$  using this equivalent circuit. (08 Marks)




- b. State and prove Norton's theorem. (05 Marks)



- c. Find  $Z_L$  for maximum power transfer for the circuit shown in fig.Q4(c). And also find the average maximum power absorbed by  $Z_L$ . (07 Marks)


Fig.Q4(c)

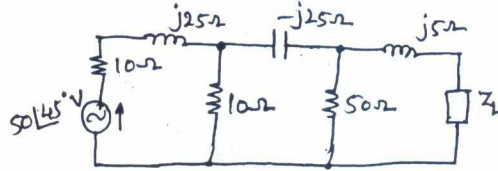

**PART - B**


- 5 a. For the circuit shown in fig.Q5(a), find the transfer function, resonant frequency half power frequencies, bandwidth and Q - factor. (10 Marks)

Fig.Q5(a)

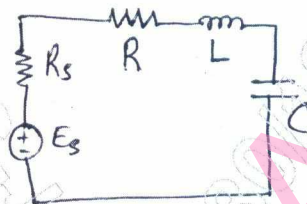


- b. Define the term Q - factor. Using this definition find the Q - factor of an inductor and a capacitor. (05 Marks)  
 c. For the network shown in fig.Q5(c), find the value of C for resonance to take place at  $\omega = 5000$  rad/s. (05 Marks)

Fig.Q5(c)

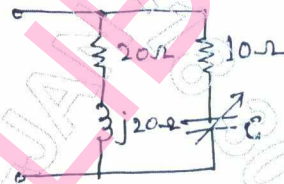


- 6 a. Write a short note on Initial and Final conditions of circuit elements under switching conditions. (06 Marks)  
 b. In the circuit shown in fig.Q6(b), the switch  $S_1$  has been open for a long time before closing at  $t = 0$ . Find  $V_c(0^+)$ ,  $i_L(0^+)$ ,  $V_c(\infty)$ ,  $i_L(\infty)$ ,  $\frac{di_L}{dt}(0^+)$  and  $\frac{d^2i_L}{dt^2}(0^+)$ . (06 Marks)

Fig.Q6(b)

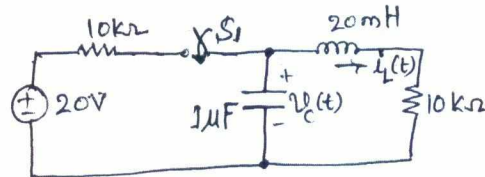


- c. For the circuit shown in fig.Q6(c), calculate  $i_L(0^+)$ ,  $\frac{di_L}{dt}(0^+)$ ,  $\frac{d}{dt}V_c(0^+)$ ,  $V_R(\infty)$ ,  $V_c(\infty)$  and  $i_L(\infty)$ . (08 Marks)


Fig.Q6(c)

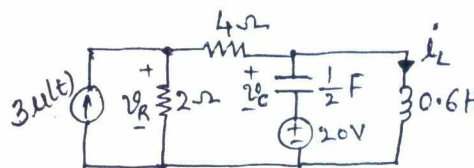

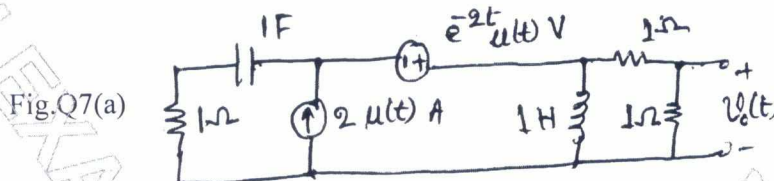
- 7 a. Find  $V_o(t)$  of the circuit shown in fig.Q7(a). (10 Marks)



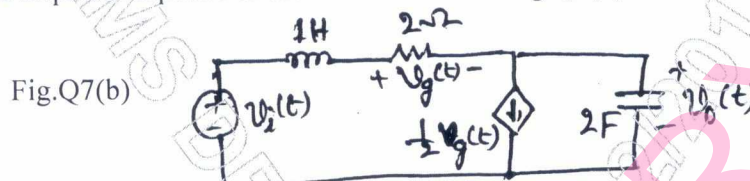
- b. Find the impulse response of the circuit shown in fig.Q7(b). (06 Marks)



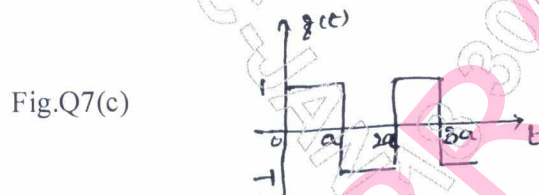
- c. Find the Laplace Transform of non – sinusoidal periodic waveform shown in fig.Q7(c). (04 Marks)



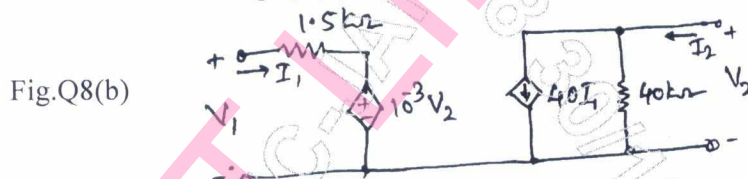- 8 a. Find the Z – transform in terms of Y - parameters. (04 Marks)  
 b. For the network shown in fig.Q8(b), find the transmission line parameters. (08 Marks)



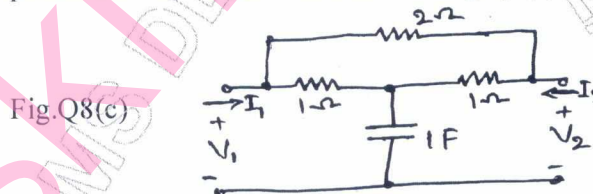- c. Find the h – parameters of the network shown in fig.Q8(c). (08 Marks)



\*\*\*\*\*

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Third Semester B.E. Degree Examination, Dec.2017/Jan.2018

## Electrical & Electronic Measurements & Instrumentation

Time: 3 hrs.

Max. Marks:100

Note: Answer FIVE full questions, selecting at least TWO questions from each part.

### PART – A

- 1 a. Define the following:
  - (i) SI units
  - (ii) Fundamental units
  - (iii) Absolute units
  - (iv) Derived units. (04 Marks)
- b. The expression for eddy current loss P per meter length of the wire may be written as  $P_e \propto f^a B_m^b d^c \rho^g$  where f = frequency,  $B_m$  = maximum flux density, d = diameter of wire,  $\rho$  = resistivity and a, b, c and g are constants. Determine the values of a, b, c, g from the dimensions of equation in LMTI system. (07 Marks)
- c. Obtain Wheatstone bridge sensitivity in terms of the parameters of the bridge. (09 Marks)
- 2 a. With the help of neat diagram, explain the working of a Megger, used for the measurement of earth resistance. (08 Marks)
- b. Explain how Anderson bridge is used for measurement of inductance of the coil. (08 Marks)
- c. Write a note on shielding of bridges. (04 Marks)
- 3 a. What are shunts and multipliers? Derive an expression for both, with reference to the meters with which they are used in electrical circuits. (08 Marks)
- b. Explain the working of CT and PT with phasor diagrams and applications of the same. (08 Marks)
- c. Write a note on turns compensation used in CTs. (04 Marks)
- 4 a. Explain the construction and working principle of single phase induction type energymeter. What are the adjustments required for error calibration? (10 Marks)
- b. With a neat diagram, explain the construction and operation of the electro-dynamometer type wattmeter. (06 Marks)
- c. A 3 phase 500 V motor load has a power factor of 0.4. Two wattmeters are connected to measure the input. They show that input to be 30 KW. Find the reading of each instrument. (04 Marks)

### PART – B

- 5 a. How are Digital Volt Meters (DVM) are classified? Explain with neat circuit diagram, the working of successive approximation type of DVM. (07 Marks)
- b. Explain the construction and operation of Weston frequency meter. (08 Marks)
- c. A coil is tuned to resonance at 600 kHz with a resonating capacitance of 40 pF. At 300 kHz, the resonance is obtained with a resonating capacitance of 175 pF. Find the self-capacitance of the coil and its inductance. (05 Marks)
- 6 a. With a neat block diagram, explain the working of a digital storage oscilloscope. (10 Marks)
- b. Explain the front panel details of a typical dual trace oscilloscope. (10 Marks)
- 7 a. Explain with a neat sketch, the construction and working of a LVDT. (08 Marks)
- b. What are the different types of strain gauges? Derive an expression for the gauge factor. (08 Marks)
- c. Explain the classification and selection of the transducers. (04 Marks)
- 8 a. Explain with a block diagram, the functional operation of digital data acquisition system and mention its uses. (08 Marks)
- b. With a neat sketch, explain the working of X-Y recorders. (07 Marks)
- c. Write a note on display devices. (05 Marks)

\* \* \* \* \*



USN

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

10EE36

**Third Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Electric Power Generation**

Time: 3 hrs.

Max. Marks:100

*Note: Answer FIVE full questions, selecting  
at least TWO questions from each part.*

**PART – A**

- 1 a. With a neat block diagram, explain the working of a Geo-thermal power plant. (08 Marks)
- b. Explain with diagrams the working of a single basin and double basin tidal power plant. (06 Marks)
- c. What is co-generation? Discuss benefits of it. (06 Marks)
- 2 a. With a neat block diagram explain in brief the main components of a diesel power plant. (10 Marks)
- b. Discuss the applications of 'distributed generation' in brief. (05 Marks)
- c. Explain in brief working of a bio-generation plant. (05 Marks)
- 3 a. Explain the thermal power station with a neat block diagram. (08 Marks)
- b. List the factors to be considered for the selection of site for a hydro – electric power station. (06 Marks)
- c. Classify the Hydro – electric plants based on :
  - i) Water flow regulation
  - ii) head
  - iii) Load
 (06 Marks)
- 4 a. Explain briefly with neat diagram components of a nuclear reactor. (10 Marks)
- b. Mention advantages and disadvantages of CANDU type reactor. (06 Marks)
- c. Describe briefly the working of pressurized water reactor. (04 Marks)

**PART – B**

- 5 a. Explain the following terms as applied to power system :
  - i) Load factor
  - ii) Plant capacity factor
  - iii) Plant use factor
  - iv) Diversity factor. (08 Marks)
- b. A generating station has a M.D of 80 MW, a Load factor of 65%, a plant capacity factor of 40% and a plant use factor of 85%. Find :
  - i) Daily energy produced
  - ii) Reserve capacity of the plant
  - iii) Maximum energy that could be produced daily if the plant runs for 12hrs at full load
  - iv) Energy produced/yr (12 Marks)
- 6 a. What is tariff? Explain : i) Block rate tariff ii) P.f tariff (08 Marks)
- b. A generating station has a M.D of 100 MW. Calculate the cost per unit generated from the following data :
 

Capital cost = Rs  $200 \times 10^6$  ; Annual Load factor = 40%

Annual cost of fuel and oil = Rs  $15 \times 10^6$

Taxes wages and salaries etc = Rs  $10 \times 10^6$

Interest and depreciation = 15% (12 Marks)
- 7 a. Mention the advantages and disadvantages of neutral grounding. (06 Marks)
- b. Explain solid grounding with neat sketches. (08 Marks)
- c. Discuss merits and demerits of resistance grounded system. (06 Marks)
- 8 a. With a schematic arrangement and phasor diagram, explain the Arc – Suppression coil grounding. (10 Marks)
- b. Explain about resistance grounding. (05 Marks)
- c. Explain about earthing transformer. (05 Marks)

\* \* \* \* \*

USN

--	--	--	--	--	--	--	--	--	--

MATDIP301

**Third Semester B.E. Degree Examination, Dec.2017/Jan.2018**  
**Advanced Mathematics - I**

Time: 3 hrs.

Max. Marks: 100

**Note:** Answer any FIVE full questions, selecting atleast TWO questions from each part.

**PART - A**

- 1 a. Find the modulus and amplitude of  $\frac{4+2i}{2-3i}$ . (06 Marks)
- b. Express the complex number  $2+3i+\frac{1}{1-i}$  in the form  $a+ib$ . (07 Marks)
- c. Simplify  $\frac{(\cos 3\theta + i \sin 3\theta)^4 (\cos 4\theta - i \sin 4\theta)^5}{(\cos 4\theta + i \sin 4\theta)^3 (\cos 5\theta + i \sin 5\theta)^{-4}}$ . (07 Marks)
- 2 a. Find the  $n^{\text{th}}$  derivative of  $e^{ax} \sin(bx + \ell)$ . (06 Marks)
- b. Find the  $n^{\text{th}}$  derivative of  $\frac{x^2}{2x^2 + 7x + 6}$ . (07 Marks)
- c. If  $y = e^{a \sin^{-1} x}$ , prove that  $(1-x^2)y_{n+2} - (2n+1)xy_{n+1} - (n^2+a^2)y_n = 0$ . (07 Marks)
- 3 a. If  $\phi$  is the angle between the tangent and radius vector to the curve  $r = f(\theta)$  at any point  $(r, \theta)$ , prove that  $\tan \theta = \frac{rd\theta}{dr}$ . (06 Marks)
- b. Find the angle of intersection between the curves  $r^n = a^n \cos n\theta$  and  $r^n = b^n \sin n\theta$ . (07 Marks)
- c. Using Maclaurin's series, expand  $\tan x$  up to the term containing  $x^5$ . (07 Marks)
- 4 a. If  $Z = f(x+ct) + \phi(x-ct)$ , prove that  $\frac{\partial^2 Z}{\partial t^2} = C^2 \frac{\partial^2 Z}{\partial x^2}$ . (06 Marks)
- b. If  $u = \sin^{-1} \left( \frac{x^2 + y^2}{x+y} \right)$ , prove that  $x \frac{\partial u}{\partial x} + y \frac{\partial u}{\partial y} = \tan u$ . (07 Marks)
- c. If  $u = f(x-y, y-z, z-x)$ , prove that  $\frac{\partial u}{\partial x} + \frac{\partial u}{\partial y} + \frac{\partial u}{\partial z} = 0$ . (07 Marks)

**PART - B**

- 5 a. Obtain the reduction formula for  $\int \cos^n x dx$ . (06 Marks)
- b. Using reduction formula evaluate  $\int_0^a \frac{x^7}{\sqrt{a^2 - x^2}} dx$ . (07 Marks)
- c. Evaluate  $\int_0^1 \int_0^1 e^{x+y} dx dy$ . (07 Marks)

- 6 a. Evaluate  $\int_0^1 \int_0^2 \int_0^2 x^2 y z \, dx dy dz$ . (07 Marks)
- b. Prove that  $\beta(m, n) = \frac{\Gamma(m)\Gamma(n)}{\Gamma(m+n)}$ . (07 Marks)
- c. Prove that  $\Gamma\left(\frac{1}{2}\right) = \sqrt{\pi}$ . (06 Marks)
- 7 a. Solve  $3e^x \tan y \, dx + (1-e^x) \sec^2 y \, dy = 0$ . (06 Marks)
- b. Solve  $(2x + 3y + 4)dx + (4x + 6y + 5) \, dy = 0$ . (07 Marks)
- c. Solve  $\frac{dy}{dx} + y \tan x = \cos x$ . (07 Marks)
- 8 a. Solve  $\frac{d^2y}{dx^2} + 4\frac{dy}{dx} + 5y = -2 \cos hx$ . (06 Marks)
- b. Solve  $(D^2 - 4D + 3)y = \sin 3x \cos 2x$ . (07 Marks)
- c. Solve  $\frac{d^2y}{dx^2} + 4y = x^2 + \cos 2x$ . (07 Marks)

\*\*\*\*\*